

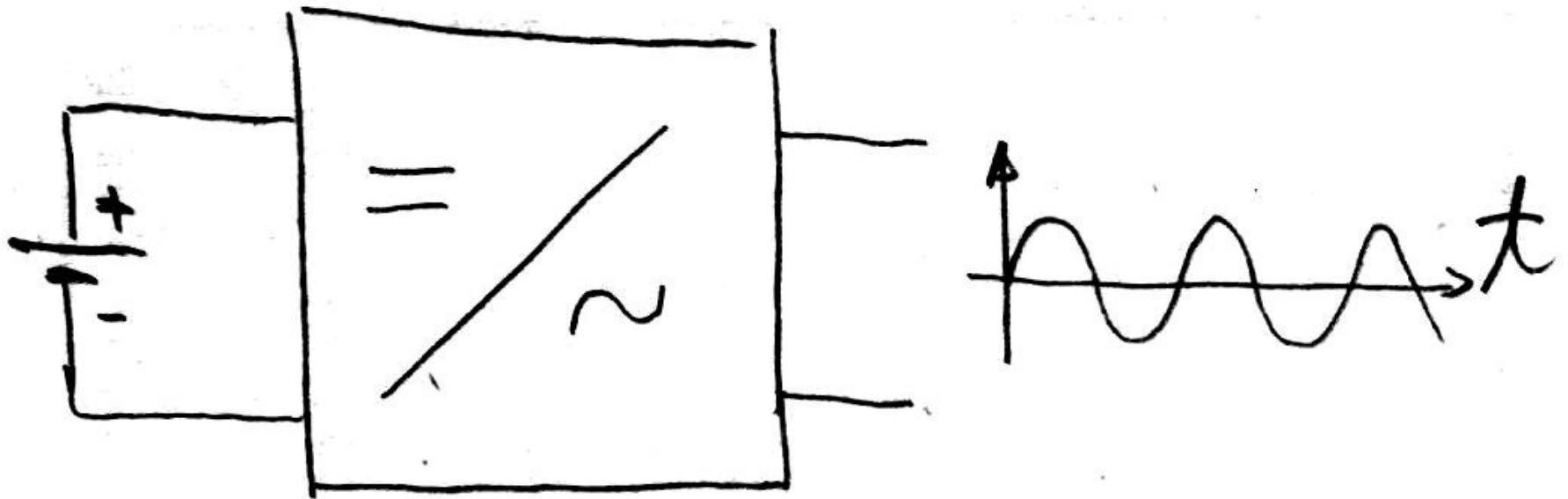


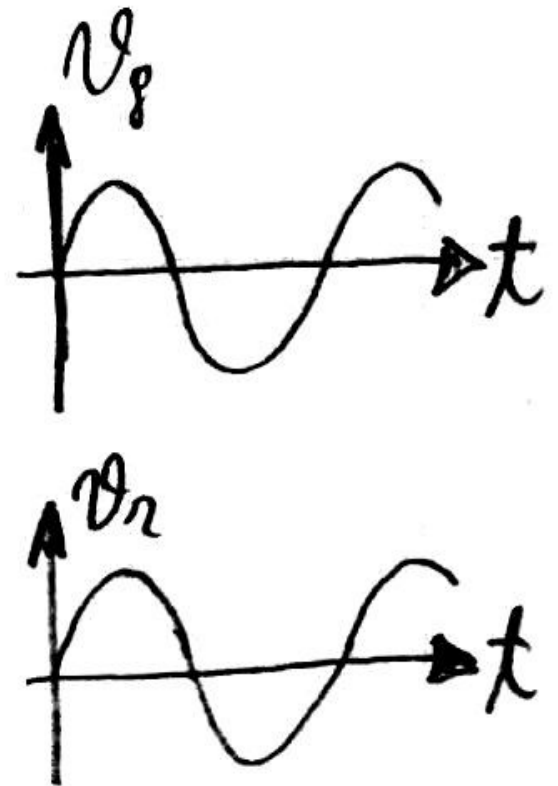**OSCILLATORI**

Oscilator pretvara jednosmjernu energiju u naizmjenicnu






# Od pojačavaca do oscilatora

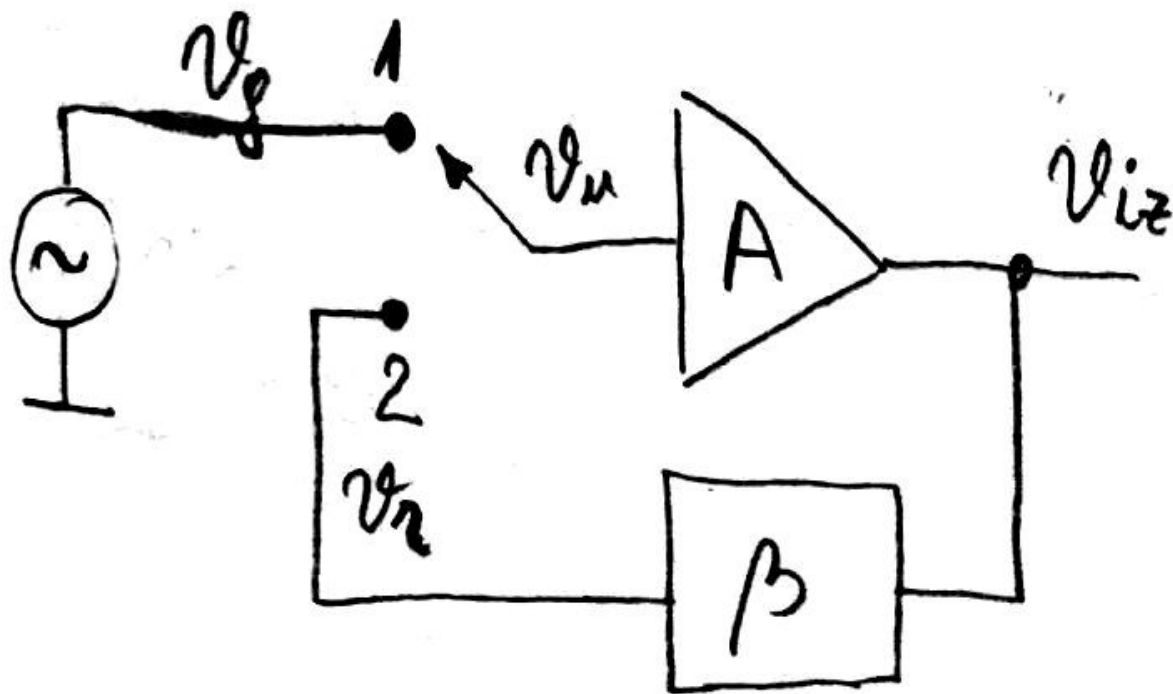

# Uslov oscilovanja

$$A_{\beta} = 1 \begin{cases} \Rightarrow \begin{cases} \operatorname{Re}\{A_{\beta}\} = 1 \\ \operatorname{Im}\{A_{\beta}\} = 0 \end{cases} \\ \Downarrow \begin{cases} |A_{\beta}| = 1 \\ \operatorname{Arg}\{A_{\beta}\} = \phi = 0 \end{cases} \end{cases}$$

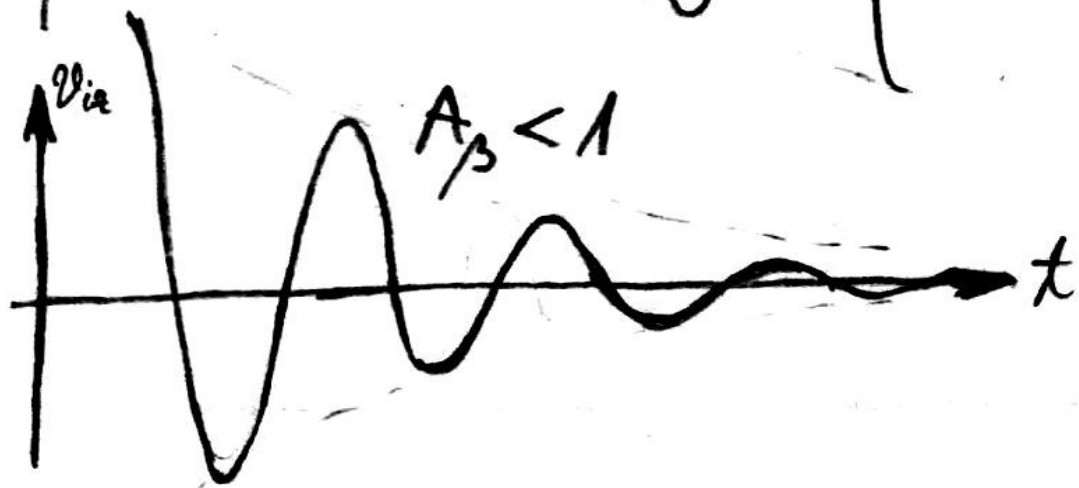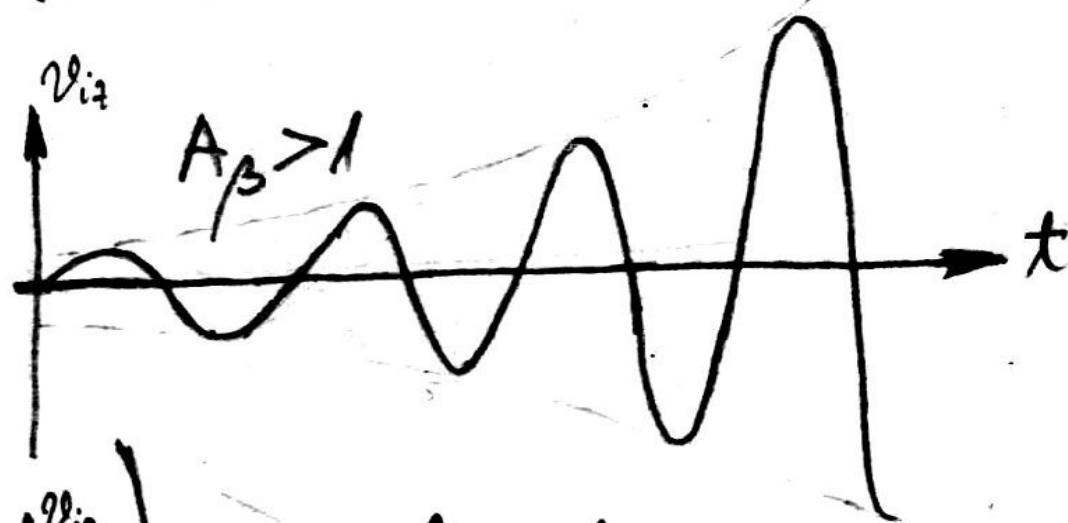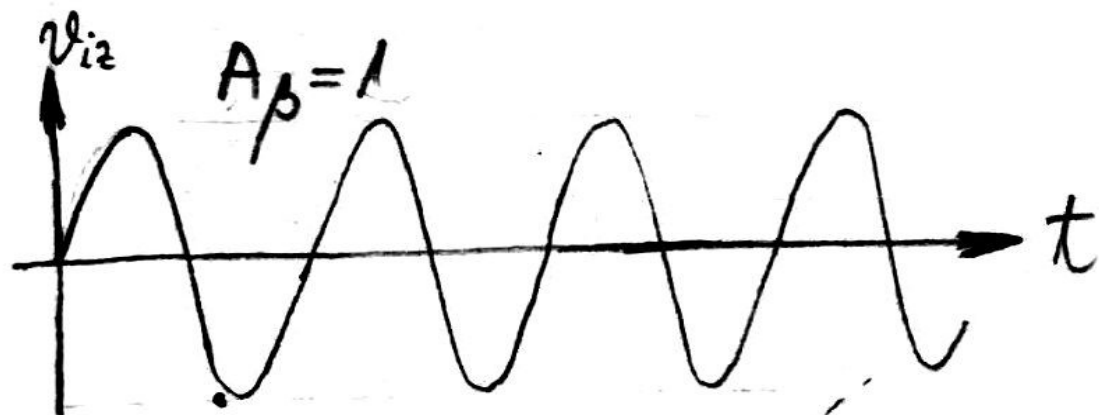


Od  $A_{\beta}$   
zavisi da  
li ce  
oscilacije  
biti:  
stalne  
rastuce ili  
opadajuće


Da li ovo kolo ima  $A_{\beta}=1$ ?

Sta se desava kada se spoji i  $R_p$ ?


$$A_{\beta} = 1 \quad ?$$

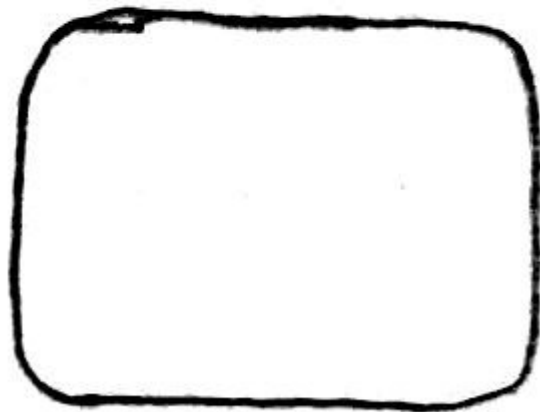

Naci fosc i potreban odnos  $R/R_1$ .

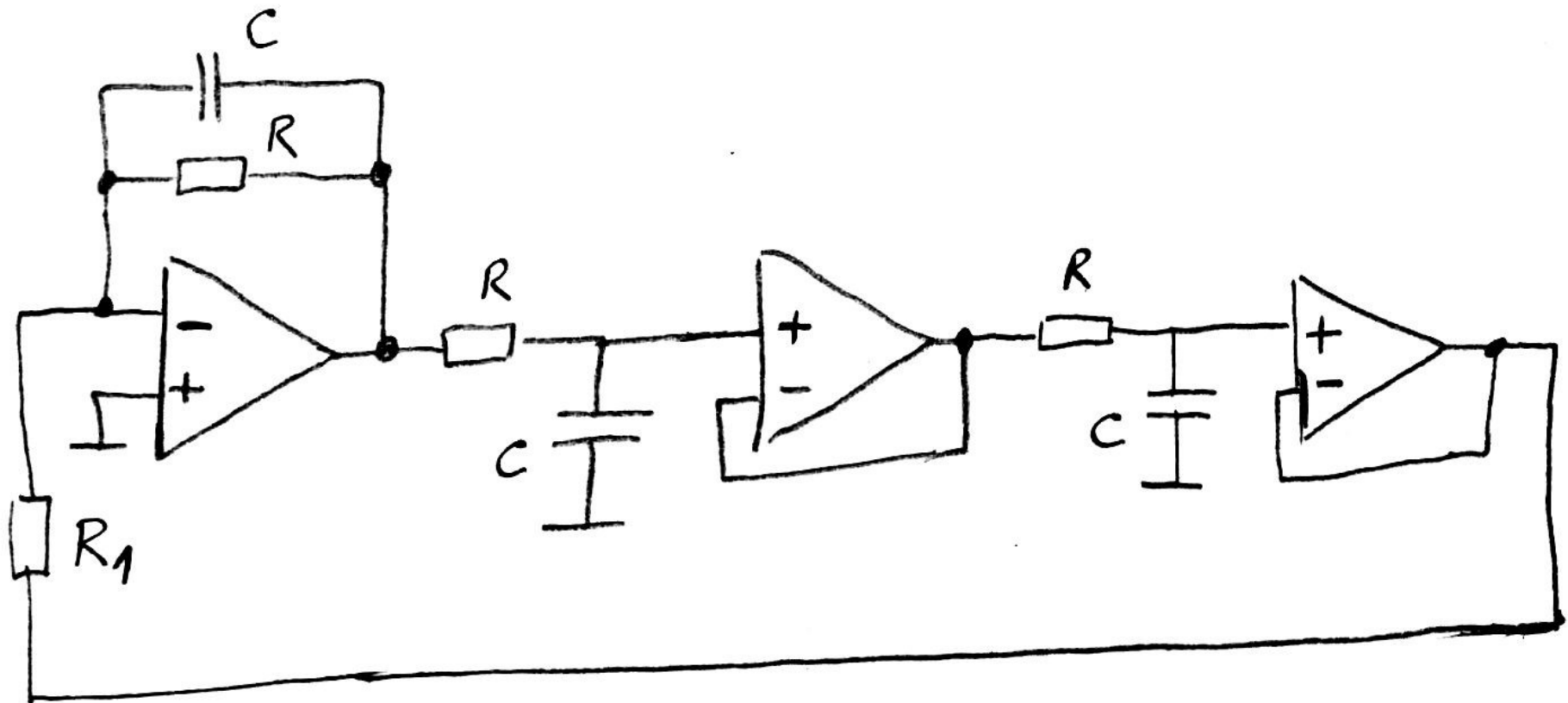

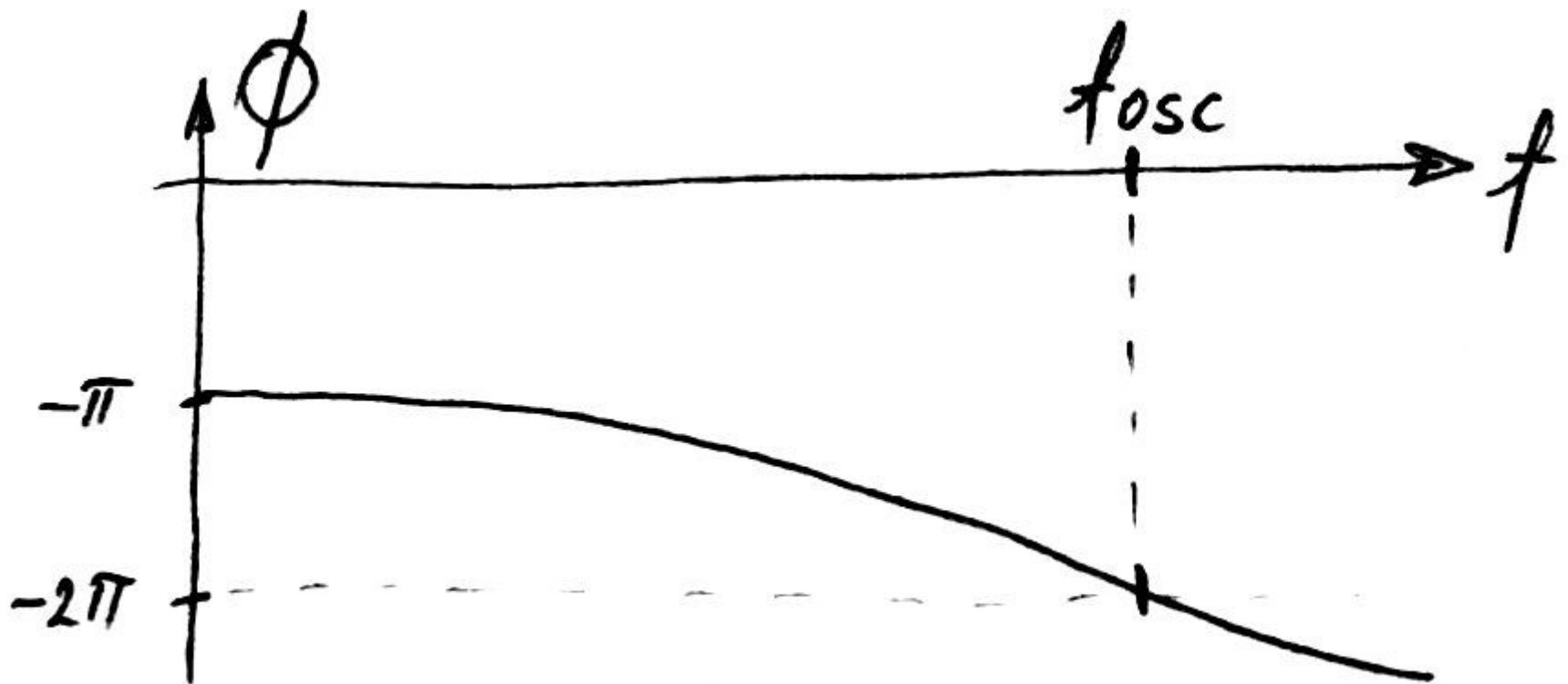Ucestanost oscilovanja  $f_{osc}$  ce biti u tacki gdje je fazni pomak jednak  $2 \cdot N \cdot \pi$










HARMONIC MIXER

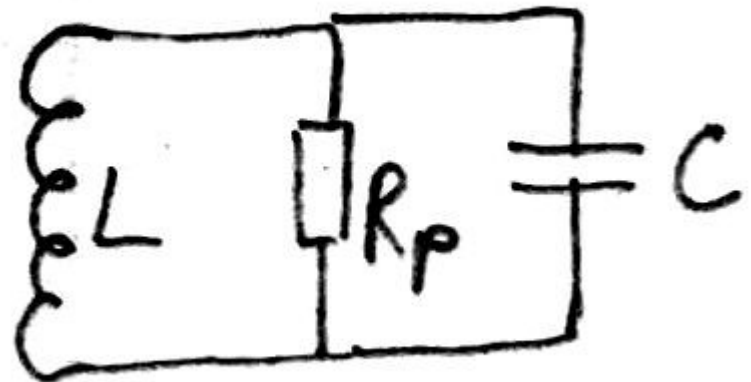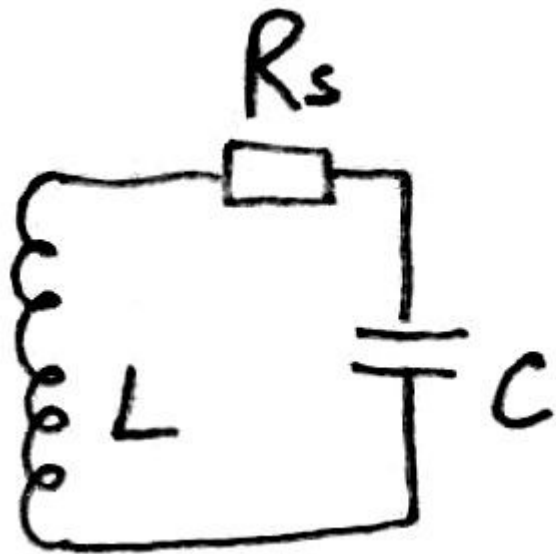
Oscilatorno kolo ima prigusene oscilacije zbog gubitaka u  $R_s$  ili  $R_p$



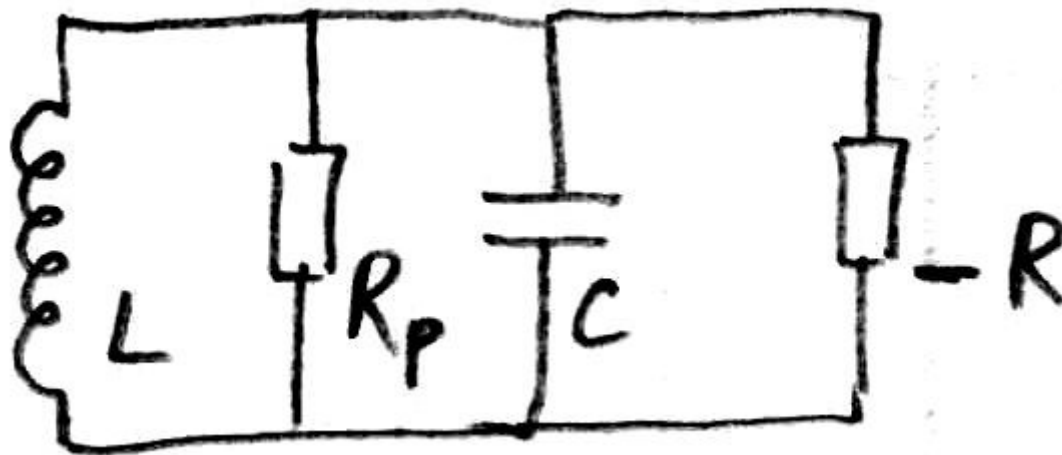
Negativna otpornost je izvor energije koji moze da nadoknadi gubitke na  $R_p$  i omoguci stalne oscilacije u kolu



Tunnel-dioda ima negativnu otpornost

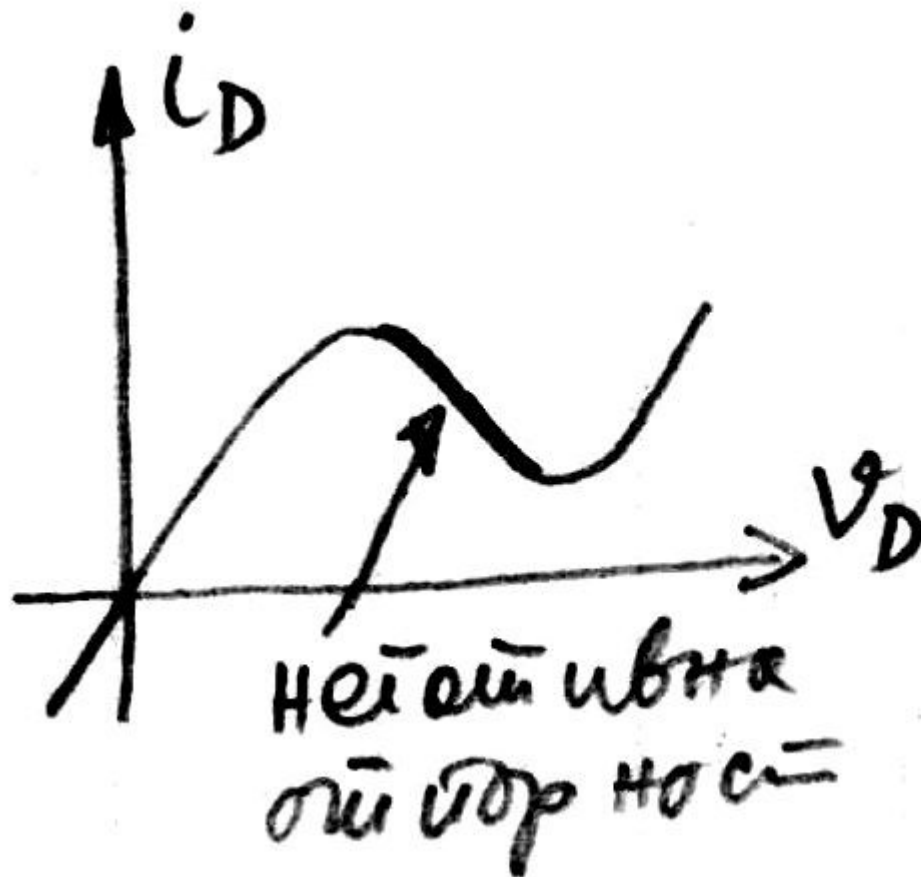

# Oscilator sa tunelskom diodom

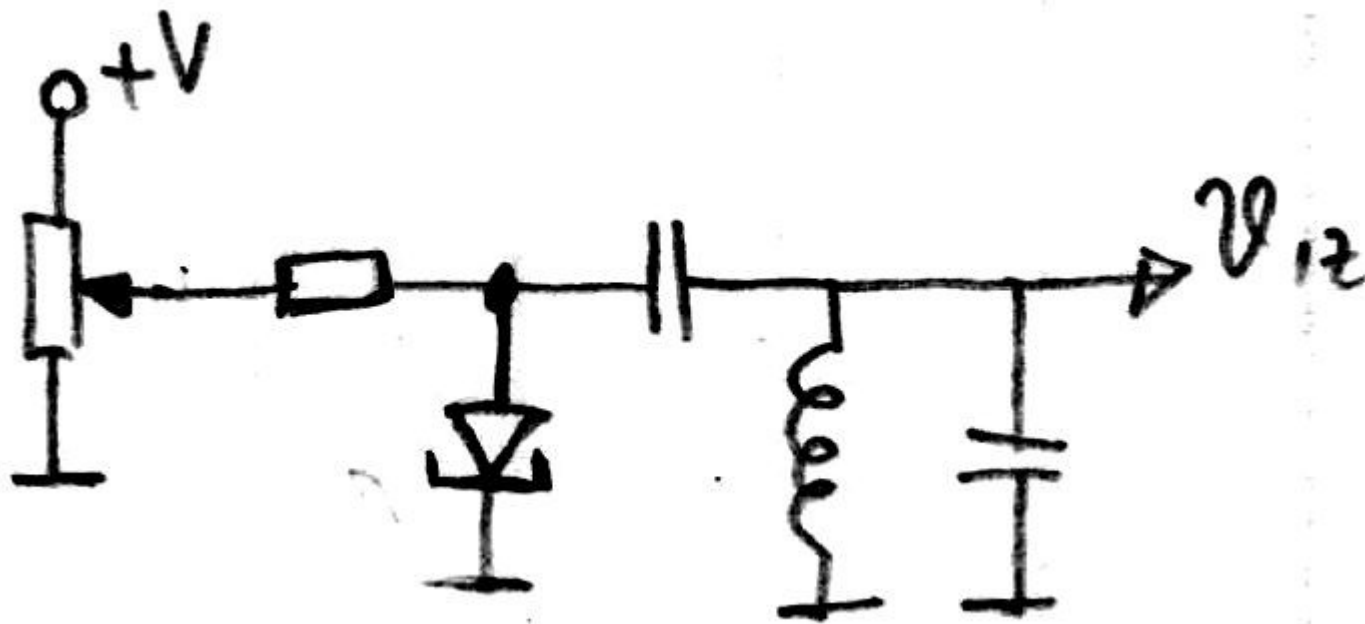

# Sema oscilatora sa tunelnom diodom

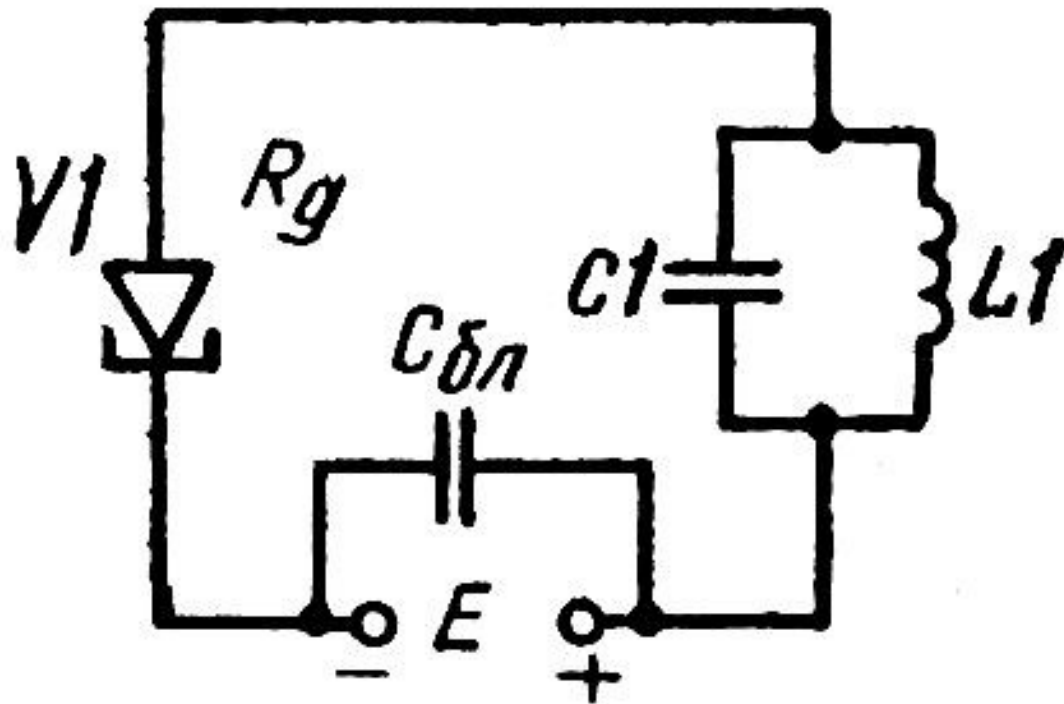


Рис. 11.43. Схема генератора на туннельном диоде.

# Појасавас са тунелном диодом

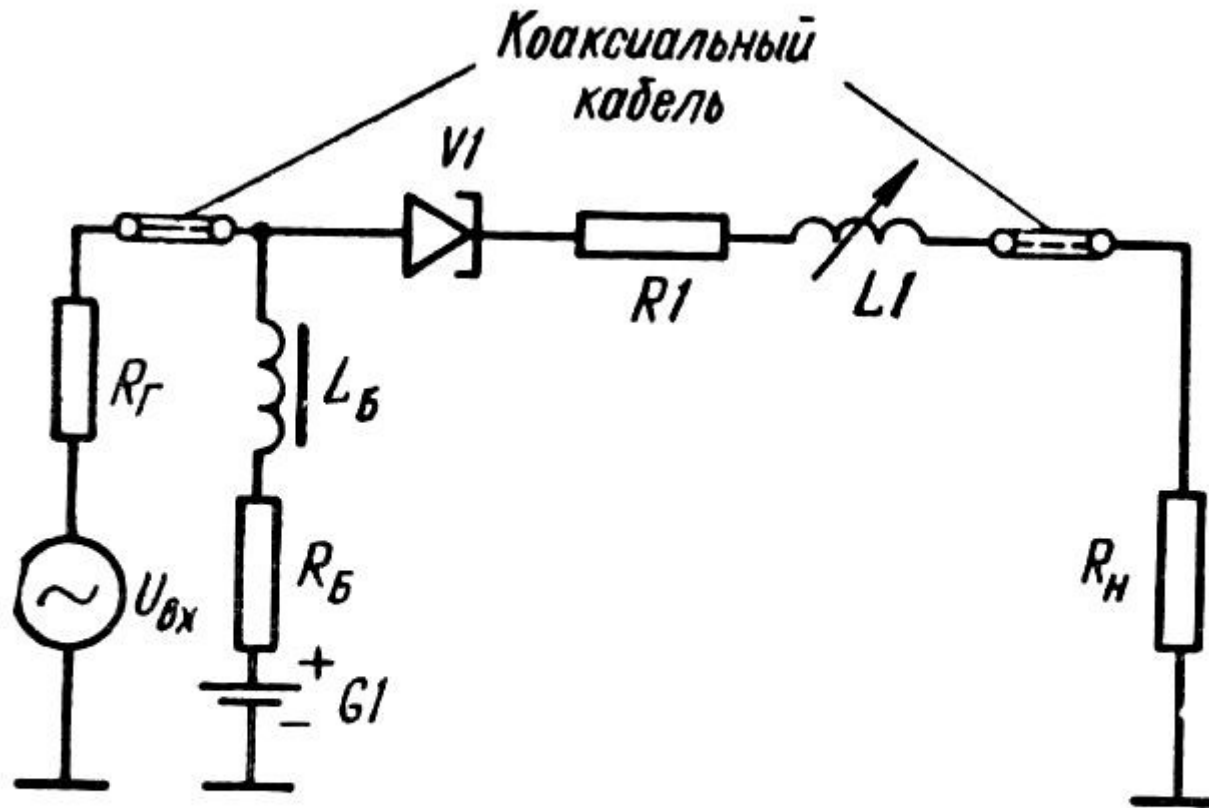
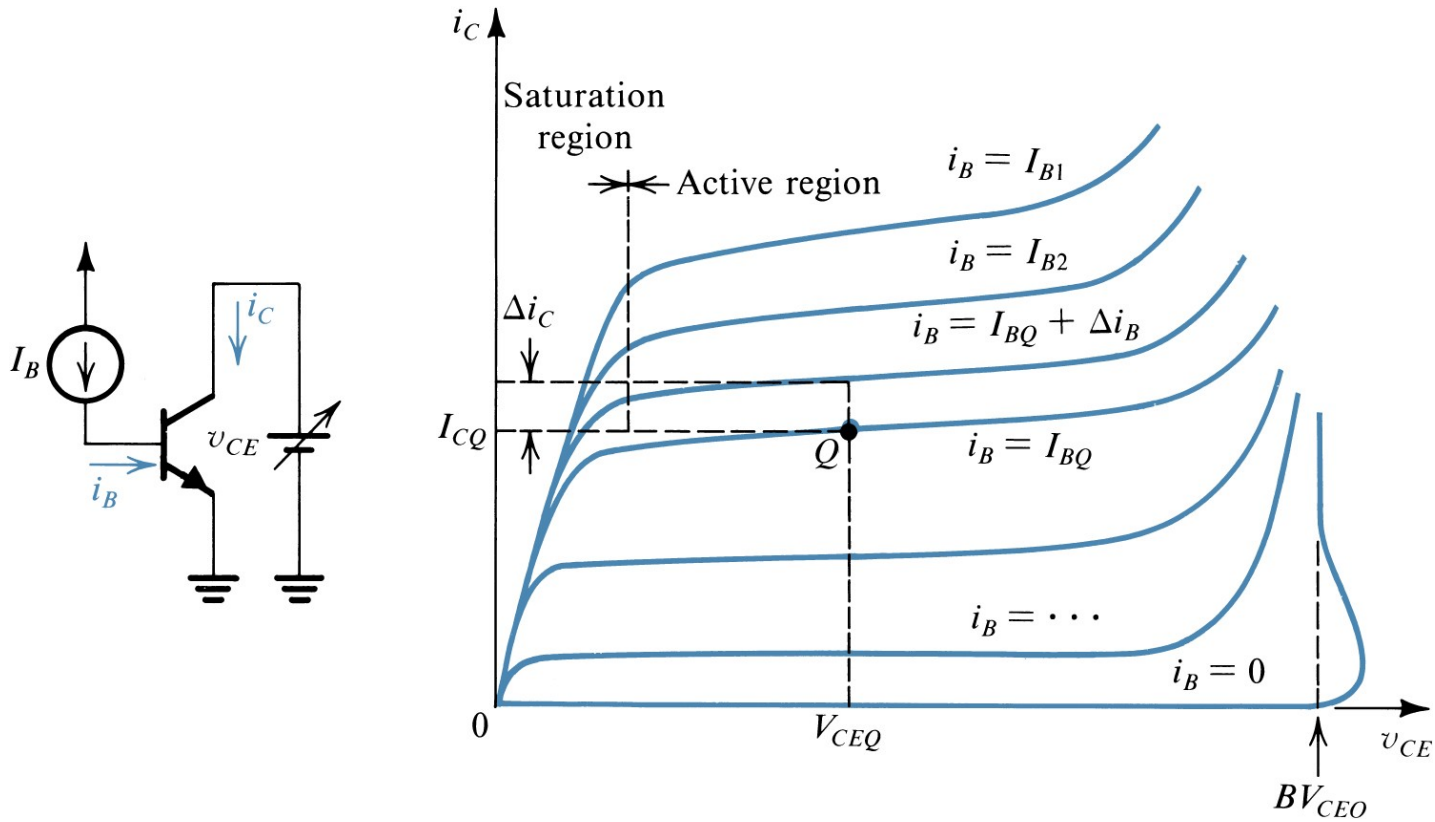


Рис. 11.42. Принципиальная схема усилителя на туннельном диоде.

Tinjalica, takodje, ima negativnu otpornost, pa se i sa njom moze napraviti oscilator

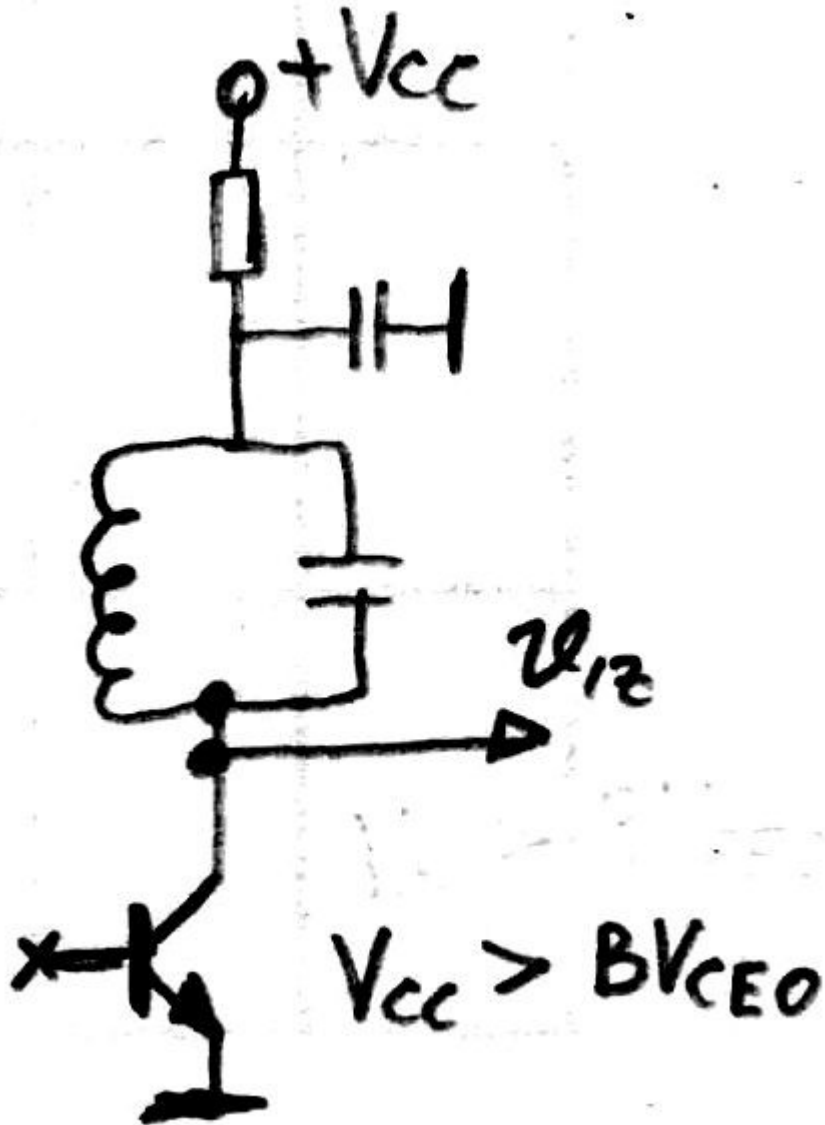







**Fig. 4.65** Common-emitter characteristics. Note that the horizontal scale is expanded around the origin to show the saturation region in some detail.

Oscilator se može napraviti i korišćenjem negativne otpornosti koju BJT ima u režimu proboja sa otvorenom bazom




# Oscilator sa Vinovim mostom

**Figure 9. Wien Bridge Oscillator**

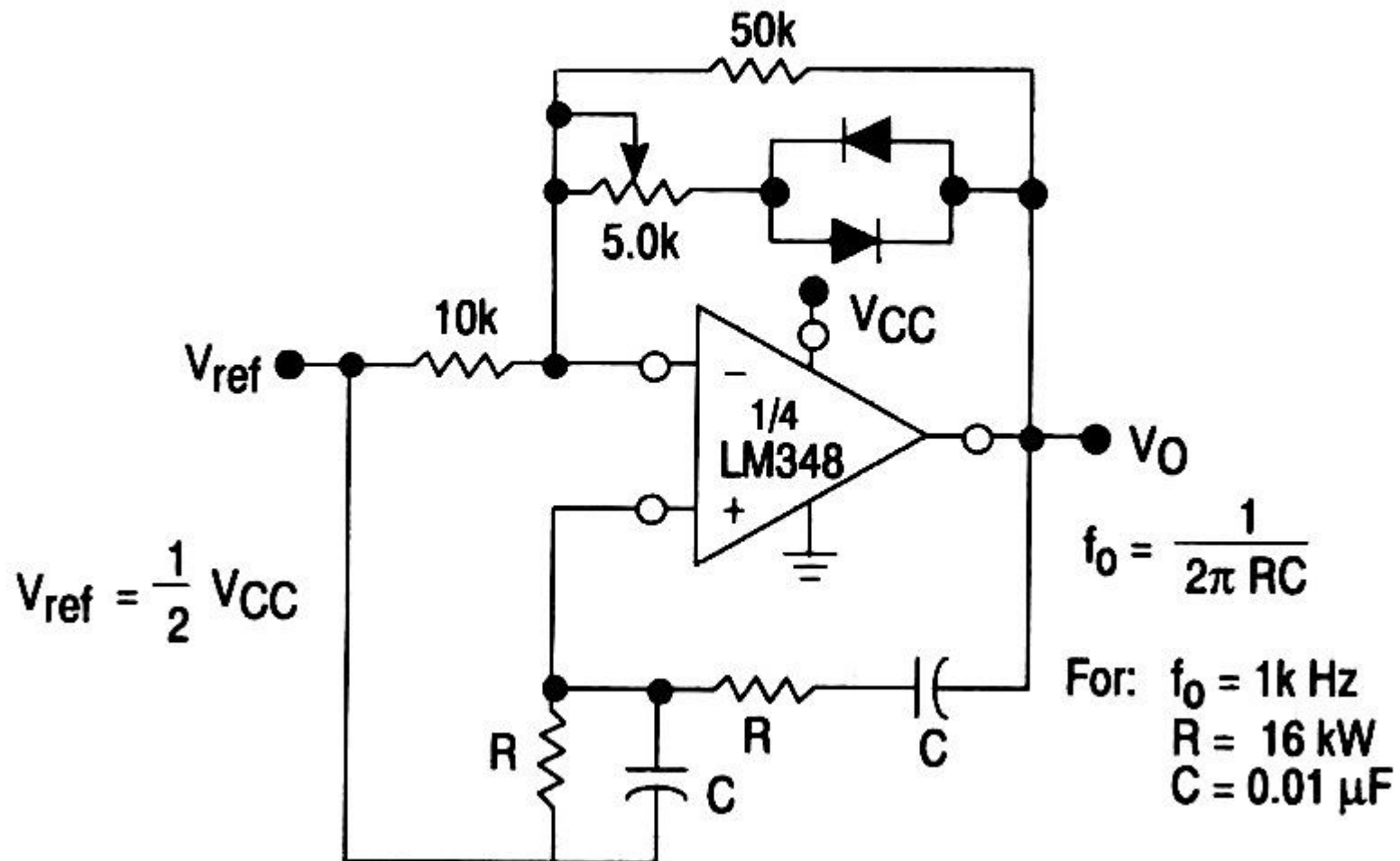


# Oscilatori 2


(regulacija  
amplitude  
oscilovanja)

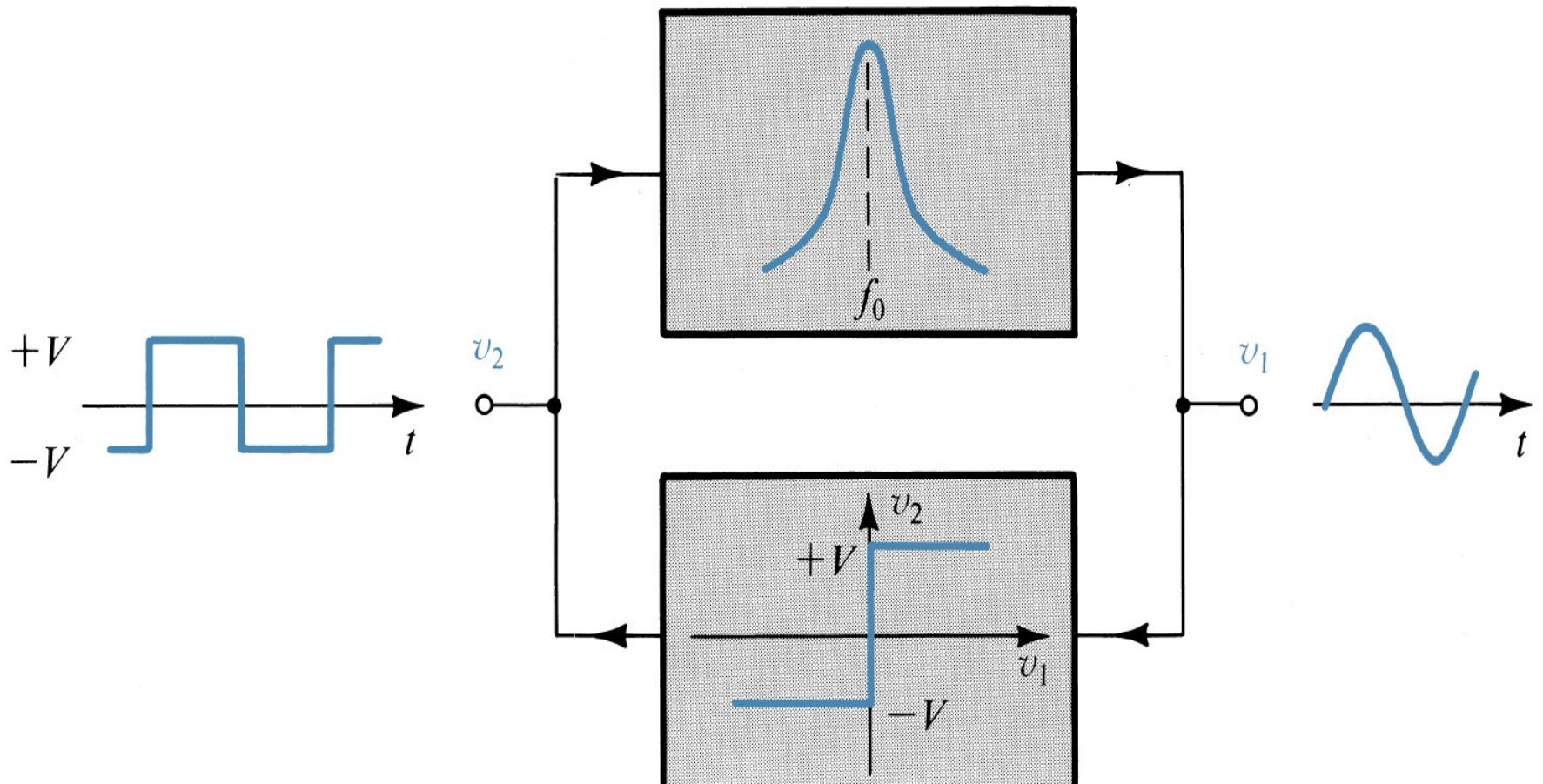

**Fig. 12.10** Block diagram of the active-filter tuned oscillator.

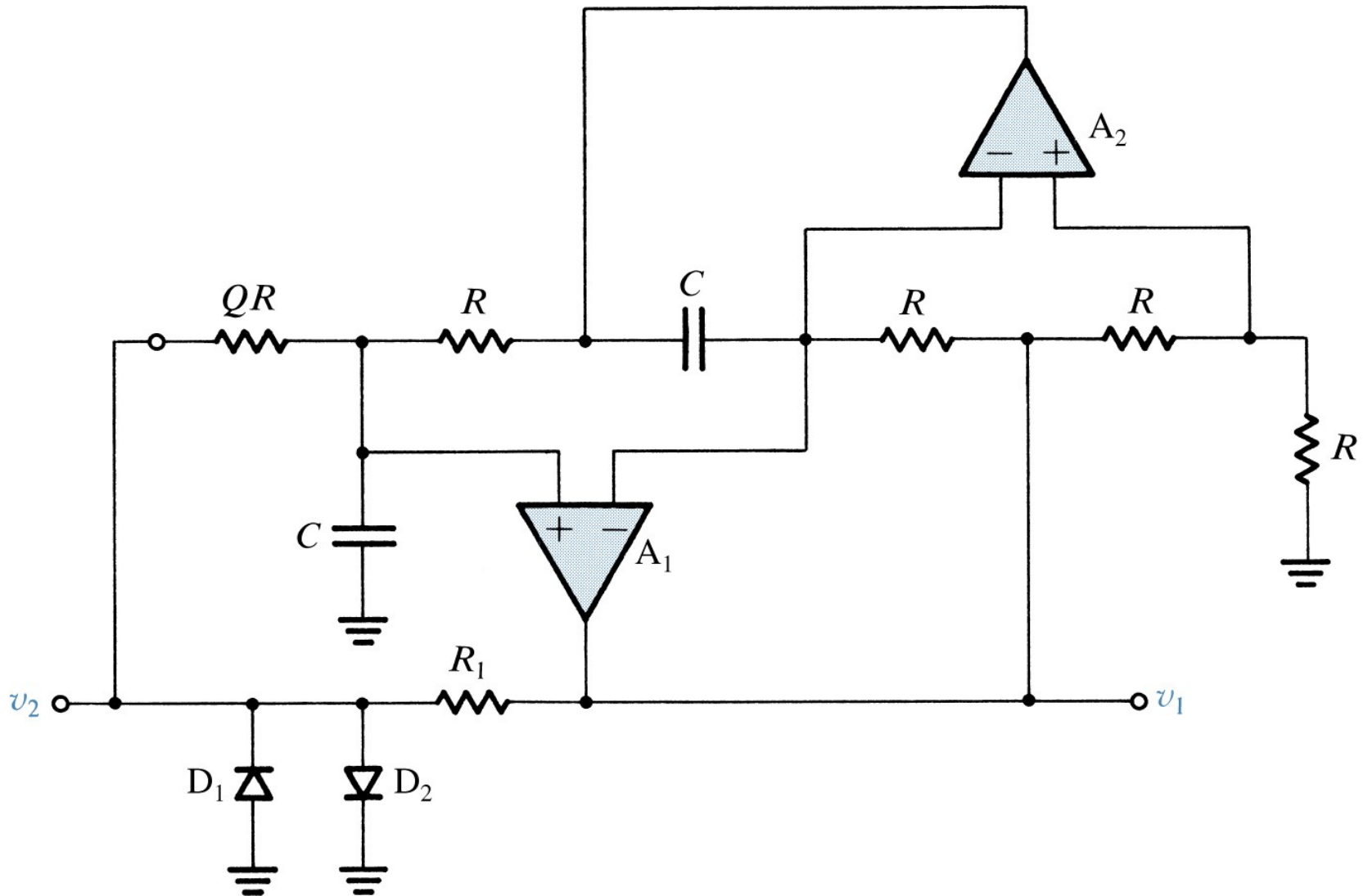


**Fig. 12.11** Practical implementation of the active-filter tuned oscillator.

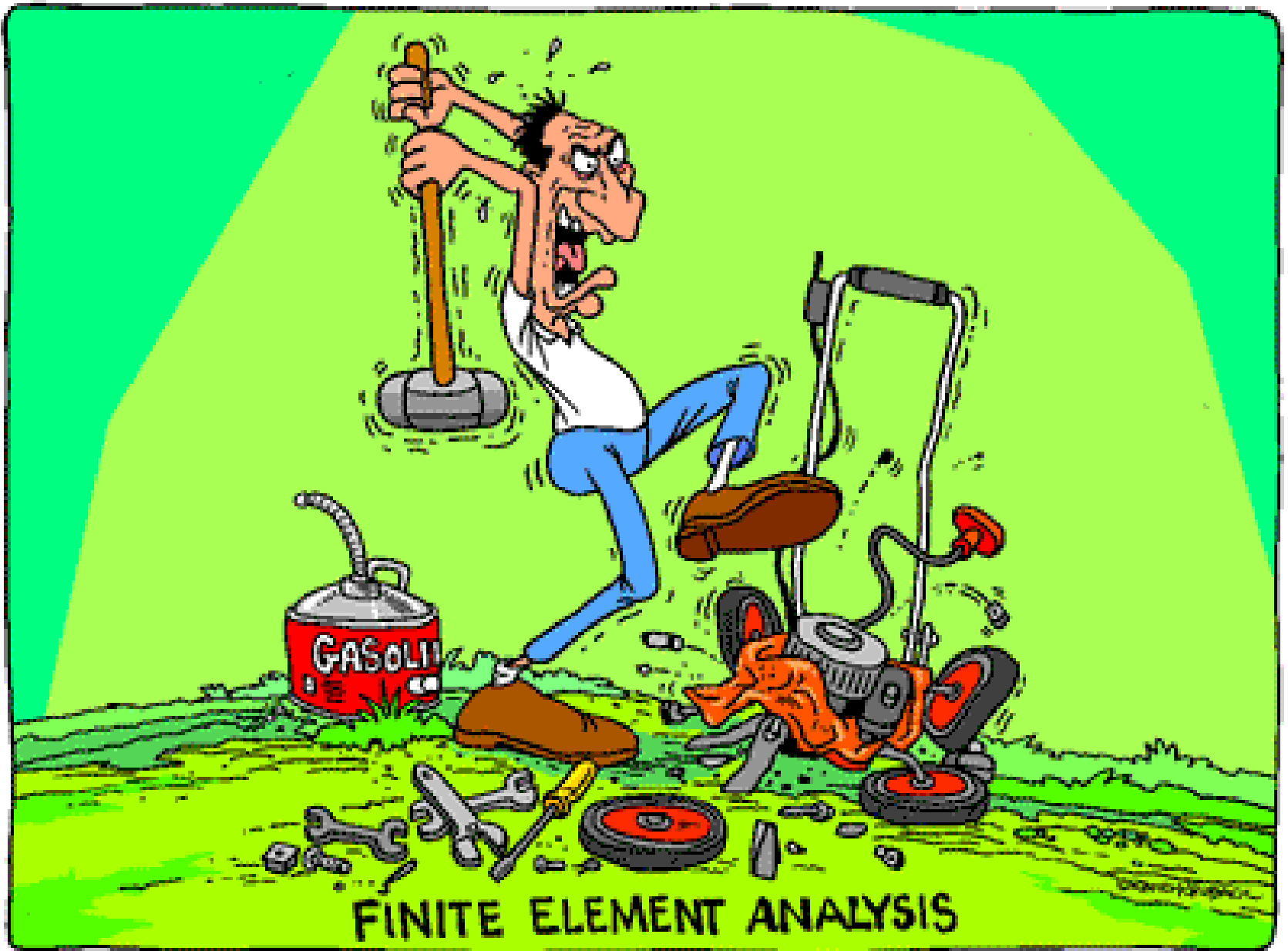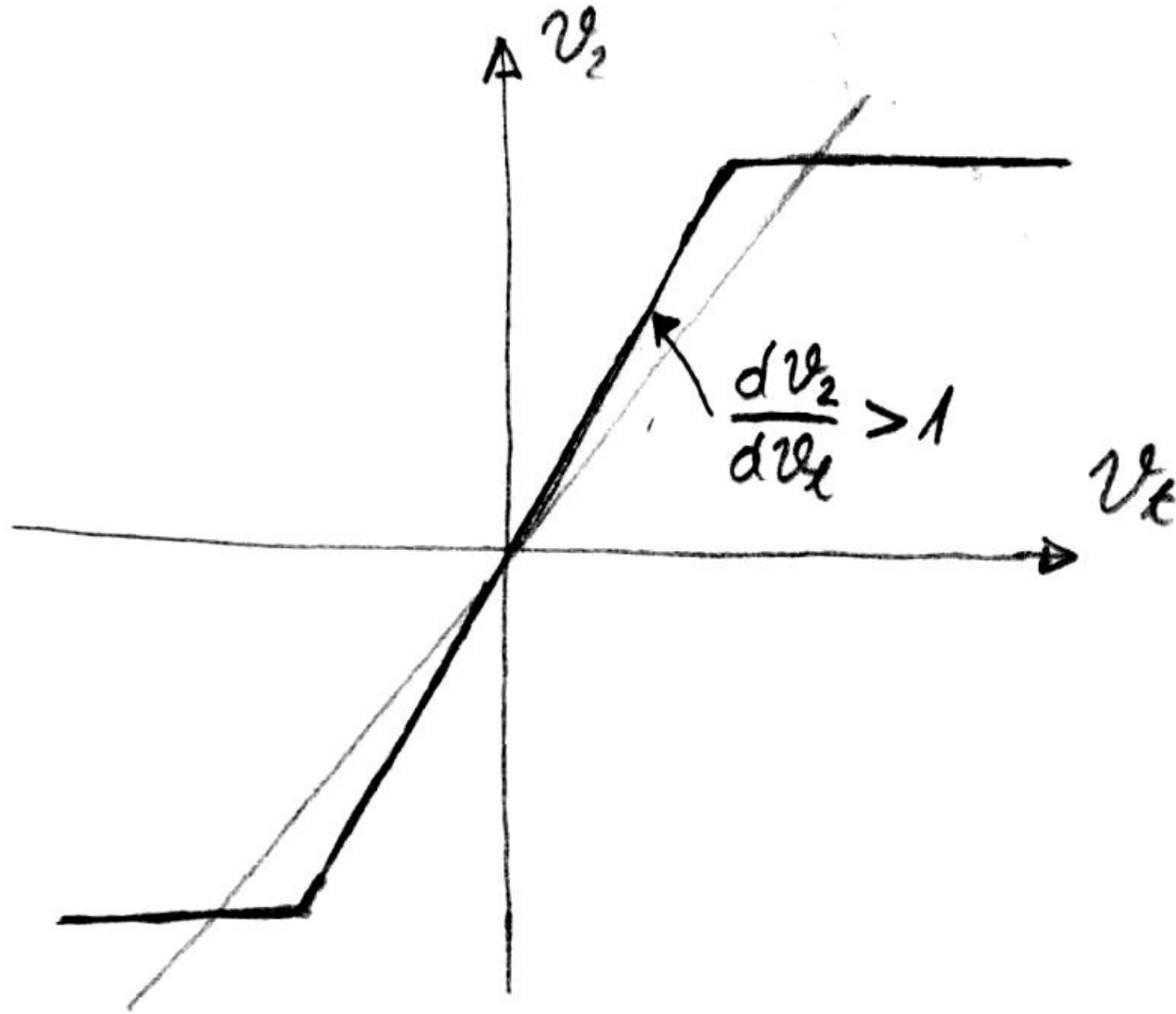

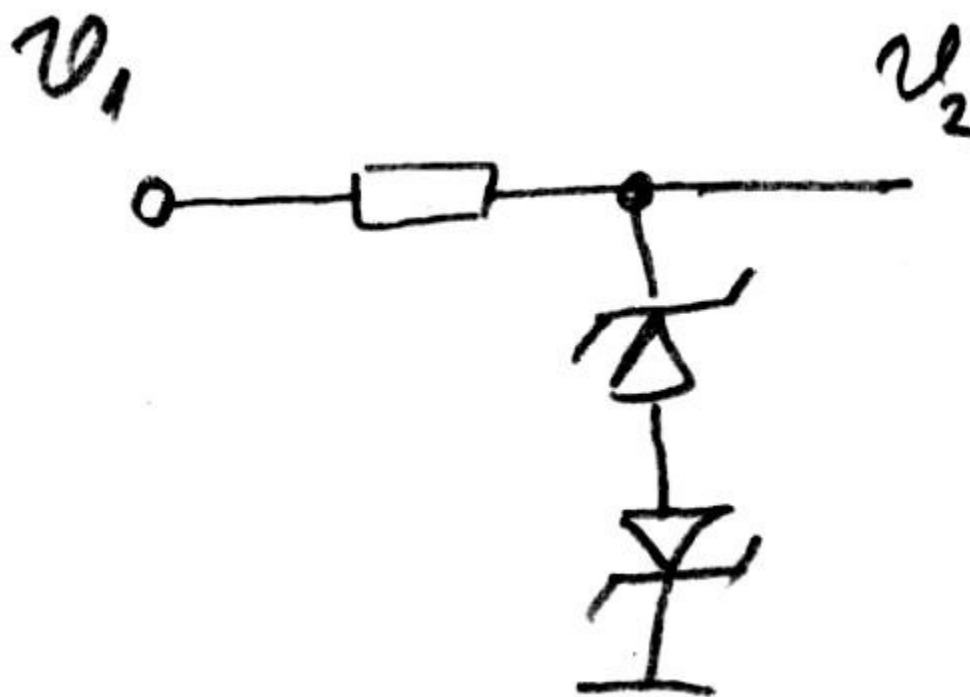
**FINITE ELEMENT ANALYSIS**

Svaki pojačavač ima nelinearnost  
tipa zasícenja







Nelinearnost se moze dodati u  
oscilator i pomocu kola sa 2  
Cenerove diode



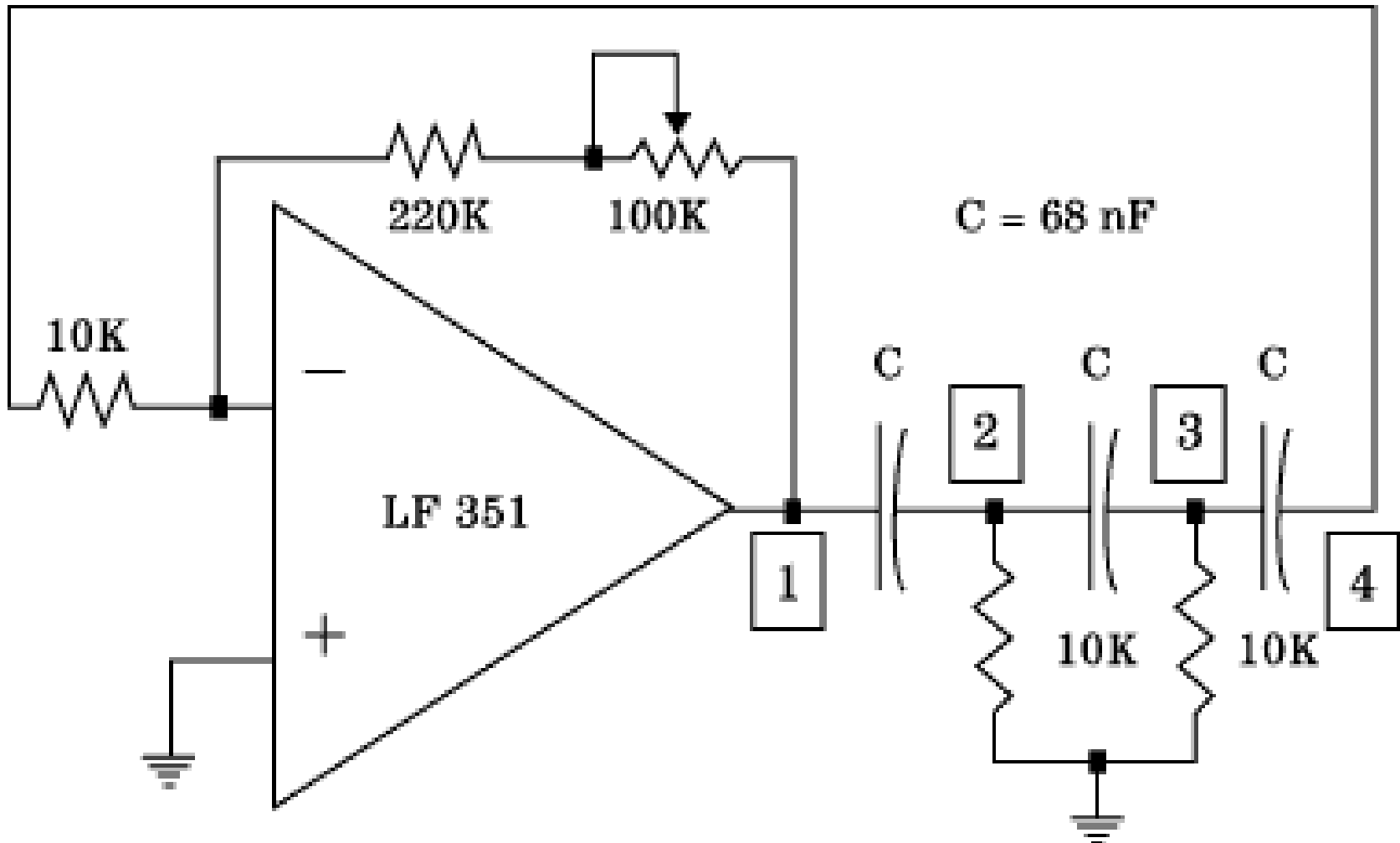RC oscilator - amplituda je  
odredjena granicama zasicenja OP





# Naponi u cvorovima 1, 2, 3 i 4

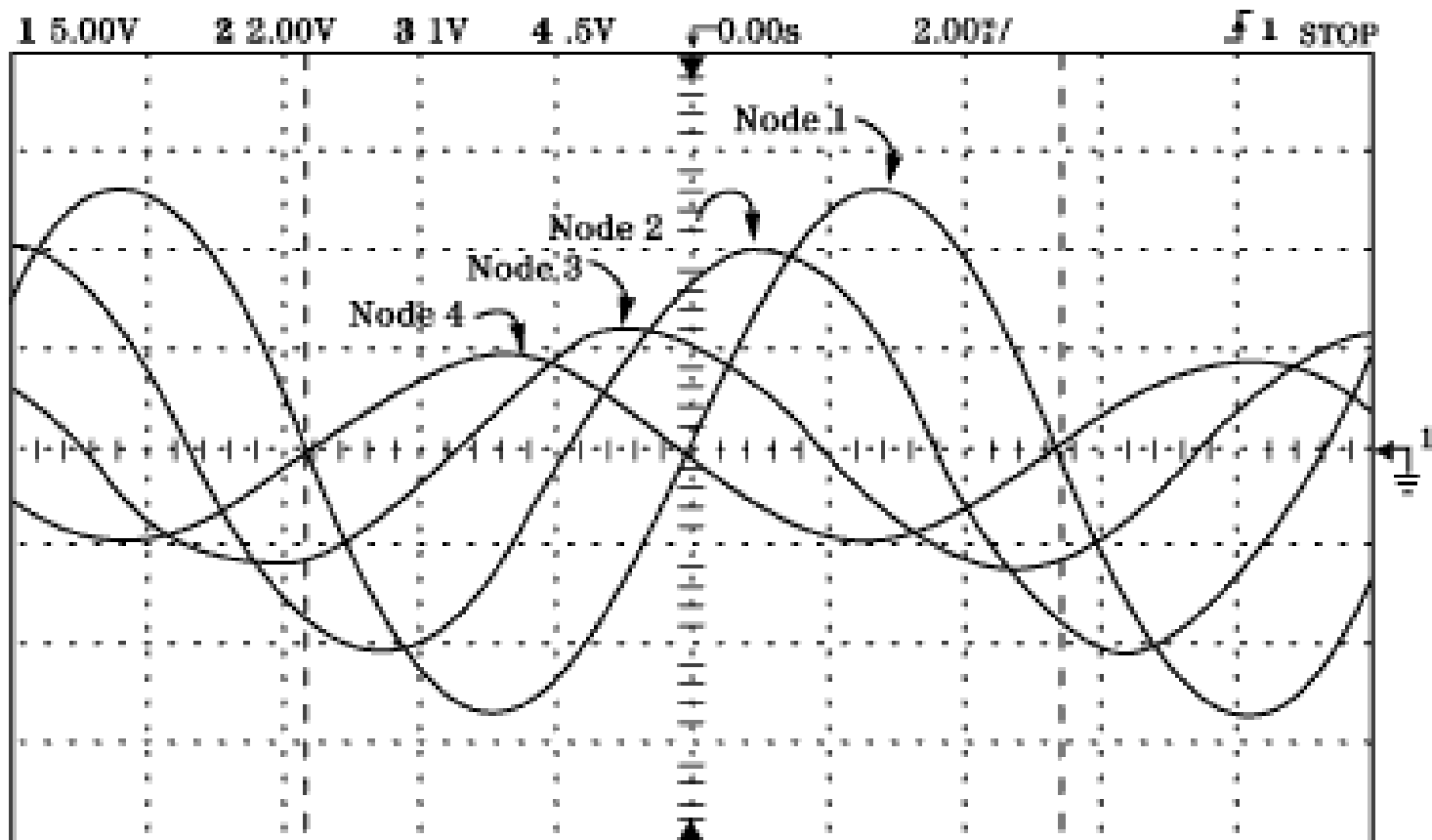


Freq(1)=91.24 Hz

**Figure 1 Voltages at Four Points in Phase-Shift Oscillator RC Network**

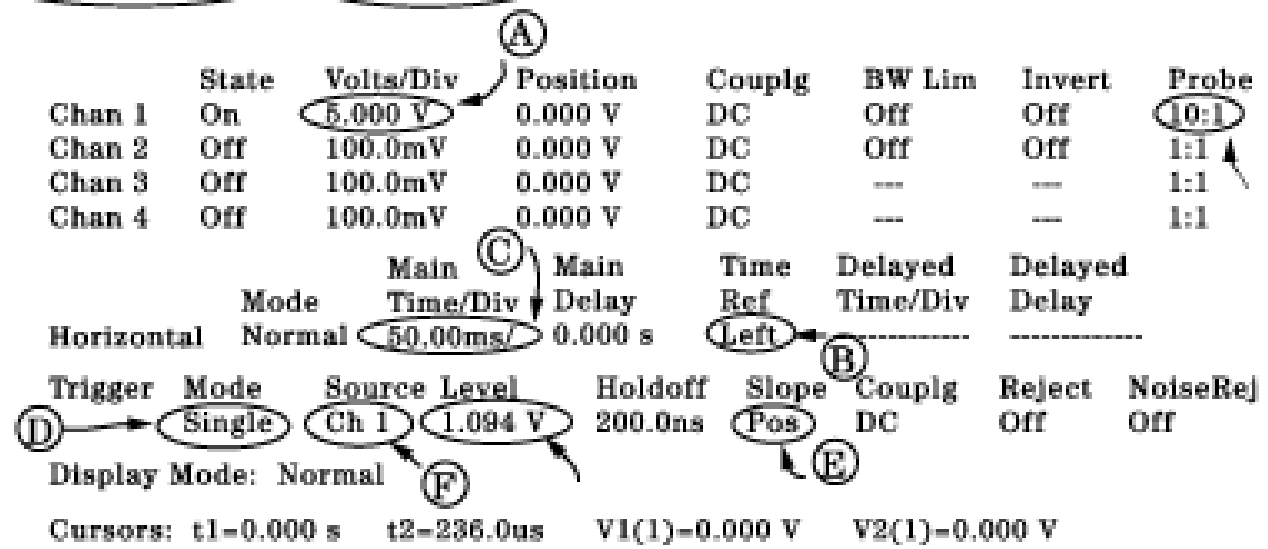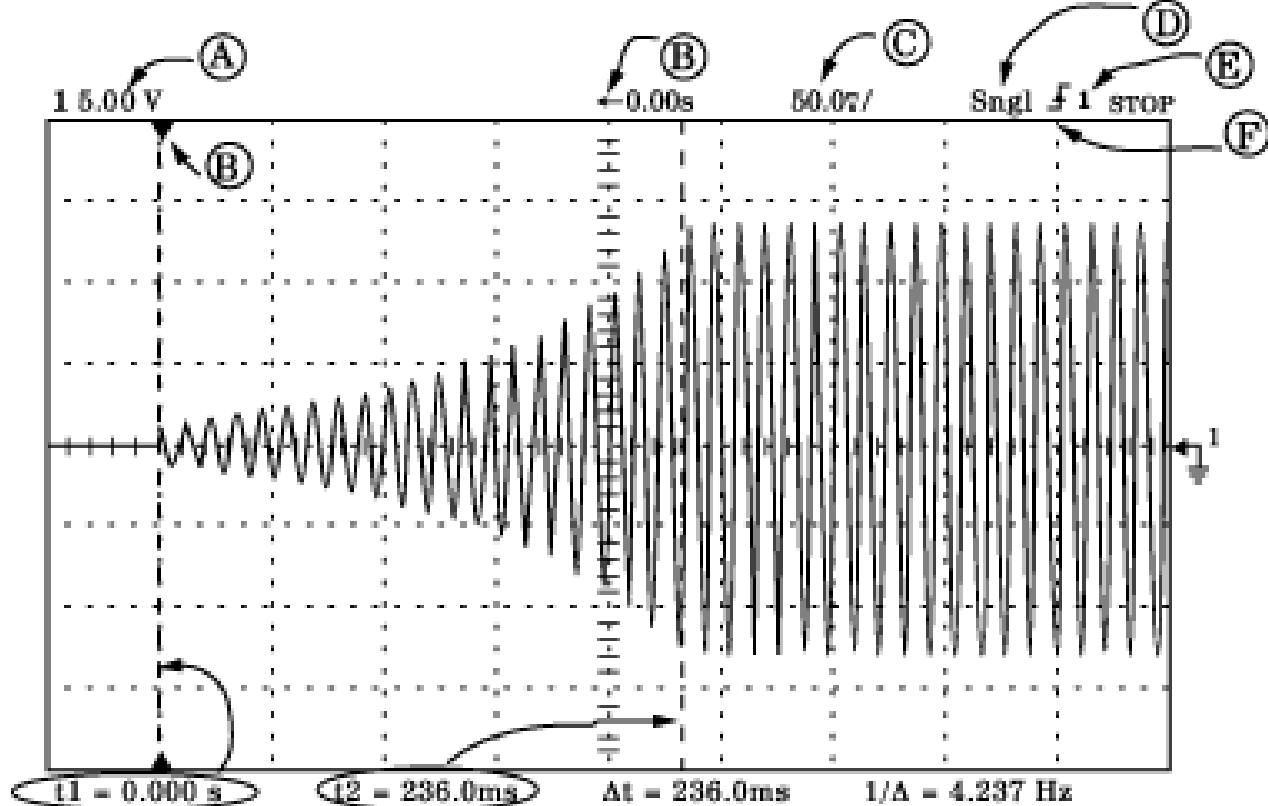


Zaletanje  
oscilacija  
RC  
oscilatora  
(sa  
pomakom  
faze)


Figure 2 - Start-up of RC Phase-Shift Oscillator

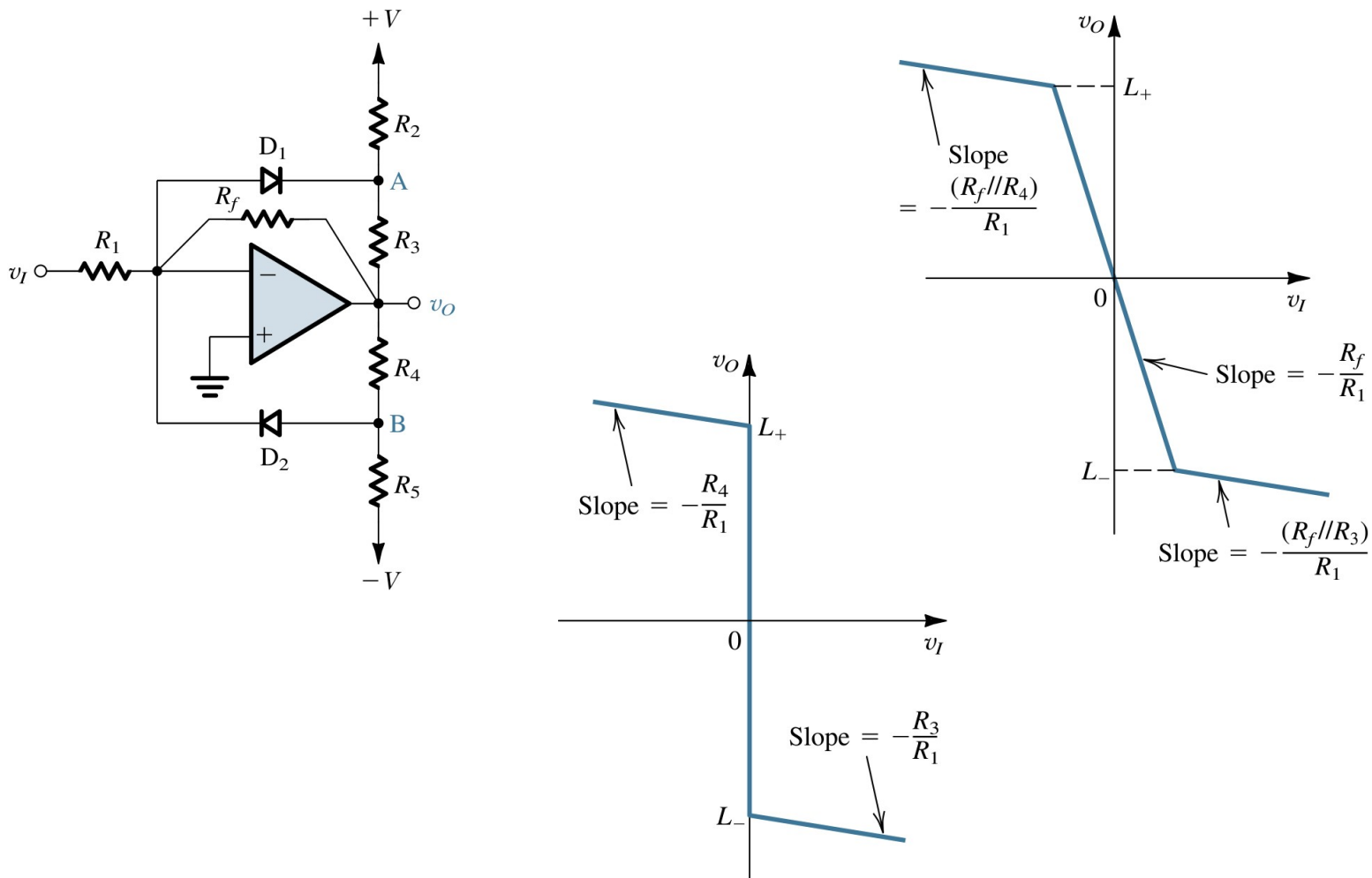


**Fig. 12.3** (a) A popular limiter circuit. (b) Transfer characteristic of the limiter circuit;  $L_-$  and  $L_+$  are given by Eqs. (12.8) and (12.9), respectively. (c) When  $R_f$  is removed the limiter turns into a comparator with characteristics shown.

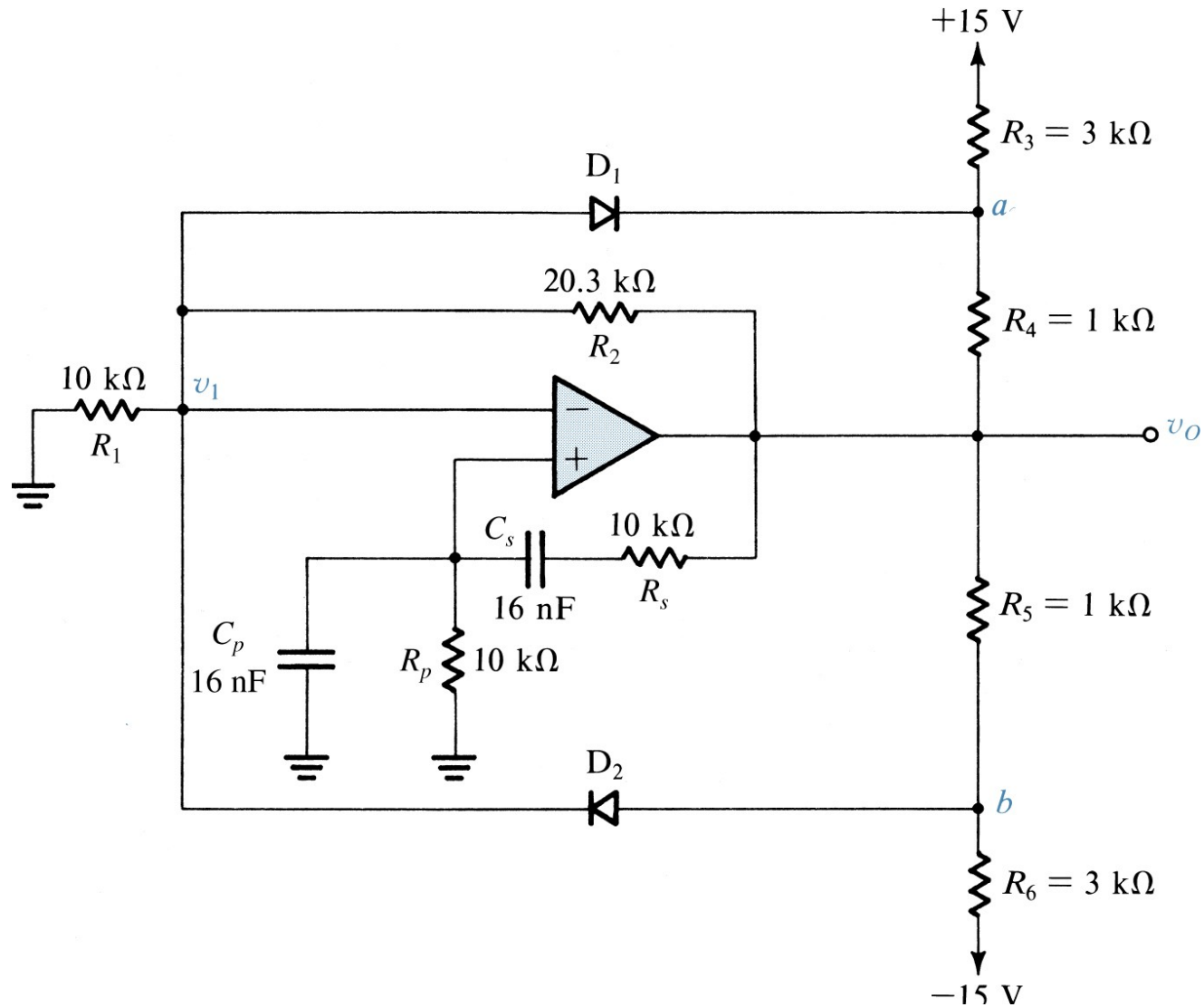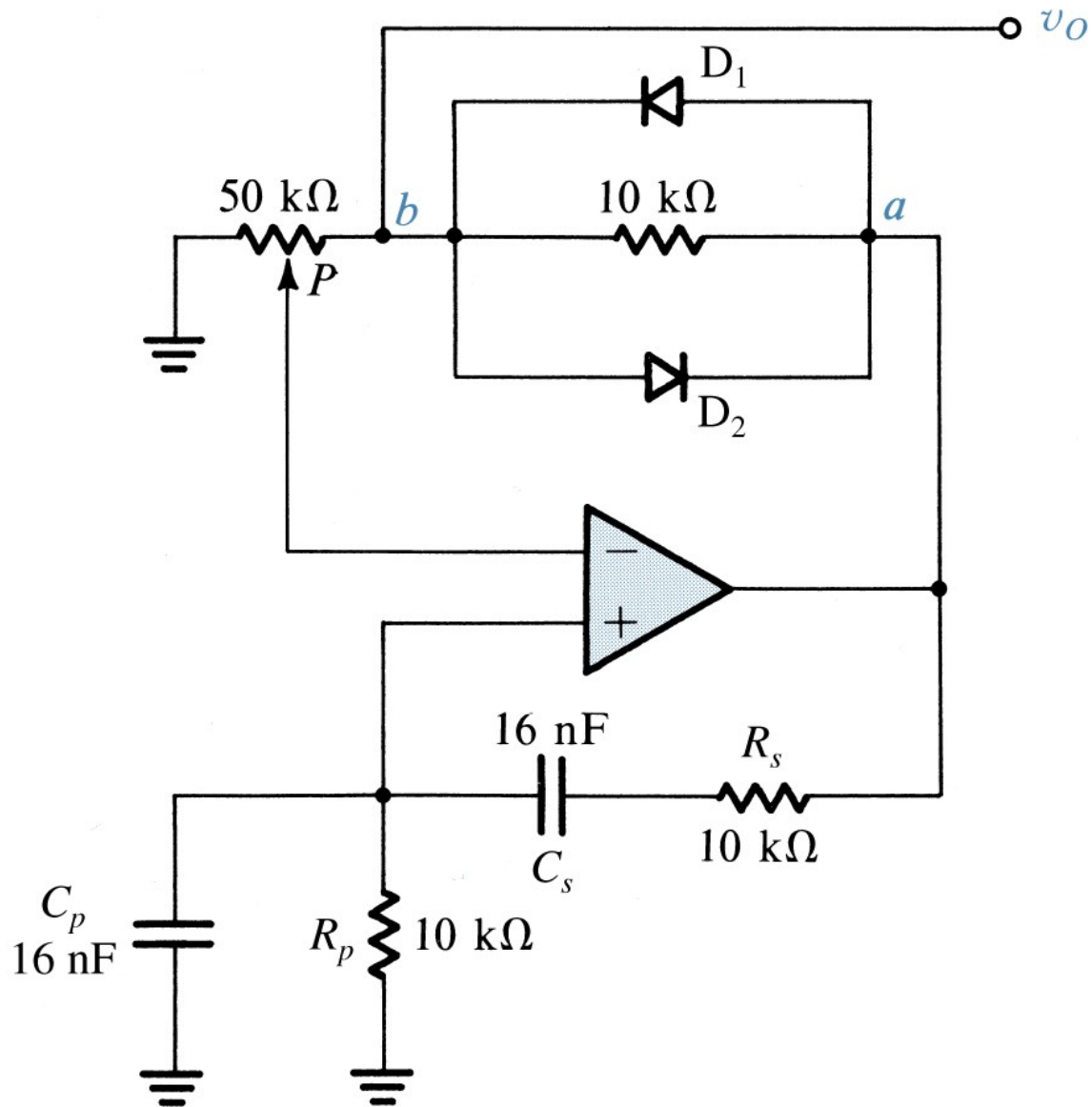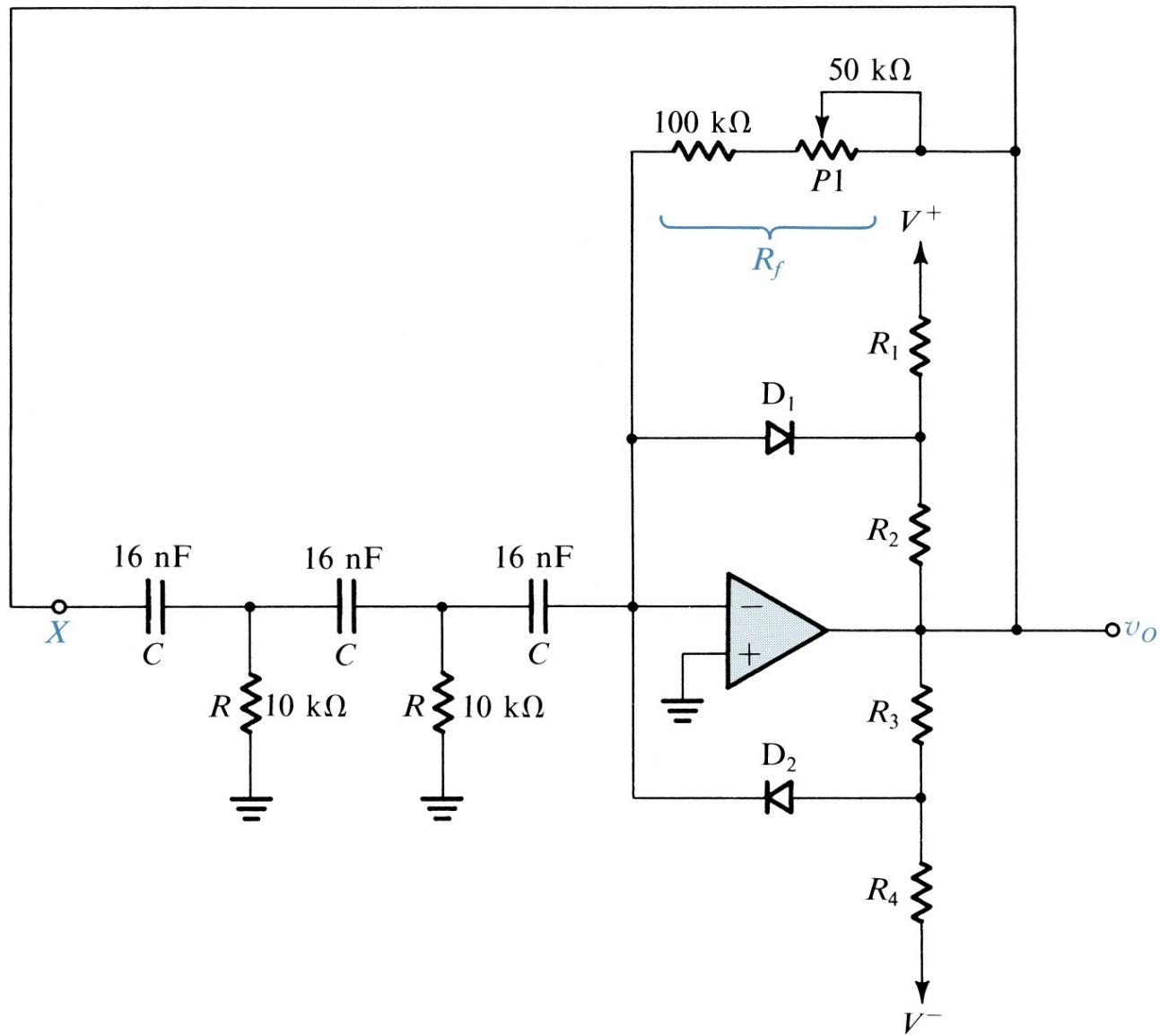

**Fig. 12.5** A Wien-bridge oscillator with a limiter used for amplitude control.

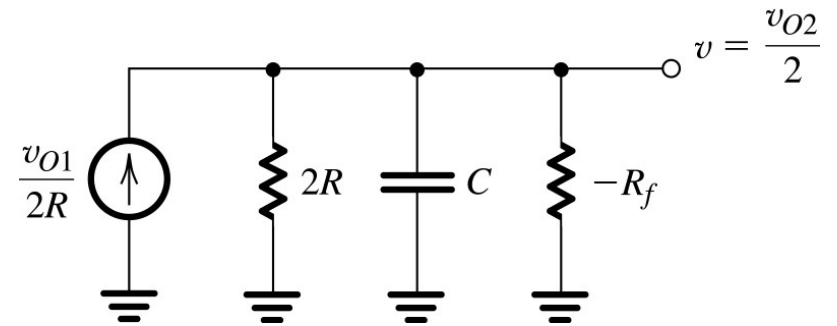
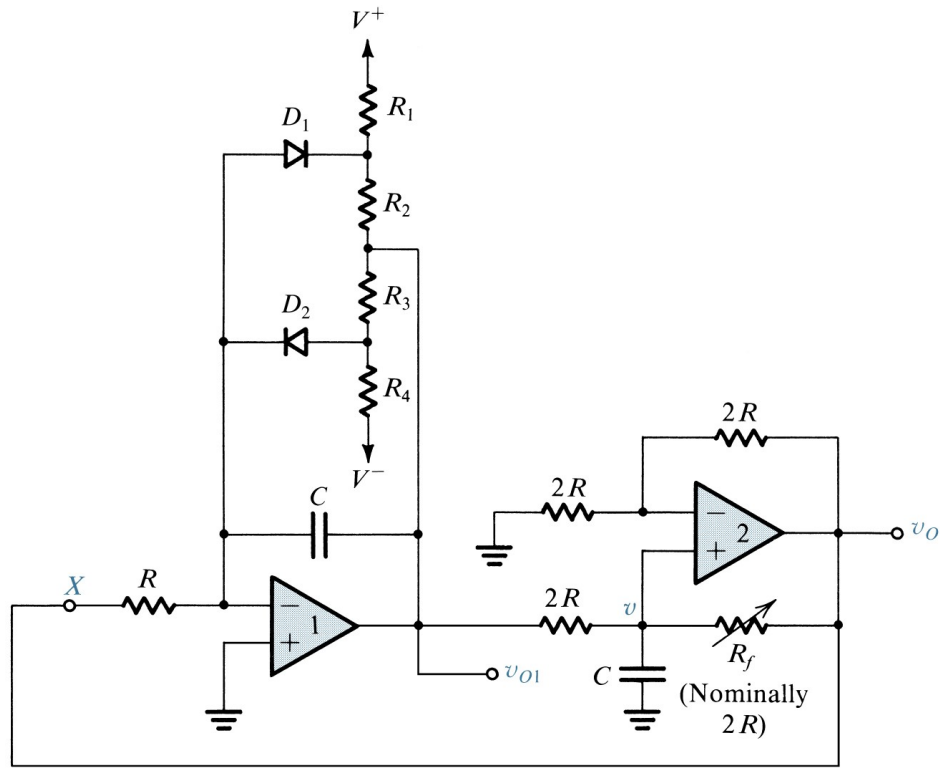


**Fig. 12.6** A Wien-bridge oscillator with an alternative method for amplitude stabilization.

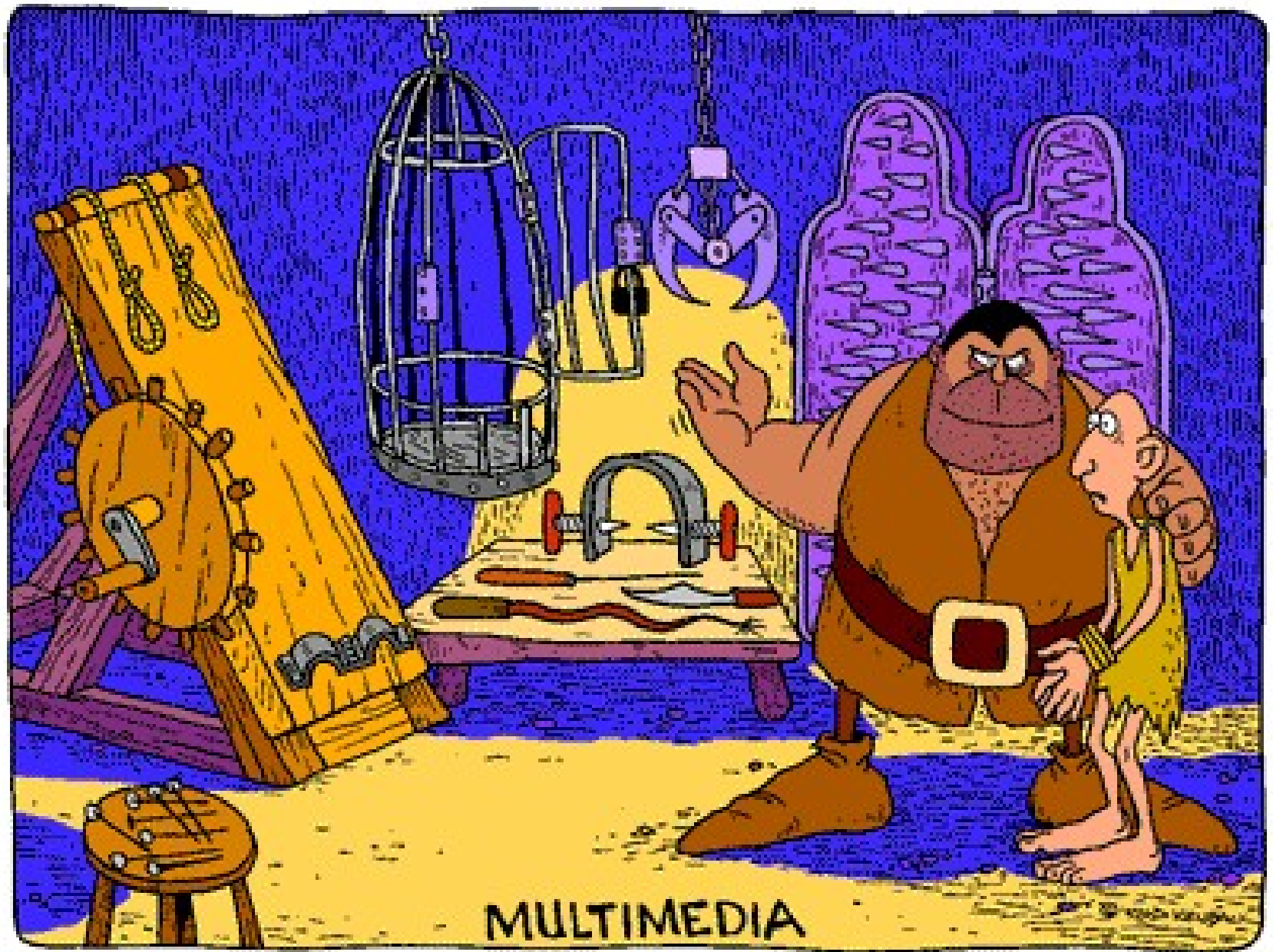


**Fig. 12.8** Practical phase-shift oscillator with a limiter for amplitude stabilization.





**Fig. 12.9** (a) A quadrature oscillator circuit. (b) equivalent circuit at the input of op amp 2.




MULTIMEDIA

*[http://www.ccsr.uiuc.edu/  
People/gmk/Projects/  
ChuaSoundMusic/](http://www.ccsr.uiuc.edu/People/gmk/Projects/ChuaSoundMusic/)*


# **Chua's Oscillator: Applications of Chaos to Sound and Music**
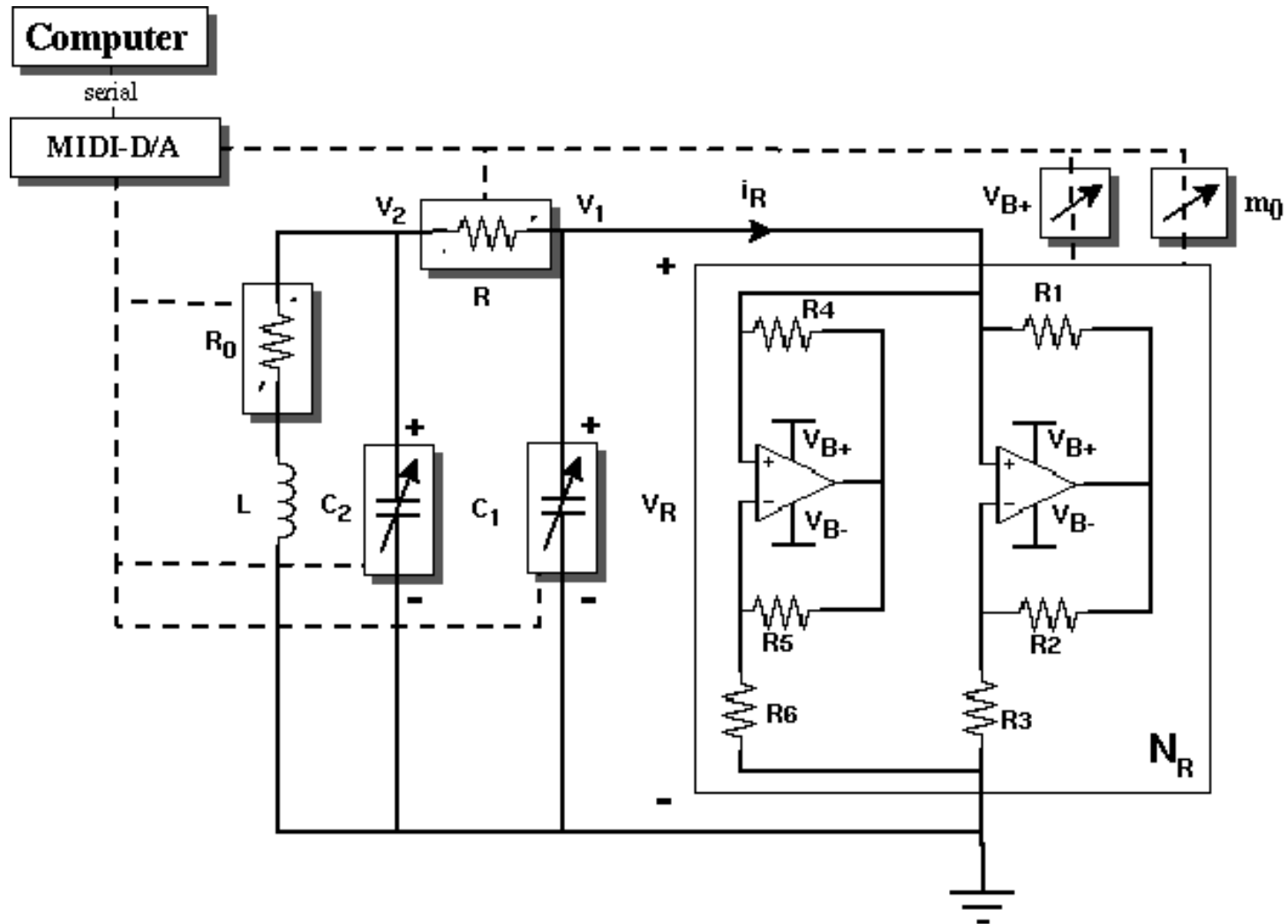
# Chua oscillator

<http://www.ccsr.uiuc.edu/People/gmk/Projects/ChuaSoundMusic/>



# Nelinearna otpornost NR

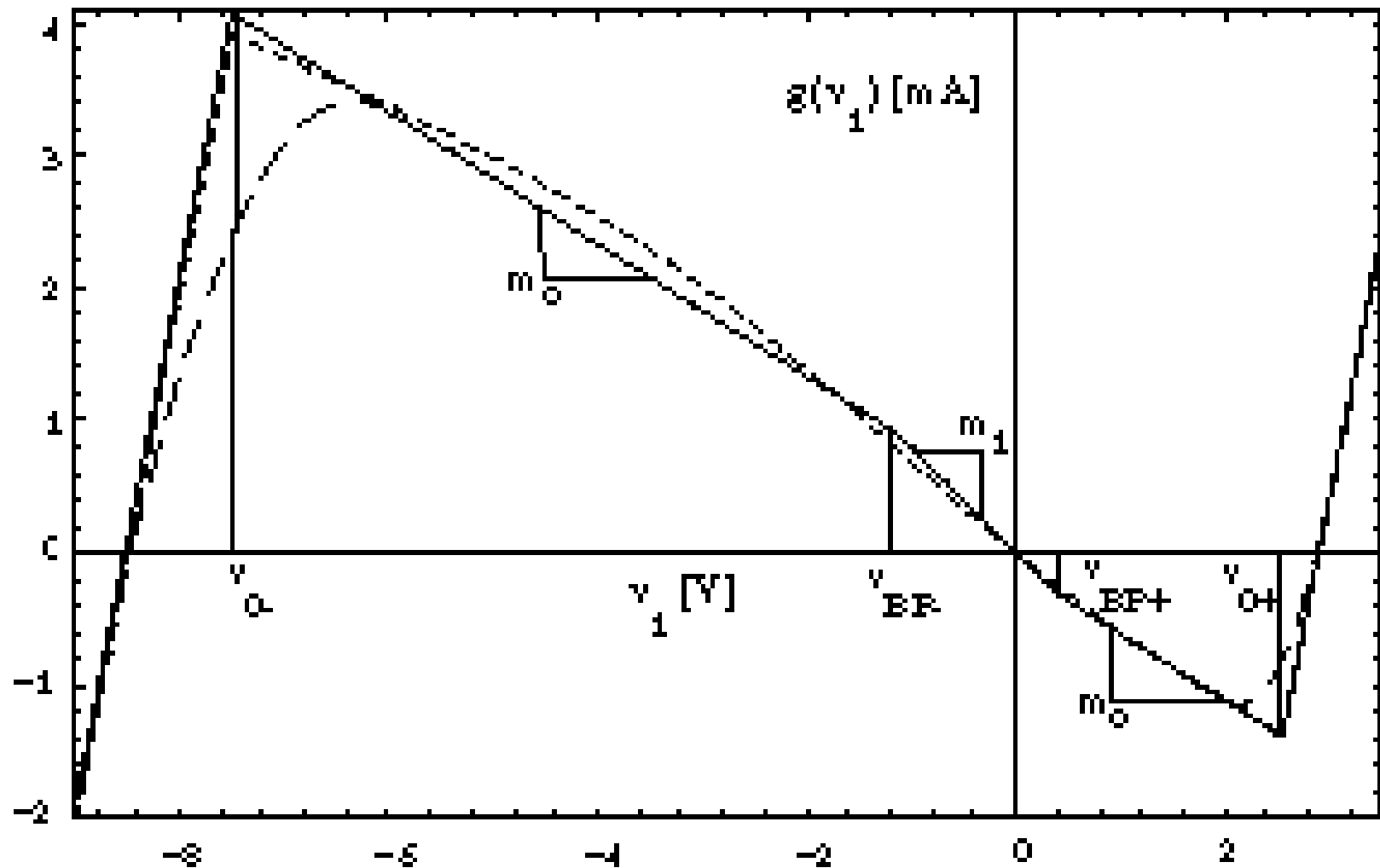

# RC oscillatori


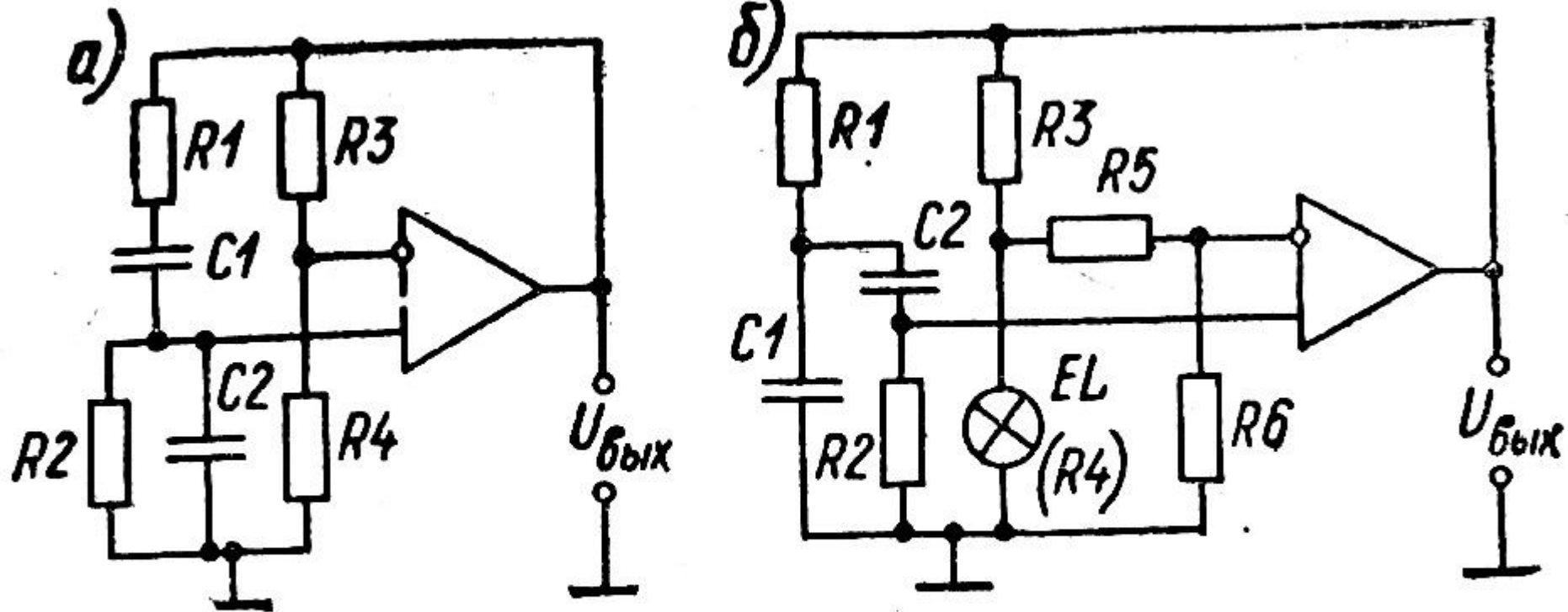



Рис. 3.10. Схемы гармонических RC-генераторов

# RC oscillators sa Nortonovim OP

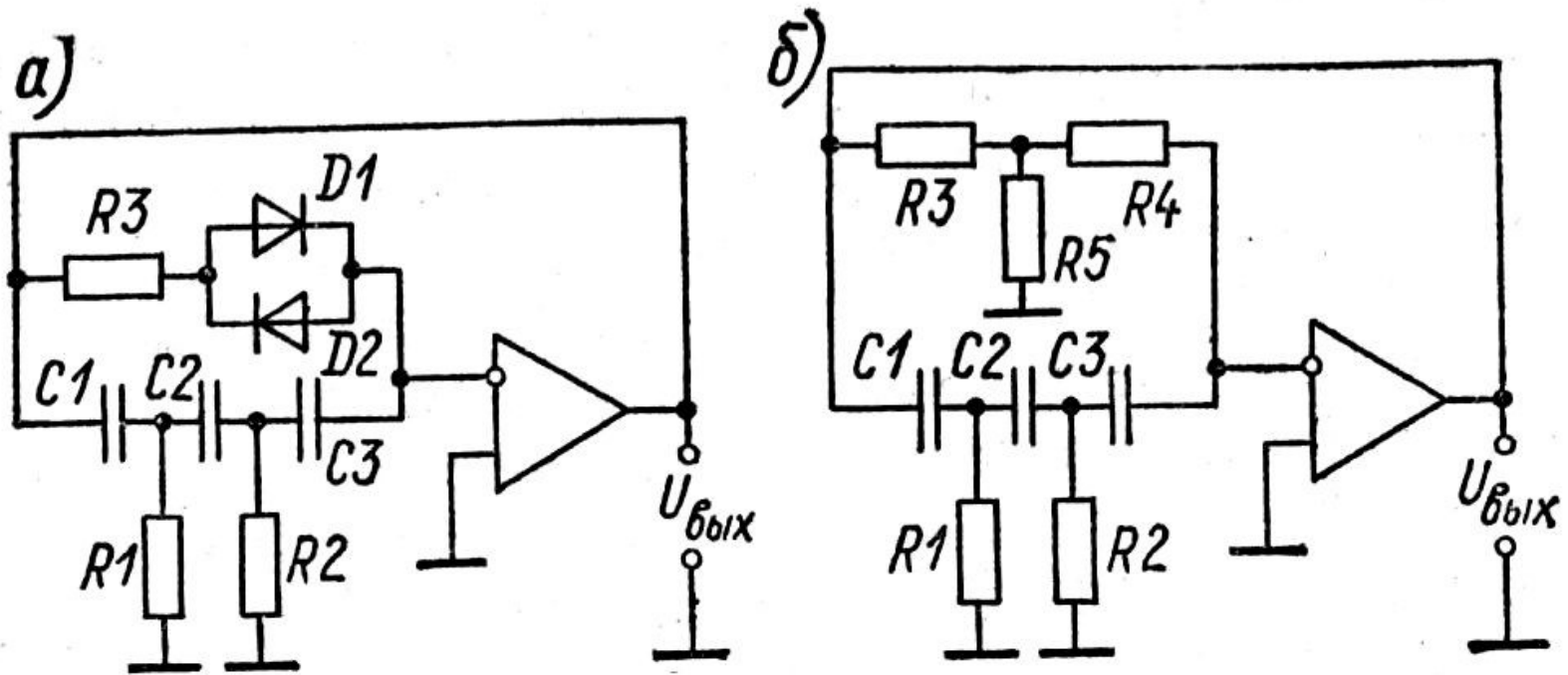

**Рис. 3.11.** Схемы RC-генераторов с потенциально-токовыми избирательными цепями

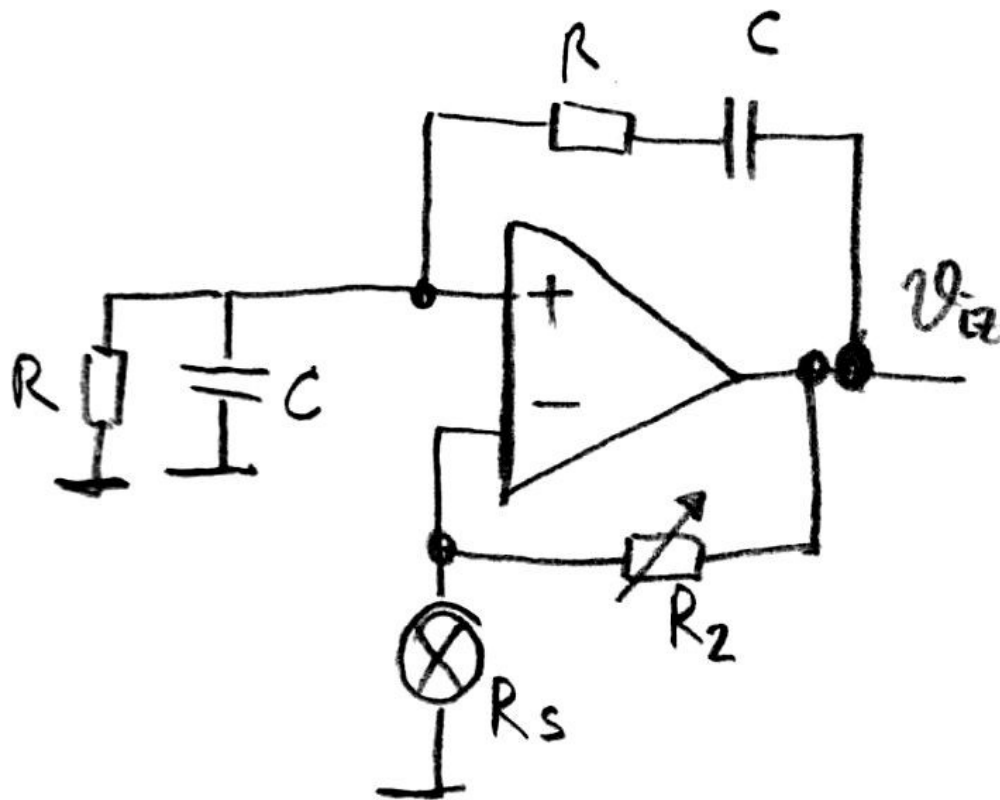
# Regulacija amplitude oscilacija pomocu termozavisnog otpora $R_s$



$V_m \uparrow, I_s \uparrow, P_s \uparrow,$   
 $T_s \uparrow, R_s \uparrow, A_\beta \downarrow,$   
 $V_m \downarrow$



# Automatska regulacija amplitude


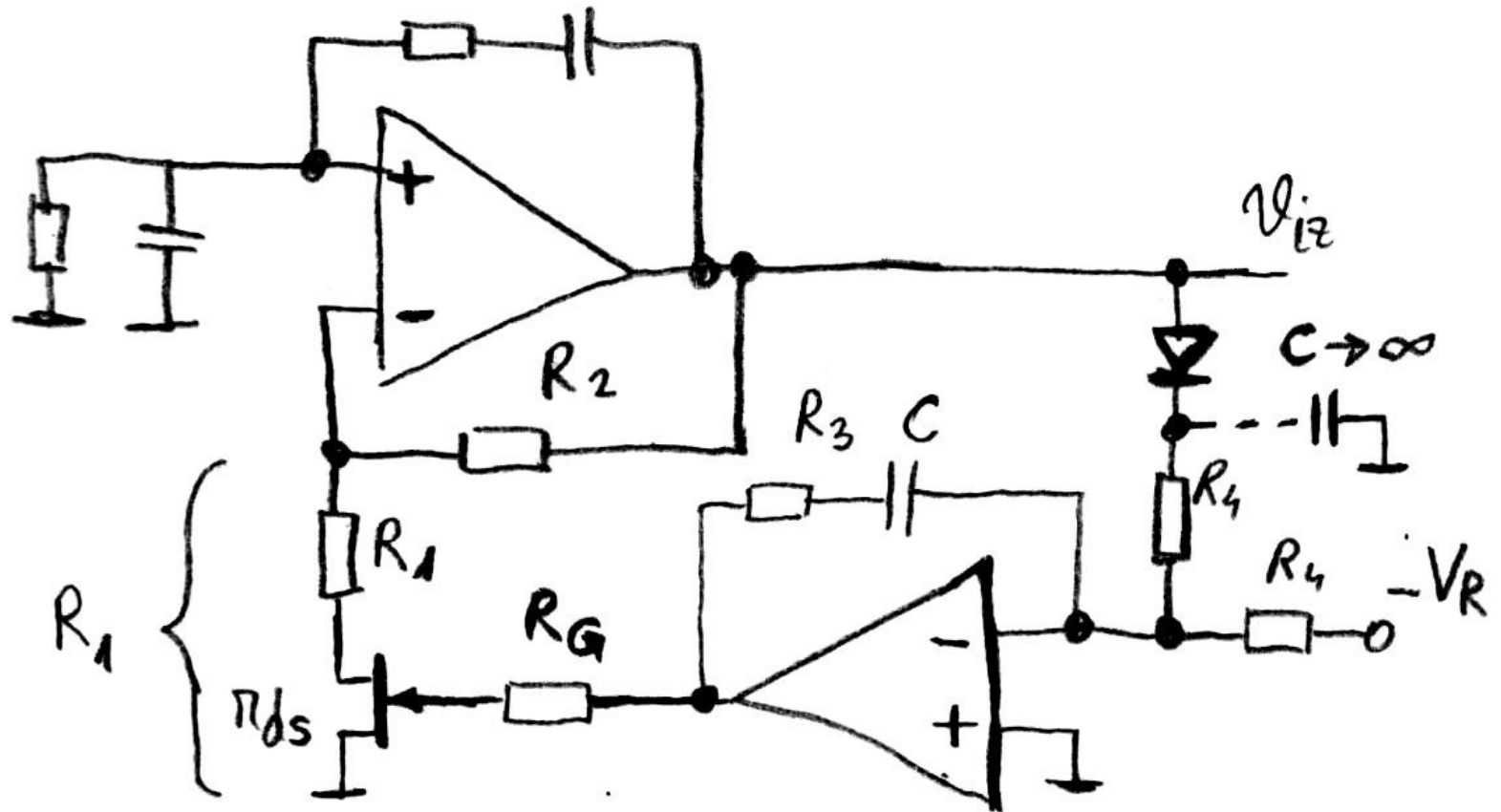


$V_m \uparrow, v^- \uparrow, v_G \downarrow, r_{ds} \uparrow, A_{\beta} \downarrow, V_m \downarrow$




WHITE NOISE

# Oscilatori u 3 tacke (BCE ili GDS)

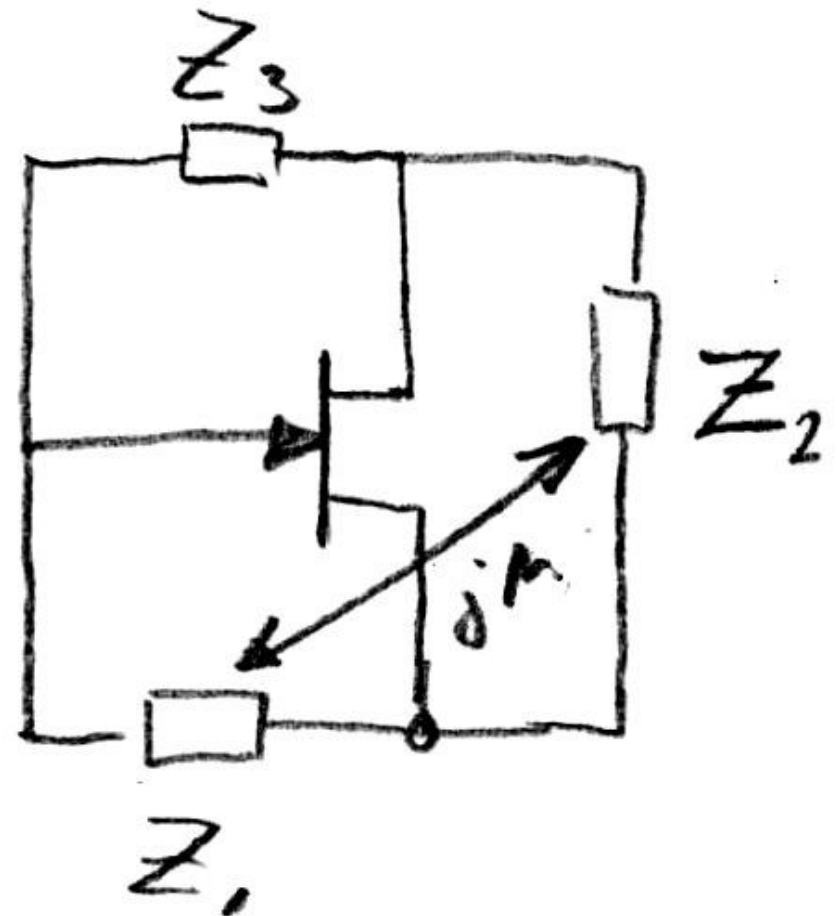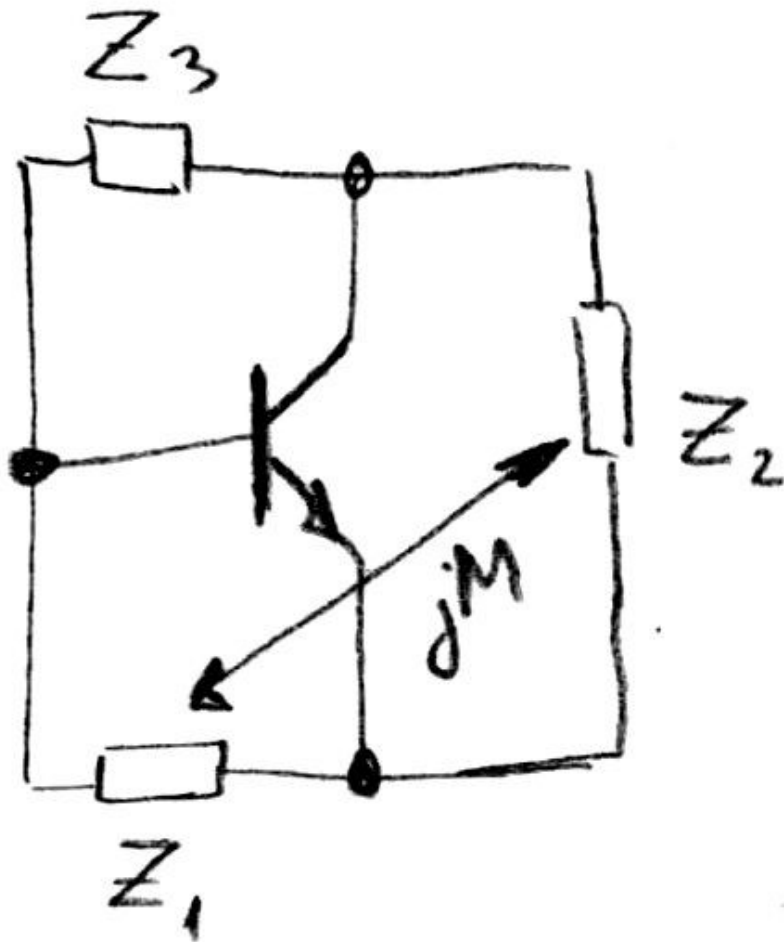
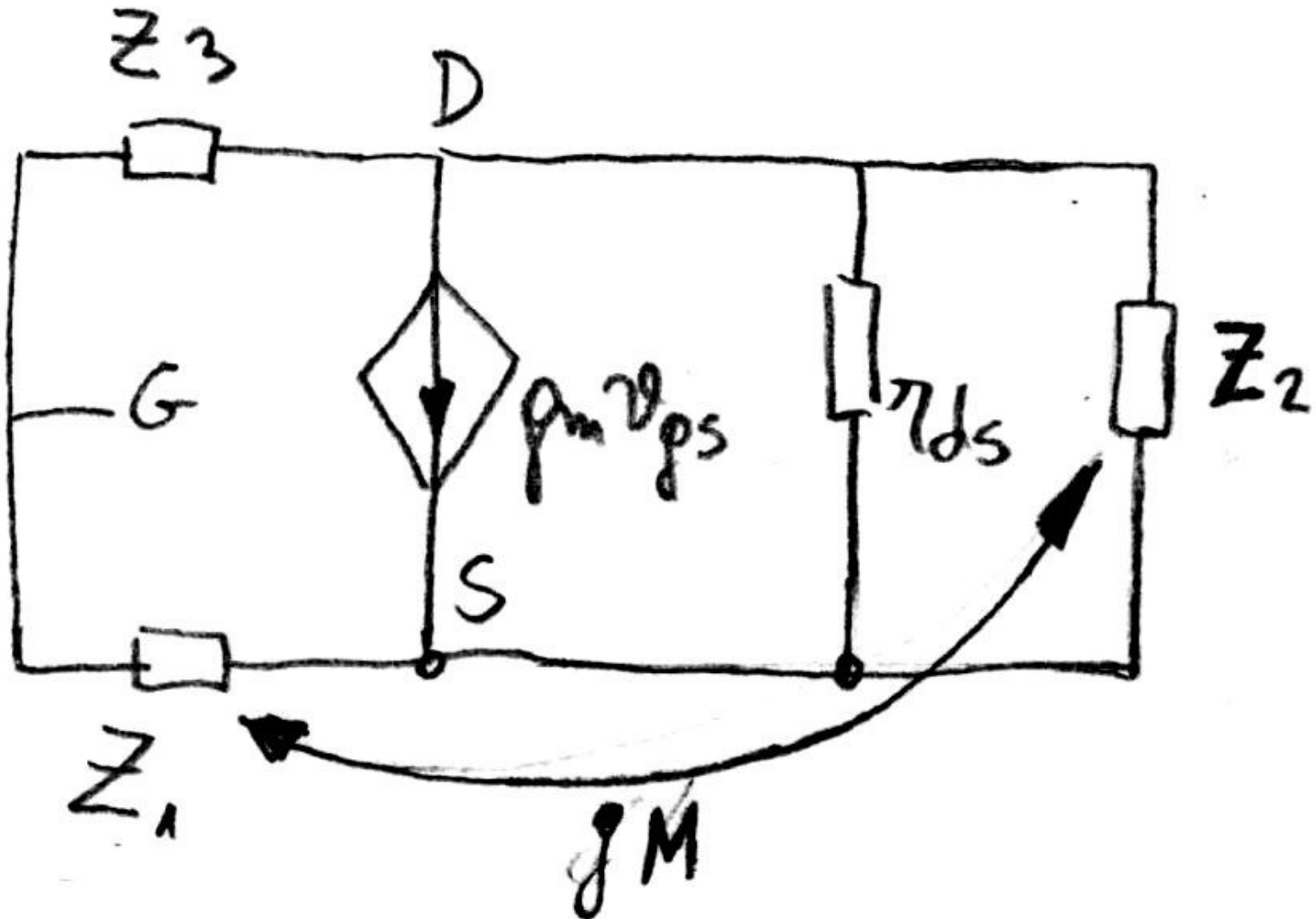
# Model za male signale za oscilator u 3 tacke




Neodredjenost amplitude kod oscilatora  $\Rightarrow$  determinanta=0

$$\text{Det} = 0$$


$$\Rightarrow \begin{cases} \text{Im} \{ \text{Det} \} = 0 \\ \text{Re} \{ \text{Det} \} = 0 \end{cases}$$


$$\Rightarrow \begin{cases} X_1 + X_2 + X_3 \pm 2X_m = 0 \\ g_m r_{ds} \geq \frac{X_2 \pm X_m}{X_1 \pm X_m} \end{cases}$$

# Oscilator u 3 tacke - primjer 1

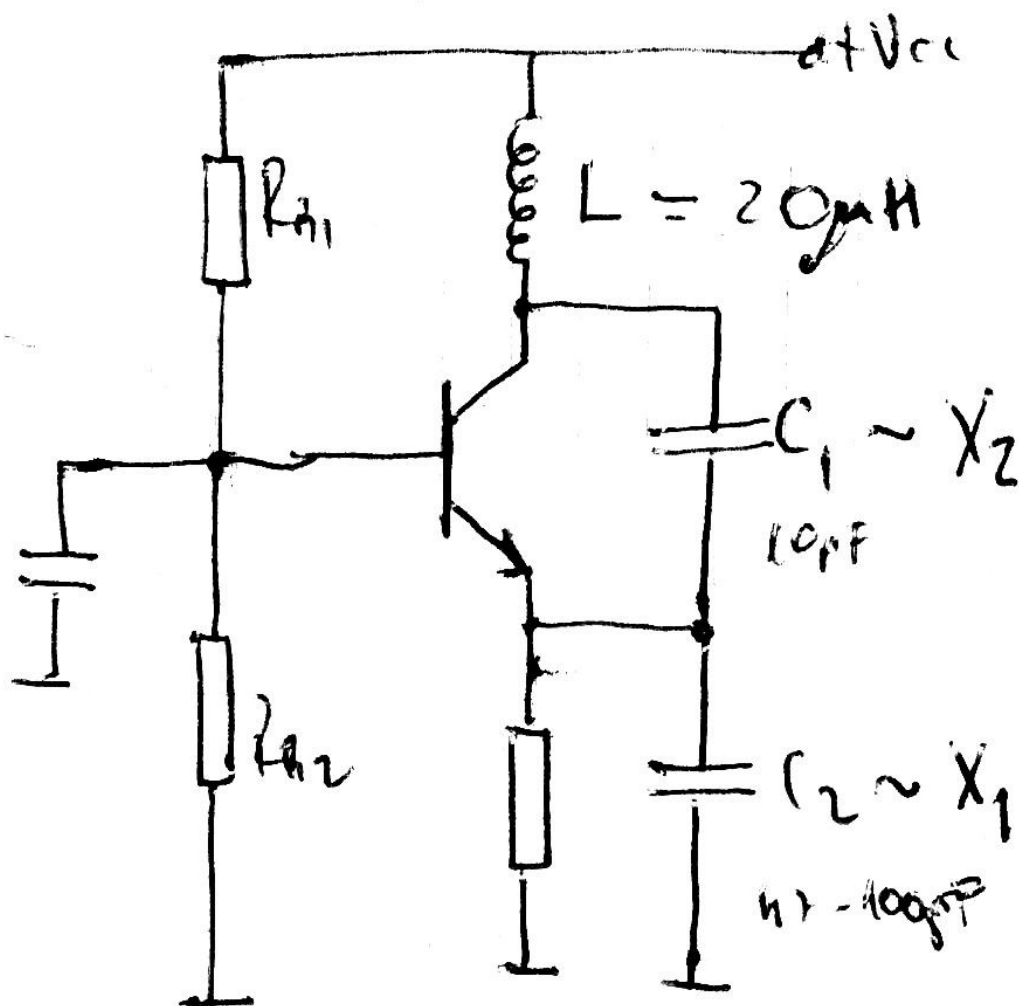

# Oscilator u 3 tacke - primjer 2

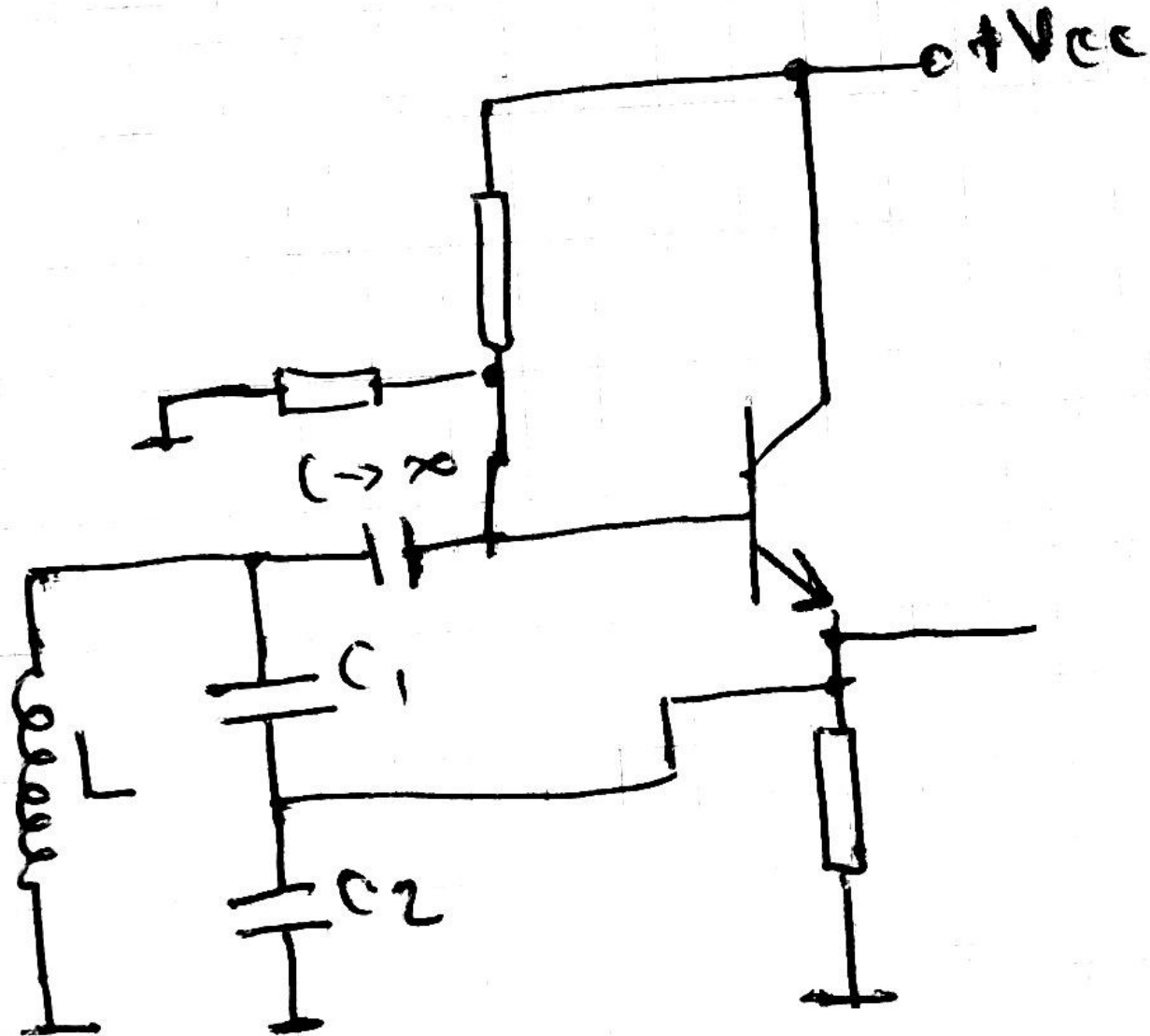


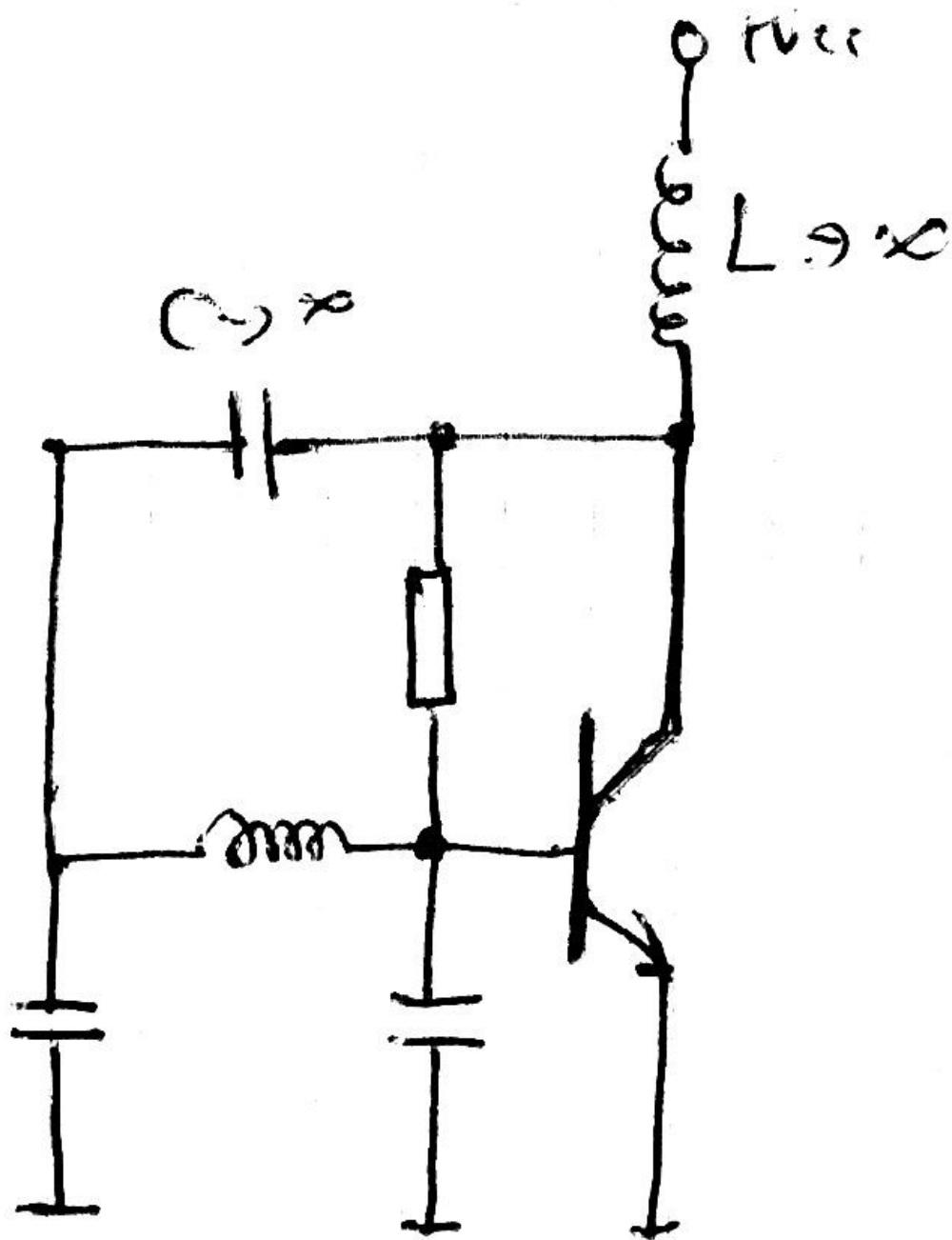


Oscilator  
u 3 tacke -  
primjer 3



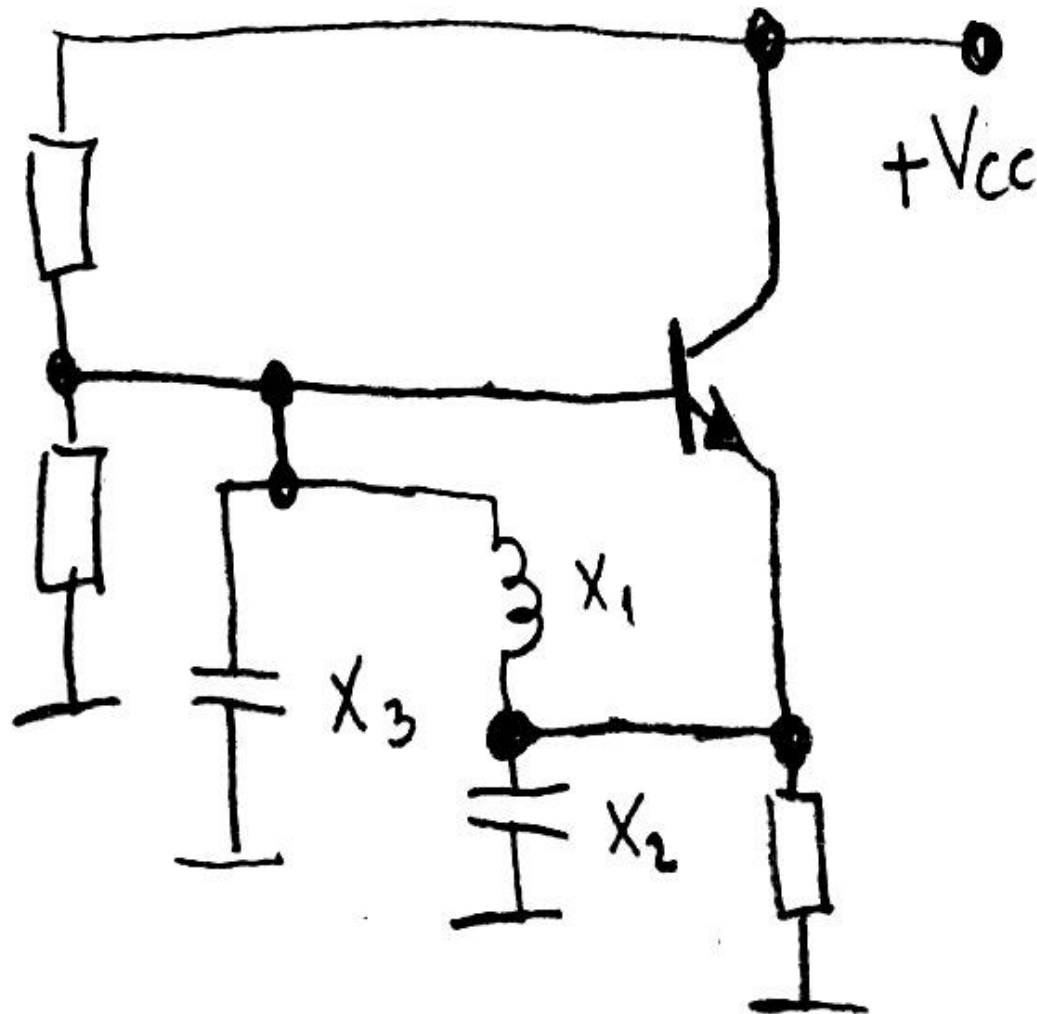Ovo kole ne moze da osciluje jer su  $X_1$  i  $X_2$  reaktanse razlicitog znaka




# Minijaturni spijunski prisluskivac - oscilator sa FM -

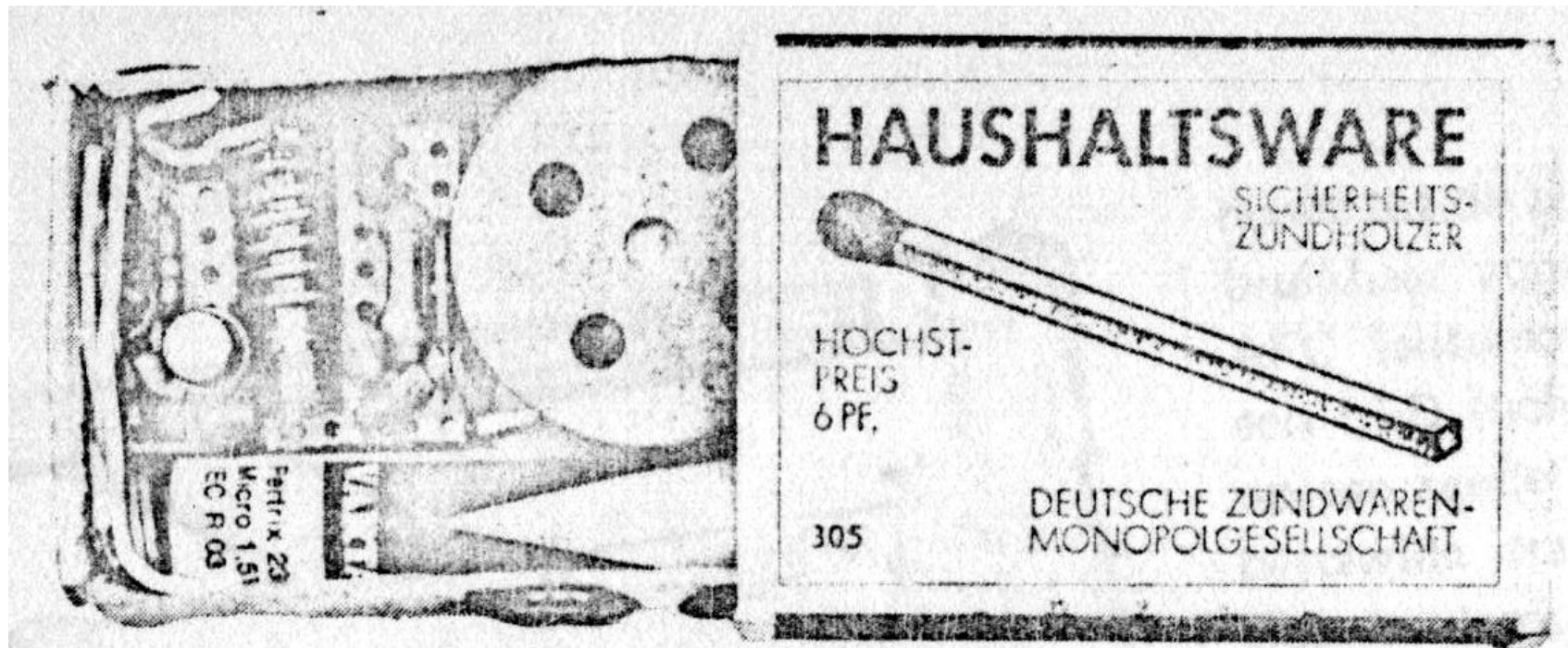


Afb. 2.

Miniatuurspion-standaardschakeling met npn-transistor voor 1,5 V.

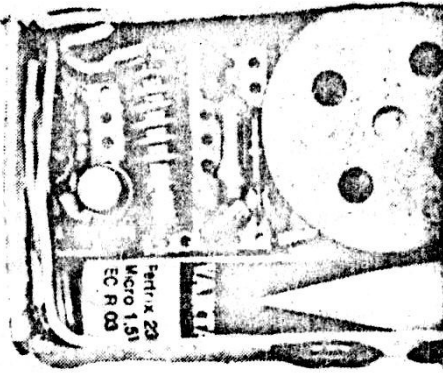

Afb. 2.  
Miniatuurspion-standaardschakeling met npn-transistor voor 1,5 V.

104 MHz  
A  
70 cm

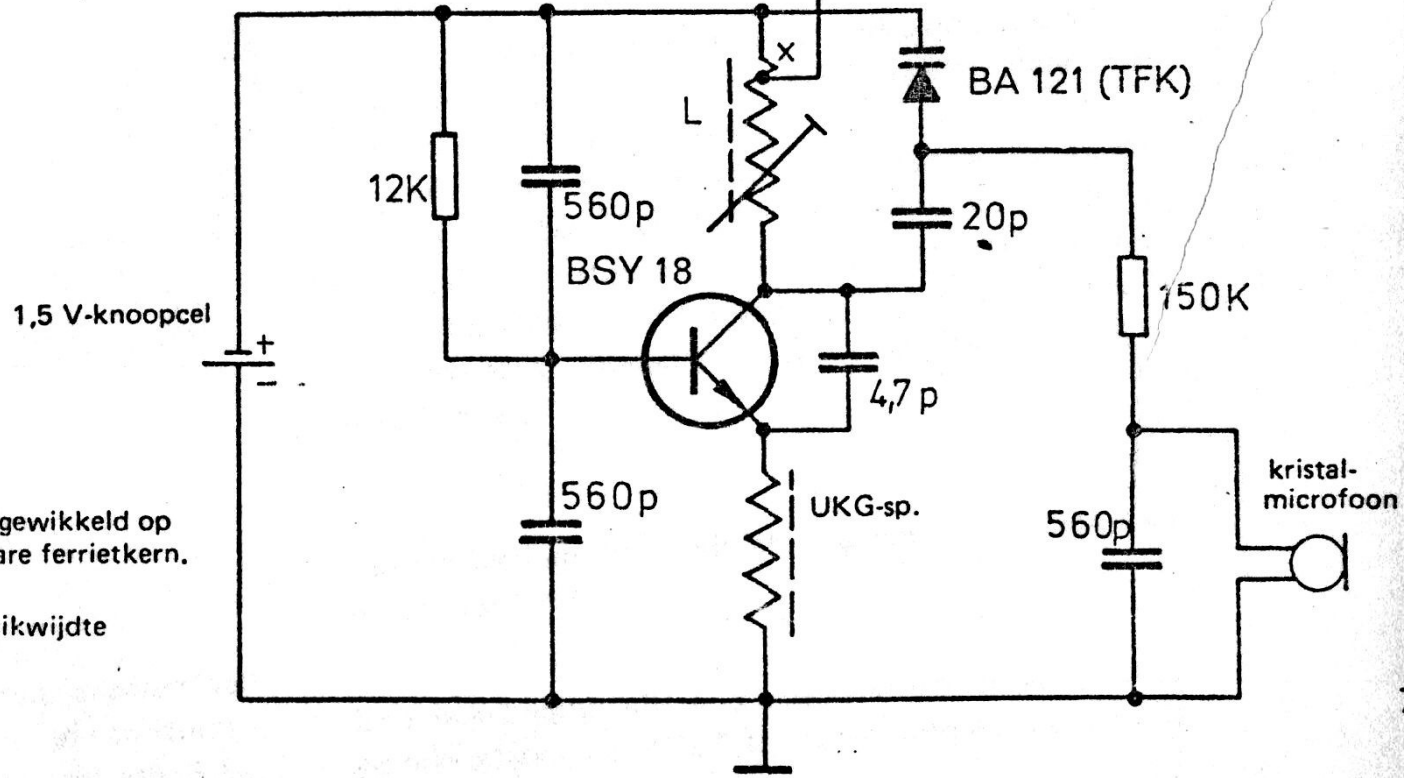

Afb. 1.  
L = 7 wdg. zilverdraad ( $\phi$  0,8 mm), gewikkeld op spoelkern ( $\phi$  5 mm) met draaibare ferrietkern.  
x = aftakking bij 0,5 ... 1 wdg.  
zendfrequentie ca. 100 MHz; reikwijdte 100 ... 200 m.