


Primjer: Rising-edge detector

Projektovati kolo koje obavlja funkciju detektora rastuće ivice signala na ulazu. Po detektovanju rastuće ivice, kolo generiše kratak impuls (**tick**). Realizovati isto kolo na bazi *Moore*-ovog i na bazi *Mealy*-jevog automata.

Rješenje:

Realizacija rising-edge detector-a na bazi Moore-ovog automata

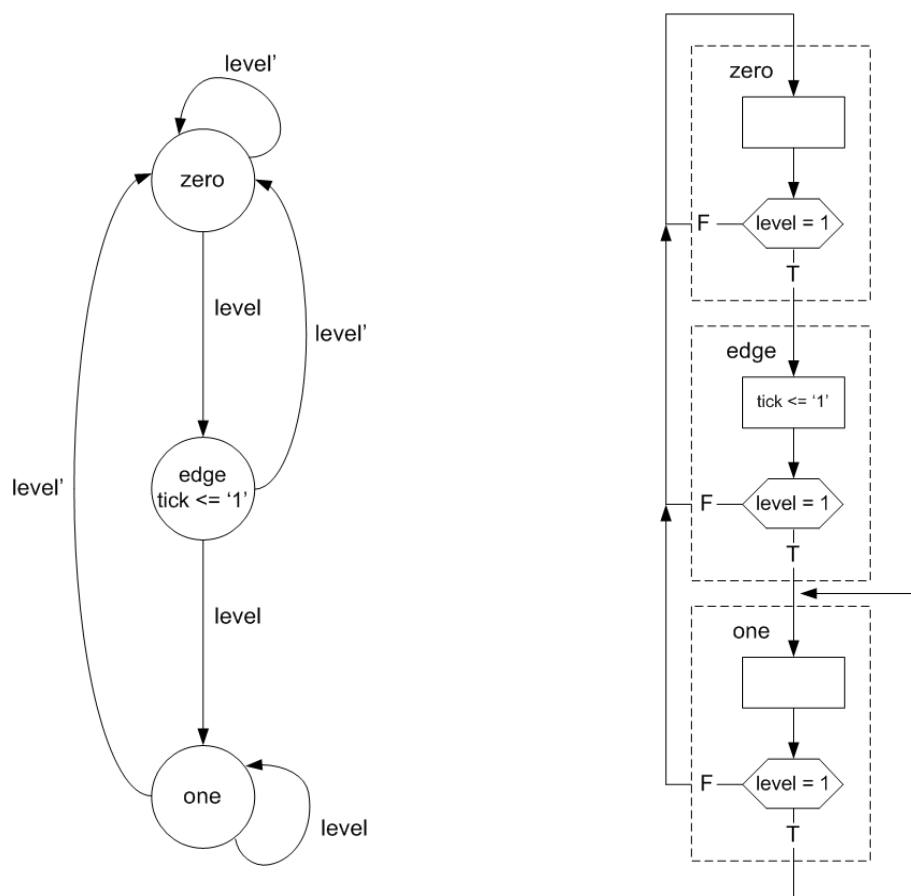Dijagram stanja i ASM dijagram kola dat je na slici 1.



Slika 1 Dijagram stanja i ASM dijagram kola za detekciju rastuće ivice ulaznog signala na bazi *Moore*-ovog automata

VHDL kod moguće realizacije **rising-edge detector**-a na bazi *Moore*-ovog automata dat je u listingu 1.

Listing 1 – Rising-edge detector na bazi Moore-ovog automata

```
library ieee;
use ieee.std_logic_1164.all;

entity egde_detector is
  port
  (
```

```

        clk, rst : in std_logic;
        level : in std_logic;
        tick : out std_logic
    );
end egde_detector;

architecture arch of egde_detector is
    type state_type is (zero, edge, one);
    signal state_reg, state_next : state_type;
begin
    process(clk, rst)
    begin
        if(rst = '1') then
            state_reg <= zero;
        elsif(clk'event and clk = '1') then
            state_reg <= state_next;
        end if;
    end process;

    process(state_reg, level)
    begin
        state_next <= state_reg;
        tick <= '0';
        case state_reg is
            when zero =>
                if (level = '1') then
                    state_next <= edge;
                end if;
            when edge =>
                tick <= '1';
                if (level = '1') then
                    state_next <= one;
                else
                    state_next <= zero;
                end if;
            when one =>
                if (level = '0') then
                    state_next <= zero;
                end if;
        end case;
    end process;
end arch;

```


Kreirati VHDL **testbench** (pogledati vježbe 4). Izvršiti simulaciju rada kola. Prikazati rezultate simulacije.

Realizacija rising-edge detector-a na bazi Mealy-ovog automata

Dijagram stanja i ASM dijagram kola dat je na slici 2.

VHDL kod moguće realizacije **rising-edge detector**-a na bazi *Mealy*-ovog automata dat je u listingu 2.

 Kreirati VHDL **testbench** (pogledati vježbe 4). Izvršiti simulaciju rada kola. Prikazati rezultate simulacije.



Slika 2 Dijagram stanja i ASM dijagram kola za detekciju rastuće ivice ulaznog signala na bazi *Moore*-ovog automata

Listing 2 – Rising-edge detector na bazi Mealy-ovog automata

```

library ieee;
use ieee.std_logic_1164.all;

entity edge_detector is
    port
    (
        clk, rst : in std_logic;
        level : in std_logic;
        tick : out std_logic
    );
end edge_detector;

architecture arch of edge_detector is
    type state_type is (zero, one);
    signal state_reg, state_next : state_type;
begin
    process(clk, rst)
    begin
        if (rst = '1') then
            state_reg <= zero;
        elsif (clk'event and clk = '1') then
            state_reg <= state_next;
        end if;
    end process;

    process(state_reg, level)
    begin
        state_next <= state_reg;
        tick <= '0';
        case state_reg is
            when zero =>
                if (level = '1') then

```


```

        state_next <= one;
        tick <= '1' ;
    end if;
    when one =>
        if (level = '0') then
            state_next <= zero;
        end if;
    end case;
end process;
end arch;

```

Primjer: Debouncing circuit

Projektovati **debouncing** kolo koje filtrira **glitch**-eve koji se generišu prilikom aktivacije mehaničkih prekidača i tastera na razvojnoj ploči, slika 3.

 


Slika 3

Rješenje:

Dijagram stanja i ASM dijagram kola dat je na slici 4.

VHDL kod moguće realizacije **debouncing** kola dat je u listingu 3.

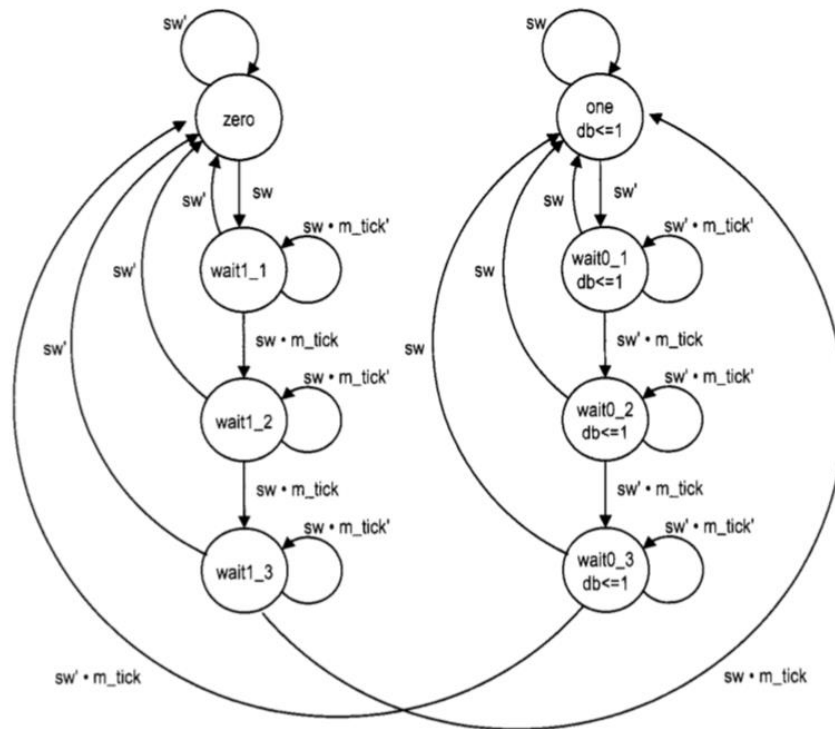Kreirati VHDL **testbench** (pogledati vježbe 4). Izvršiti simulaciju rada kola. Prikazati rezultate simulacije.



Slika 4 Dijagram stanja debouncing kola

Listing 3 – Debouncing circuit

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity debouncing_circuit is
    port
    (
        clk, rst : in std_logic;
        sw : in std_logic;
        db : out std_logic
    );
end debouncing_circuit;

architecture arch of debouncing_circuit is

    constant N : integer := 19;
    signal q_reg, q_next : unsigned(N-1 downto 0);
    signal m_tick : std_logic;
    type eg_state_type is (zero, wait1_1, wait1_2, wait1_3, one, wait0_1,
wait0_2, wait0_3);
    signal state_reg, state_next : eg_state_type;
begin
    ----- counter to generate 10 ms tick -----
    process(clk, rst)
    begin
        if (rst = '1') then
            q_reg <= (others=>'0');
        elsif (clk'event and clk = '1') then

```

```

        q_reg <= q_next;
    end if;
end process;
-- next-state logic --
q_next <= q_reg + 1;
-- output logic --
m_tick <= '1' when q_reg = 0 else
        '0';
----- debouncing circuit FSM -----
process(clk, rst)
-- state register --
begin
    if(rst = '1') then
        state_reg <= zero;
    elsif(clk'event and clk = '1') then
        state_reg <= state_next;
    end if;
end process;
-- next-state / output logic --
process(state_reg, sw, m_tick)
begin
    state_next <= state_reg;
    db <= '0';
    case state_reg is
        when zero =>
            if(sw = '1') then
                state_next <= wait1_1;
            end if;
        when wait1_1 =>
            if(sw = '0') then
                state_next <= zero;
            else
                if(m_tick = '1') then
                    state_next <= wait1_2;
                end if;
            end if;
        when wait1_2 =>
            if(sw = '0') then
                state_next <= zero;
            else
                if(m_tick = '1') then
                    state_next <= wait1_3;
                end if;
            end if;
        when wait1_3 =>
            if(sw = '0') then
                state_next <= zero;
            else
                if(m_tick = '1') then
                    state_next <= one;
                end if;
            end if;
        when one =>
            db <= '1';
            if(sw = '0') then
                state_next <= wait0_1;
            end if;
        when wait0_1 =>
            db <= '1';
            if(sw = '1') then
                state_next <= one;
            else
                if(m_tick = '1') then
                    state_next <= wait0_2;
                end if;
            end if;
    end case;
end process;


```

```

        end if;
    when wait0_2 =>
        db <= '1';
        if(sw = '1') then
            state_next <= one;
        else
            if(m_tick = '1') then
                state_next <= wait0_3;
            end if;
        end if;
    when wait0_3 =>
        db <= '1';
        if(sw = '1') then
            state_next <= one;
        else
            if(m_tick = '1') then
                state_next <= zero;
            end if;
        end if;
    end case;
end process;
end arch;

```

U cilju verifikacije rada sistema, razviti testno kolo kako je prikazano na slici 5 (pogledati vježbe 4). **Test_IN** ulazni signal je izlaz tastera, izlaze **withoutDC** i **withDC** prikazati pomoću odgovarajućih dioda na razvojnoj FPGA ploči, izlaze **TickWithoutDC**, **TickWithDC** i **db** posmatrati pomoću osciloskopa. VHDL kod **simple_counter** kola dat je u listingu 4.

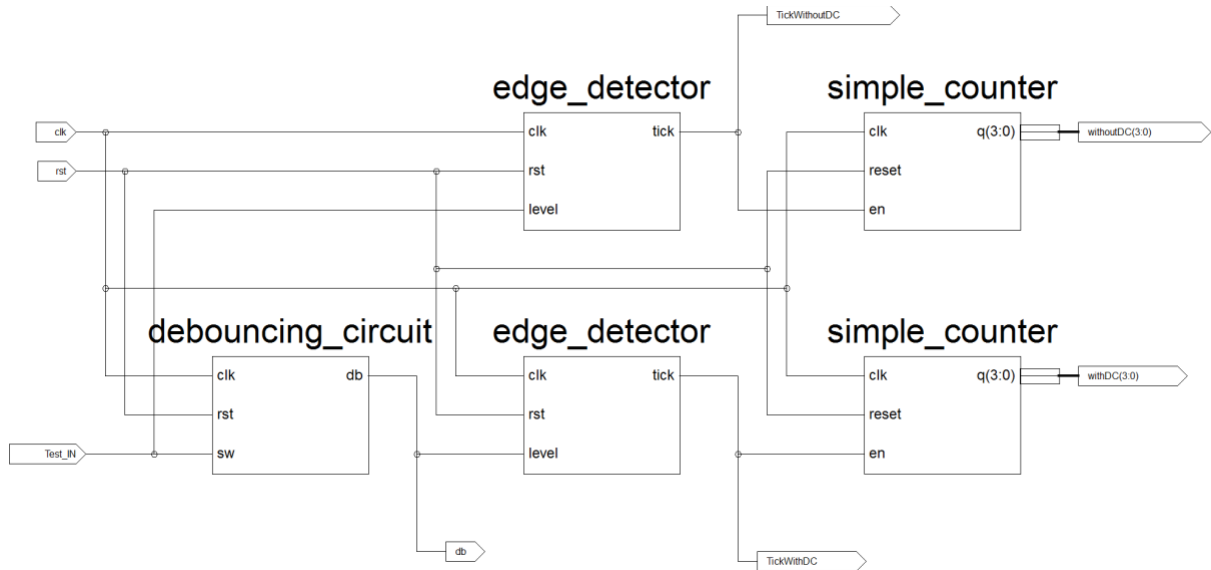

Slika 5

Izvršiti procese **synthesize**, **translate**, **map** i **place & route**.

Izvršiti implementaciju kola uz pomoć **Spartan-3E Starter Kit** razvojne platforme (pogledati uputstvo u okviru vježbi 2) i verifikovati rad kola.

Listing 4 – Simple counter

```
library IEEE;
use IEEE.std_logic_1164.all;
use ieee.numeric_std.all;

entity simple_counter is
generic(N: integer := 4);
  port
  (
    clk, reset: in std_logic;
    en : in std_logic;
    q: out std_logic_vector(N-1 downto 0)
  );
end simple_counter;
architecture arch of simple_counter is
  signal r_reg: unsigned(N-1 downto 0);
  signal r_next: unsigned(N-1 downto 0);
begin
  process(clk, reset)
  begin
    if (reset = '1') then
      r_reg <= (others=>'0');
    elsif (clk' event and clk = '1') then
      r_reg <= r_next;
    end if;
  end process;
  r_next <=
    r_reg + 1 when en = '1' else
    r_reg;
  q <= std_logic_vector(r_reg);
end arch;
```