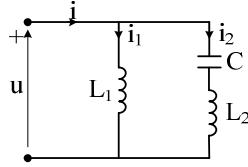


ANALIZA KOLA U USTALJENOM PSEUDOPERIODIČNOM I SLOŽENOPERIODIČNOM REŽIMU

1. Dato je reaktivno kolo prikazano na slici:



napon je složenoperiodičan

$$e = \sqrt{2}U^{(1)} \cos \omega t + \sqrt{2}U^{(3)} \cos 3\omega t$$

- a) Odrediti učestanost napona kola da ukupna struja bude prostoperiodična učestanosti osnovnog harmonika napona.
- b) Odrediti trenutnu vrijednost struje u kalemu induktivnosti L_1 , klir faktor ove struje i napona U .
- c) Odrediti aktivnu, reaktivnu i prividnu snagu i snagu izobličenja u grani sa kondenzatorom.

Rješenje

- a) ako se prvo odredi ulazna impedansa

$$\underline{Z}_{ul}^{(k)} = \frac{jk\omega L_1 \left(jk\omega L_2 + \frac{1}{jk\omega C} \right)}{jk\omega L_1 + jk\omega L_2 + \frac{1}{jk\omega C}} = \frac{jk\omega L_1 (1 - k^2 \omega^2 L_2 C)}{1 - k^2 \omega^2 C (L_1 + L_2)}$$

poznato je da važi

$$\underline{I}^{(k)} = \frac{\underline{U}^{(k)}}{\underline{Z}_{ul}^{(k)}} \rightarrow \underline{I}^{(1)} = \frac{\underline{U}^{(1)}}{\underline{Z}_{ul}^{(1)}} \quad \underline{I}^{(3)} = \frac{\underline{U}^{(3)}}{\underline{Z}_{ul}^{(3)}}$$

Da bi ulazna struja bila prostoperiodična sa učestanostju osnovnog harmonika napona potrebno je da je struja trećeg harmonika nula, tj. odgovarajuća ulazna impedansa mora biti beskonačno velika.

$$\underline{Z}_{ul}^{(3)} = \infty \rightarrow \frac{j3\omega L_1 (1 - 9\omega^2 L_2 C)}{1 - 9\omega^2 C (L_1 + L_2)} \rightarrow \infty$$

$$1 - 9\omega^2 C (L_1 + L_2) = 0 \rightarrow \omega = \frac{1}{3\sqrt{C(L_1 + L_2)}}$$

$$\text{b) } \underline{I}_1^{(k)} = \frac{\underline{U}^{(k)}}{jk\omega L_1} \rightarrow \underline{I}_1^{(1)} = \frac{\underline{U}^{(1)}}{j\omega L_1} = \frac{\underline{U}^{(1)}}{\omega L_1} / -90^\circ \quad \underline{I}_1^{(3)} = \frac{\underline{U}^{(3)}}{j3\omega L_1} = \frac{\underline{U}^{(3)}}{3\omega L_1} / -90^\circ$$

sada je vremenski oblik struje

$$i_1(t) = i_1^{(1)}(t) + i_1^{(3)}(t) = \sqrt{2} \frac{\underline{U}^{(1)}}{\omega L_1} \cos \left(\omega t - \frac{\pi}{2} \right) + \sqrt{2} \frac{\underline{U}^{(3)}}{3\omega L_1} \cos \left(3\omega t - \frac{\pi}{2} \right)$$

klir faktor je prema definiciji

$$k = \frac{\sqrt{(I^{(2)})^2 + (I^{(3)})^2 + (I^{(4)})^2 + \dots + (I^{(k)})^2}}{I} = \frac{\sqrt{(I^{(2)})^2 + (I^{(3)})^2 + (I^{(4)})^2 + \dots + (I^{(k)})^2}}{\sqrt{(I^{(0)})^2 + (I^{(1)})^2 + (I^{(2)})^2 + \dots + (I^{(k)})^2}}$$

klir faktor struje i_1

$$k_{i_1} = \frac{i_1^{(3)}}{\sqrt{(I_1^{(1)})^2 + (I_1^{(3)})^2}} = \frac{\frac{\underline{U}^{(3)}}{3\omega L_1}}{\sqrt{\left(\frac{\underline{U}^{(1)}}{\omega L_1}\right)^2 + \left(\frac{\underline{U}^{(3)}}{3\omega L_1}\right)^2}} = \frac{\underline{U}^{(3)}}{\sqrt{9(\underline{U}^{(1)})^2 + (\underline{U}^{(3)})^2}}$$

klir faktor napona u

$$k_u = \frac{U^{(3)}}{\sqrt{(U^{(1)})^2 + (U^{(3)})^2}}$$

c) U grani sa kondenzatorom aktivna snaga je jednaka nuli jer nema aktivnih potrošača (otpornosti). Kako bi se odredila snaga, potrebno je prvo odrediti impedansu posmatrane grane

$$\underline{Z}_2^{(k)} = jk\omega L_2 + \frac{1}{jk\omega C} = \frac{jk^2\omega^2 L_2 C - j}{k\omega C} = -j \frac{1 - k^2\omega^2 L_2 C}{k\omega C}$$

ako se zamjeni ranije dobijena vrijednost ω

$$\underline{Z}_2^{(1)} = -j \frac{1 - \frac{1}{9C(L_1 + L_2)} L_2 C}{\frac{1}{3\sqrt{C(L_1 + L_2)}} C} = -j \frac{\frac{9(L_1 + L_2) - L_2}{9C(L_1 + L_2)}}{\frac{1}{3\sqrt{C(L_1 + L_2)}}} = -j \frac{9L_1 + 8L_2}{3\sqrt{C(L_1 + L_2)}}$$

$$\underline{Z}_2^{(3)} = -j \frac{1 - 9 \frac{1}{9C(L_1 + L_2)} L_2 C}{3 \frac{1}{3\sqrt{C(L_1 + L_2)}} C} = -j \frac{\frac{9C(L_1 + L_2) - 9L_2 C}{9C(L_1 + L_2)}}{3 \frac{1}{3\sqrt{C(L_1 + L_2)}} C} = -j \frac{3L_1}{\sqrt{C(L_1 + L_2)}}$$

reakтивna snaga posmatrane grane kola je

$$\underline{Q}_2^{(1)} = -\frac{(U^{(1)})^2}{Z_2^{(1)}} \quad \underline{Q}_2^{(3)} = -\frac{(U^{(3)})^2}{Z_2^{(3)}}$$

ukupna reaktivna snaga je

$$Q_2 = Q_2^{(1)} + Q_2^{(3)} = -\frac{3\sqrt{C(L_1 + L_2)}}{9L_1 + 8L_2} [U^{(1)}]^2 - \frac{\sqrt{C(L_1 + L_2)}}{L_1} [U^{(3)}]^2$$

Pravidna snaga je prema definiciji


$$S_2 = UI_2 = \sqrt{(U^{(1)})^2 + (U^{(3)})^2} \sqrt{\left(\frac{U^{(1)}}{Z_2^{(1)}}\right)^2 + \left(\frac{U^{(3)}}{Z_2^{(3)}}\right)^2}$$

Snaga izobličenja je

$$\begin{aligned} D_2 &= \sqrt{S_2^2 - Q_2^2} = \sqrt{\left((U^{(1)})^2 + (U^{(3)})^2\right) \left(\left(\frac{U^{(1)}}{Z_2^{(1)}}\right)^2 + \left(\frac{U^{(3)}}{Z_2^{(3)}}\right)^2\right) - \left(\frac{(U^{(1)})^2}{Z_2^{(1)}} + \frac{(U^{(3)})^2}{Z_2^{(3)}}\right)^2} = \\ &= \sqrt{\left(\frac{(U^{(1)})^4}{(Z_2^{(1)})^2} + \frac{(U^{(1)})^2(U^{(3)})^2}{(Z_2^{(3)})^2} + \frac{(U^{(3)})^2(U^{(1)})^2}{(Z_2^{(1)})^2} + \frac{(U^{(3)})^4}{(Z_2^{(3)})^2}\right) - \left(\frac{(U^{(1)})^4}{(Z_2^{(1)})^2} + \frac{(U^{(3)})^4}{(Z_2^{(3)})^2}\right)} = \\ &= \sqrt{\frac{(U^{(1)})^2(U^{(3)})^2}{(Z_2^{(3)})^2} + \frac{(U^{(3)})^2(U^{(1)})^2}{(Z_2^{(1)})^2} - 2 \frac{(U^{(1)})^2(U^{(3)})^2}{Z_2^{(1)}Z_2^{(3)}} - \frac{(U^{(3)})^4}{(Z_2^{(3)})^2}} = \\ &= \sqrt{\frac{(U^{(1)})^2(U^{(3)})^2}{(Z_2^{(3)})^2} + \frac{(U^{(3)})^2(U^{(1)})^2}{(Z_2^{(1)})^2} - 2 \frac{(U^{(1)})^2(U^{(3)})^2}{Z_2^{(1)}Z_2^{(3)}}} = \sqrt{\frac{U^{(1)}U^{(3)}}{Z_2^{(3)}} - \frac{U^{(3)}U^{(1)}}{Z_2^{(1)}}} = \left| \frac{U^{(1)}U^{(3)}}{Z_2^{(3)}} - \frac{U^{(3)}U^{(1)}}{Z_2^{(1)}} \right| = \\ &= U^{(1)}U^{(3)} \left(\frac{\sqrt{C(L_1 + L_2)}}{3L_1} - \frac{3\sqrt{C(L_1 + L_2)}}{9L_1 + 8L_2} \right) \end{aligned}$$

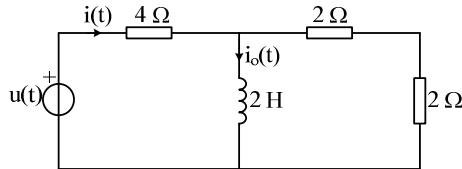2. Naći izraz za struju $i_0(t)$, ako je napon izvora dat u obliku Furijeovog reda

$$u(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{1+n^2} (\cos nt - n \sin nt).$$



Rješenje

Izraz za ulazni napon može se transformisati jer važi

$$k_1 \cos x + k_2 \sin x = \sqrt{k_1^2 + k_2^2} \cos\left(x + \arctg \frac{-k_2}{k_1}\right)$$

pa je napon

$$u(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{\sqrt{1+n^2}} \cos(nt + \arctg n)$$

ili ako se razvije red

$$u(t) = 1 - 1.414 \cos(t + 45^\circ) + 0.8944 \cos(2t + 63.45^\circ) - 0.6345 \cos(3t + 71.56^\circ) + \dots$$

Struja i_o se može naći ako se prvo odredi struja i , pa onda struja i_o na osnovu strujnog razdjelnika.

Ulagana impedansa n -tog harmonika je

$$\underline{Z}^{(n)} = 4 + \frac{j\omega_n 2 \cdot 4}{4 + j\omega_n 2} = \frac{8 + j\omega_n 8}{2 + j\omega_n}$$

struja je

$$\underline{I}^{(n)} = \frac{\underline{U}^{(n)}}{\underline{Z}^{(n)}} = \frac{2 + j\omega_n}{8 + j\omega_n 8} \underline{U}^{(n)} \rightarrow \underline{I}_o^{(n)} = \frac{4}{4 + j\omega_n 2} \underline{I}^{(n)} = \frac{4}{4 + j\omega_n 2} \frac{2 + j\omega_n}{8 + j\omega_n 8} \underline{U}^{(n)} = \frac{1}{4 + j\omega_n 4} \underline{U}^{(n)}$$

Kako se vidi iz definicije reda, važi

$$\omega_n = n \rightarrow \underline{I}_o^{(n)} = \frac{\underline{U}^{(n)}}{4 + jn4} = \frac{\underline{U}^{(n)}}{4\sqrt{1+n^2}/\arctg n}$$

$$n = 0 \rightarrow \underline{I}_o = \frac{1}{4}$$

Za n -ti harmonik

$$\underline{U}^{(n)} = \frac{2(-1)^n}{\sqrt{1+n^2}} / \arctg n \rightarrow \underline{I}_o^{(n)} = \frac{\frac{2(-1)^n}{\sqrt{1+n^2}} / \arctg n}{4\sqrt{1+n^2} / \arctg n} = \frac{2(-1)^n}{4(1+n^2)} = \frac{(-1)^n}{2(1+n^2)} / 0^\circ$$


sada je vremenski oblik struje

$$i_o(t) = \frac{1}{4} + \sum_{n=1}^{\infty} \frac{(-1)^n}{2(1+n^2)} \cos nt [A]$$

3. Za kolo prema slici poznato je: ω , G , $i_g(t) = I^{(1)} \cos \omega t + I^{(3)} \cos 3\omega t$

a) Odrediti parametre L i C tako da osnovni harmonik napona otpornika ne zavisi od G i da amplituda trećeg harmonika struje u otporniku iznosi 90% od amplitude trećeg harmonika struje izvora.

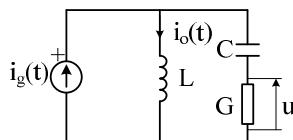b) Izračunati trenutnu vrijednost napona na otporniku i snagu izobličenja kondenzatora.



Rješenje

Napon na otporniku je, koristeći strujni razdjelnik

$$\underline{U}^{(k)} = \frac{jk\omega L}{jk\omega L + \frac{1}{G} + \frac{1}{jk\omega C}} \underline{I}_g^{(k)} \cdot \frac{1}{G} = \frac{jk\omega L}{jk\omega GL + 1 + \frac{G}{jk\omega C}} \underline{I}_g^{(k)} = \frac{jk\omega L}{1 + jG\left(k\omega L - \frac{1}{k\omega C}\right)} \underline{I}_g^{(k)}$$

Prvi uslov zadatka je da osnovni harmonik napona na otporniku ne zavisi od G, a to je ispunjeno samo u slučaju kada važi

$$\omega L - \frac{1}{\omega C} = 0 \quad (*)$$

Drugi uslov je da je amplituda trećeg harmonika struje u otporniku iznosi 90% amplitude trećeg harmonika izvora.

$$\underline{I}^{(k)} = GU^{(k)} = G \frac{jk\omega L}{1 + jG\left(k\omega L - \frac{1}{k\omega C}\right)} \underline{I}_g^{(k)}$$

pa se može pisati

$$0.9I_g^{(3)} = \frac{3\omega GL}{\sqrt{1 + G^2\left(3\omega L - \frac{1}{3\omega C}\right)^2}} I_g^{(3)} \quad (**)$$

Riješavajući sistem koji čine relacije (*) i (**) dolazi se do

$$C = \frac{2G}{\omega} \quad L = \frac{1}{2G\omega}$$

b) Trenutna vrijednost napona

$$\underline{U}^{(k)} = \frac{j \frac{k}{2G}}{1 + j \frac{1}{2} \left(k - \frac{1}{k} \right)} \underline{I}_g^{(k)} \rightarrow \underline{U}^{(1)} = j \frac{1}{2G} \underline{I}_g^{(1)} \rightarrow u^{(1)}(t) = \frac{1}{2G} I^{(1)} \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\underline{U}^{(3)} = j \frac{3}{2G} \frac{1}{1 + j \frac{3}{4}} \underline{I}_g^{(3)} = \frac{3}{2G} \frac{3}{4 - j3} \underline{I}_g^{(3)} = 0.9 \frac{\underline{I}_g^{(3)}}{G} e^{j\arctg \frac{3}{4}} \rightarrow u^{(3)}(t) = 0.9 \frac{I^{(3)}}{G} \cos\left(3\omega t + \arctg \frac{3}{4}\right)$$

$$u(t) = u^{(1)}(t) + u^{(3)}(t)$$

Snaga izobličenja je

$$D_C = \sqrt{S^2 - P^2 - Q^2} = \frac{1}{2} |U_c^{(1)} I_c^{(3)} - U_c^{(3)} I_c^{(1)}| = \frac{1}{2} \left| \frac{1}{\omega C} I_c^{(1)} I_c^{(3)} - \frac{1}{3\omega C} I_c^{(3)} I_c^{(1)} \right| = \frac{1}{3\omega C} I_c^{(1)} I_c^{(3)}$$

zna se da važi


$$I_c^{(1)} = I_G^{(1)} = GU^{(1)} = \frac{I_g^{(1)}}{2}$$

$$I_c^{(3)} = I_G^{(3)} = GU^{(3)} = 0.9I_g^{(3)}$$

pa je

$$D_C = \frac{1}{3 \cdot 26} \frac{I_g^{(1)}}{2} 0.9I_g^{(3)} = \frac{3I_g^{(1)} I_g^{(3)}}{406}$$

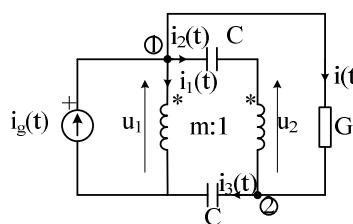4. Ako je struja strujnog generatora u kolu prema slici $i_g(t) = I_o + I_1 \cos \omega t$ odrediti trenutnu vrijednost ustaljenog odziva u otporniku ako je $m=1/2$.



Rješenje

Cilj je odrediti struju $i(t)$. Sa slike važi:

$$\frac{\underline{U}_1}{\underline{U}_2} = m \quad \frac{\underline{I}_1}{\underline{I}_2} = -\frac{1}{m}$$

a kako je m poznato onda

$$\underline{U}_2 = 2\underline{U}_1 \quad \underline{I}_1 = -2\underline{I}_2$$

Iz KZS za čvor 1:

$$\underline{I}_1 + \underline{I}_2 + \underline{I} = \underline{I}_g \rightarrow -2\underline{I}_2 + \underline{I}_2 + \underline{I} = \underline{I}_g \rightarrow \underline{I}_2 = \underline{I} - \underline{I}_g$$

Iz KZS za čvor 2:

$$\underline{I}_3 - \underline{I}_2 - \underline{I} = 0 \rightarrow \underline{I}_3 = 2\underline{I} - \underline{I}_g$$

Naponi \underline{U}_1 i \underline{U}_2 su

$$\underline{U}_1 = \frac{\underline{I}}{G} + \frac{1}{j\omega C} \underline{I}_3 = \frac{\underline{I}}{G} + \frac{1}{j\omega C} (2\underline{I} - \underline{I}_g)$$

$$\underline{U}_2 = \frac{\underline{I}}{G} - \frac{1}{j\omega C} \underline{I}_2 = \frac{\underline{I}}{G} - \frac{1}{j\omega C} (\underline{I} - \underline{I}_g)$$

Vrativši se na početnu relaciju za napone idealnog transformatora

$$\underline{U}_2 = 2\underline{U}_1 \rightarrow \frac{\underline{I}}{G} - \frac{1}{j\omega C} (\underline{I} - \underline{I}_g) = 2 \left[\frac{\underline{I}}{G} + \frac{1}{j\omega C} (2\underline{I} - \underline{I}_g) \right]$$

$$\frac{\underline{I}}{G} + 5 \frac{1}{j\omega C} \underline{I} - \frac{3}{j\omega C} \underline{I}_g = 0 \rightarrow \underline{I} = \frac{\frac{3}{j\omega C}}{\frac{1}{G} + \frac{5}{j\omega C}} \underline{I}_g = \frac{3G}{5G + j\omega C} \underline{I}_g$$

Struja k-tog harmonika u ustaljenom režimu je:

$$\underline{I}^{(k)} = \frac{3G}{5G + jk\omega C} \underline{I}_g^{(k)} \rightarrow k = 0 \quad \underline{I}^{(o)} = \frac{3}{5} \underline{I}_g^{(o)} = \frac{3}{5} I_o$$

$$k = 1 \quad \underline{I}^{(1)} = \frac{3G}{5G + j\omega C} \underline{I}_g^{(1)} = \frac{3I_1}{\sqrt{25 + \frac{1}{G^2} C^2 \omega^2}} e^{-j\arctg \frac{\omega C}{5G}}$$

sada je tražena struja u vremenskom domenu

$$i(t) = \frac{3}{5} I_o + \frac{3I_1}{\sqrt{25 + \frac{1}{G^2} C^2 \omega^2}} \cos \left(\omega t - \arctg \frac{\omega C}{5G} \right)$$

TRIGONOMETRIJSKI FURIJEOV RED

Prema definiciji funkcija se razlaže u Furijeov red prema izrazu sa koeficijentima:

$$f(t) = \frac{a_o}{2} + \sum_{n=1}^{\infty} (a_n \cos n\omega_o t + b_n \sin n\omega_o t)$$

$$a_o = \frac{2}{T} \int_0^T f(t) dt$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_o t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_o t dt$$

Alternativna forma je amplitudno fazna forma:

$$f(t) = \frac{a_o}{2} + \sum_{n=1}^{\infty} A_n \cos(n\omega_o t + \phi_n)$$

$$A_n = \sqrt{a_n^2 + b_n^2} \quad \phi_n = -\arctg \frac{b_n}{a_n} \quad \underline{A}_n = a_n + jb_n$$

$$* a \cos \alpha + b \sin \alpha = \sqrt{a^2 + b^2} \cos \left(\alpha - \arctan \frac{b}{a} \right)$$

Grafik A_n po $n\omega_o$ naziva se amplitudski spektar, a grafik ϕ_n po $n\omega_o$ naziva se fazni spektar. Oba grafika čine frekvencijski spektar. Neki korisni integrali:

$$\int \cos at dt = \frac{1}{a} \sin at \quad \int \sin at dt = -\frac{1}{a} \cos at$$

$$\int t \cos at dt = \frac{1}{a^2} \cos at + \frac{1}{a} t \sin at \quad \int t \sin at dt = \frac{1}{a^2} \sin at - \frac{1}{a} t \cos at$$

Određivanje faznog stava kompleksnog broja

$$z = x + jy \quad \theta = \arctg \frac{y}{x}$$

$$z = -x + jy \quad \theta = 180^\circ - \arctg \frac{y}{x}$$

$$z = -x - jy \quad \theta = 180^\circ + \arctg \frac{y}{x}$$

$$z = x - jy \quad \theta = 360^\circ - \arctg \frac{y}{x}$$

Neki korisni identiteti:

$$\cos 2n\pi = 1 \quad \cos n\pi = (-1)^n$$


$$\sin 2n\pi = 0 \quad \sin n\pi = 0$$

$$\cos \frac{n\pi}{2} = \begin{cases} (-1)^{\frac{n}{2}}, & n \text{ parno} \\ 0, & n \text{ neparno} \end{cases} \quad \sin \frac{n\pi}{2} = \begin{cases} (-1)^{\frac{(n-1)}{2}}, & n \text{ parno} \\ 0, & n \text{ neparno} \end{cases}$$

$$e^{jn\pi} = 1 \quad e^{jn\pi} = (-1)^n$$

$$e^{jn\frac{\pi}{2}} = \begin{cases} (-1)^{\frac{n}{2}}, & n \text{ parno} \\ j(-1)^{\frac{(n-1)}{2}}, & n \text{ neparno} \end{cases}$$

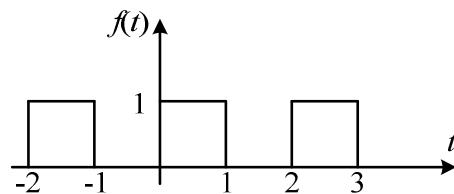1. Razviti u Furijeov red signal prikazan na slici:



Rješenje

Funkcija se može zapisati kao:

$$f(t) = \begin{cases} 1, & 0 < t < 1 \\ 0, & 1 < t < 2 \end{cases} \quad T = 2 \rightarrow \omega_o = \frac{2\pi}{T} = \pi$$

Sada su koeficijenti Furijeovog reda

$$a_o = \frac{2}{T} \int_0^T f(t) dt = \frac{2}{2} \left(\int_0^1 1 dt + \int_1^2 0 dt \right) = 1$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_o t dt = \frac{2}{2} \left(\int_0^1 1 \cdot \cos n\omega_o t dt + \int_1^2 0 \cdot \cos n\omega_o t dt \right) = \frac{1}{n\pi} \sin n\pi = 0$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_o t dt = \frac{2}{2} \left(\int_0^1 1 \cdot \sin n\omega_o t dt + \int_1^2 0 \cdot \sin n\omega_o t dt \right) = -\frac{1}{n\pi} (\cos n\pi - 1) = \frac{1}{n\pi} [1 - (-1)^n]$$

Za b_n može se pisati

$$b_n = \begin{cases} 2/n\pi, & n \text{ neparno} \\ 0, & n \text{ parno} \end{cases}$$

Sada je razvoj funkcije u red


$$f(t) = \frac{1}{2} + \frac{2}{\pi} \sin \pi t + \frac{2}{3\pi} \sin 3\pi t + \frac{2}{5\pi} \sin 5\pi t + \dots = \frac{1}{2} + \sum_{k=1}^{\infty} \frac{1}{n\pi} \sin n\pi t, \text{ gdje je } n=2k-1$$

Amplitudski i fazni spektar se dobijaju prema:


$$A_n = \sqrt{a_n^2 + b_n^2} = |b_n| = \begin{cases} 2/n\pi, & n \text{ neparno} \\ 0, & n \text{ parno} \\ 1/2, & n=0 \end{cases}$$

$$\phi_n = -\operatorname{arctg} \frac{b_n}{a_n} = \begin{cases} -90^\circ, & n \text{ neparno} \\ 0, & n \text{ parno} \end{cases}$$

a grafička predstava

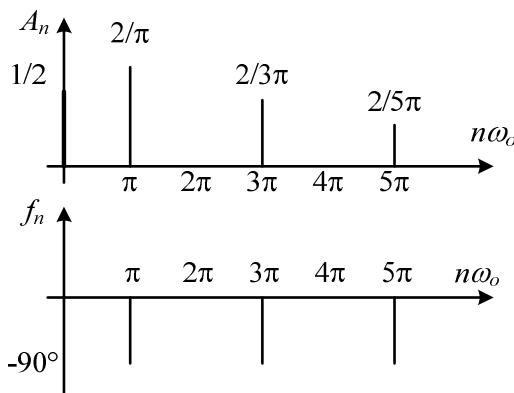

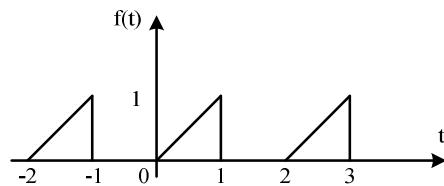2. Razviti u Furijeov red periodičnu funkciju prikazanu na slici:



Rješenje

Periodična funkcija može se napisati kao:

$$f(t) = \begin{cases} t, & 0 < t < 1 \\ 0, & 1 < t < 2 \end{cases} \quad T = 2 \rightarrow \omega_o = \frac{2\pi}{T} = \pi$$

Sada su koeficijenti Furijeovog reda

$$a_o = \frac{2}{T} \int_0^T f(t) dt = \frac{2}{2} \left(\int_0^1 t dt + \int_1^2 0 dt \right) = \frac{1}{2}$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_o t dt = \frac{2}{2} \left(\int_0^1 t \cdot \cos n\pi t dt + \int_1^2 0 \cdot \cos n\pi t dt \right) = \frac{1}{n^2 \pi^2} (\cos n\pi - 1) = \frac{(-1)^n - 1}{n^2 \pi^2}$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_o t dt = \frac{2}{2} \left(\int_0^1 t \cdot \sin n\pi t dt + \int_1^2 0 \cdot \sin n\pi t dt \right) = -\frac{\cos n\pi}{n\pi} = -\frac{(-1)^n}{n\pi} = \frac{(-1)^{n+1}}{n\pi}$$

sada je razvoj funkcije u red

$$f(t) = \frac{1}{4} + \sum_{n=1}^{\infty} \left[\frac{(-1)^n - 1}{n^2 \pi^2} \cos n\pi t + \frac{(-1)^{n+1}}{n\pi} \sin n\pi t \right]$$

Može se primjetiti da važi, za parne harmonike

$$a_n = 0 \quad b_n = -\frac{1}{n\pi}$$

$$A_n / \phi_n = a_n - jb_n = 0 + j \frac{1}{n\pi}$$

$$A_n = \sqrt{a_n^2 + b_n^2} = |b_n| = \frac{1}{n\pi}, \quad n = 2, 4, \dots$$

$$\phi_n = 90^\circ, \quad n = 2, 4, \dots$$

za neparne harmonike


$$a_n = -\frac{2}{n^2 \pi^2} \quad b_n = \frac{1}{n\pi}$$

$$A_n / \phi_n = a_n - jb_n = -\frac{2}{n^2 \pi^2} - j \frac{1}{n\pi}$$


$$A_n = \sqrt{a_n^2 + b_n^2} = \frac{1}{n^2 \pi^2} \sqrt{4 + n^2 \pi^2}, \quad n = 1, 3, \dots$$

$$\phi_n = 180^\circ + \operatorname{arctg} \frac{n\pi}{2}, \quad n = 1, 3, \dots$$

Grafički prikaz je

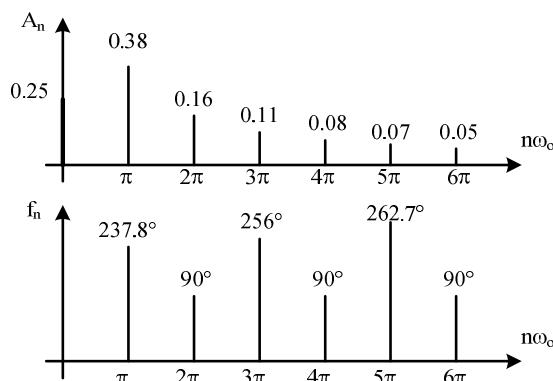

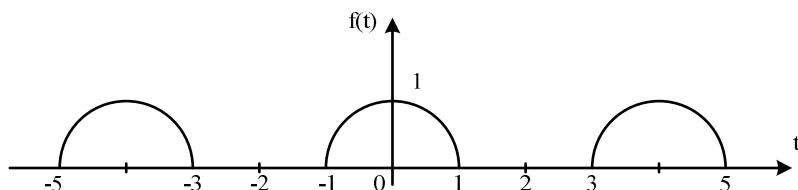3. Odrediti Furijeov red funkcije prikazane na slici



Rješenje

Ovo je parna funkcija (simetrična je u odnosu na ordinatu), pa je $b_n = 0$. Sa slike se vidi da je $T=4$, pa slijedi

$$\omega = \frac{2\pi}{T} = \frac{\pi}{2}$$

Funkcija se može zapisati u obliku

$$f(t) = \begin{cases} 0, & -2 < t < -1 \\ \cos \frac{\pi}{2} t, & -1 < t < 1 \\ 0, & 1 < t < 2 \end{cases}$$

Sada su koeficijenti reda:

$$a_o = 2 \frac{2}{T} \int_0^{T/2} f(t) dt = \frac{4}{4} \left(\int_0^1 \cos \frac{\pi}{2} t dt + \int_1^2 0 dt \right) = \frac{2}{\pi}$$

$$a_n = \frac{4}{T} \int_0^{T/2} f(t) \cos n\omega_o t dt = \frac{4}{4} \left(\int_0^1 \cos \frac{\pi}{2} t \cos n \frac{\pi}{2} t dt + \int_1^2 0 \cdot \cos n\pi t dt \right) =$$

$$= \frac{1}{2} \left[\cos(a+b) - \cos(a-b) \right] = \frac{1}{2} \left(\int_0^1 \left[\cos \frac{\pi}{2}(n+1)t + \cos \frac{\pi}{2}(n-1)t \right] dt \right)$$

$$n=1 \rightarrow a_1 = \frac{1}{2} \left(\int_0^1 [\cos \pi t + 1] dt \right) = \frac{1}{2}$$

$$n > 1 \rightarrow a_n = \frac{1}{\pi(n+1)} \sin \frac{\pi}{2}(n+1) + \frac{1}{\pi(n-1)} \sin \frac{\pi}{2}(n-1)$$

$$n - neparno \rightarrow (n+1) i (n-1) su parni \rightarrow \sin \frac{\pi}{2}(n+1) = \sin \frac{\pi}{2}(n-1) = 0 \rightarrow a_n = 0$$

$$n - parno \rightarrow \sin \frac{\pi}{2}(n+1) = -\sin \frac{\pi}{2}(n-1) = (-1)^{\frac{n}{2}} \rightarrow a_n = \frac{(-1)^{\frac{n}{2}}}{\pi(n+1)} + \frac{-(-1)^{\frac{n}{2}}}{\pi(n-1)} = \frac{-2(-1)^{\frac{n}{2}}}{\pi(n^2-1)}$$

sada je funkcija

$$f(t) = \frac{1}{\pi} + \frac{1}{2} \cos \frac{\pi}{2} t - \frac{2}{\pi} \sum_{\substack{n=2 \\ n \text{ parno}}}^{\infty} \frac{(-1)^{\frac{n}{2}}}{(n^2-1)} \cos \frac{n\pi}{2} t \quad \text{gdje je } n=2,4,6,\dots$$

$$f(t) = \frac{1}{\pi} + \frac{1}{2} \cos \frac{\pi}{2} t - \frac{2}{\pi} \sum_{k=1}^{\infty} \frac{(-1)^k}{(4k^2-1)} \cos k\pi t \quad \text{gdje je } n=2k$$


FURIJEVA TRANSFORMACIJA

1. Naći Furijeovu transformaciju funkcije $f(t)=e^{-at}u(t)$, $a>0$ gdje je $u(t)=h(t)$ Hevisajdova funkcija.

$$F(j\omega) = \int_{-\infty}^{+\infty} e^{-at} u(t) e^{-j\omega t} dt = \int_0^{\infty} e^{-at} e^{-j\omega t} dt = \int_0^{\infty} e^{-(a+j\omega)t} dt = \frac{1}{-(a+j\omega)} e^{-(a+j\omega)t} \Big|_0^{\infty} = \frac{1}{a+j\omega}$$

2. Naći Furijeovu transformaciju pravougaonog impulsa definisanog kao:

$$f(t) = \begin{cases} A, & -\frac{\delta}{2} < t < \frac{\delta}{2} \\ 0, & |t| > \frac{\delta}{2} \end{cases}$$

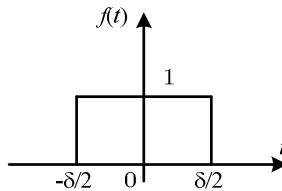


R

$$F(j\omega) = \int_{-\infty}^{+\infty} f(t) e^{-j\omega t} dt = \int_{-\frac{\delta}{2}}^{\frac{\delta}{2}} A e^{-j\omega t} dt = \frac{A}{-j\omega} e^{-j\omega t} \Big|_{-\frac{\delta}{2}}^{\frac{\delta}{2}} = \frac{2A}{j\omega} \frac{e^{j\omega\frac{\delta}{2}} - e^{-j\omega\frac{\delta}{2}}}{2} = \frac{2A}{\omega} \sin \omega \frac{\delta}{2}$$

jer se zna da važi

$$\frac{e^{j\omega t} - e^{-j\omega t}}{2} = \sin \omega t \quad \frac{e^{j\omega t} + e^{-j\omega t}}{2} = \cos \omega t$$

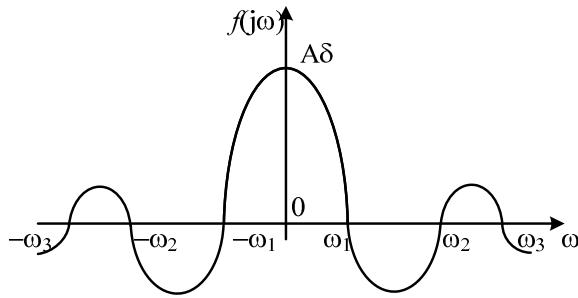Kao što se vidi, Furijeova transformacija je čisto realna, pa je moguće nacrtati njen grafik (spektar signala).




$$F(j\omega) = \frac{2A}{\omega} \sin \frac{\omega\delta}{2} = 2A \frac{\delta}{2} \frac{\sin \frac{\omega\delta}{2}}{\frac{\omega\delta}{2}} = A\delta \frac{\sin \frac{\omega\delta}{2}}{\frac{\omega\delta}{2}}$$

$$\omega_1 = \frac{2\pi}{\delta} \quad \omega_2 = \frac{4\pi}{\delta} \quad \omega_3 = \frac{6\pi}{\delta}$$

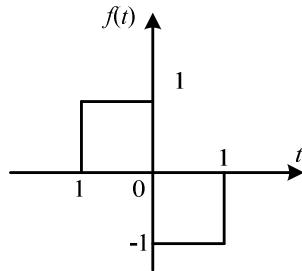3. Naći FT ako je

$$f(t) = \begin{cases} 1, & -1 < t < 0 \\ -1, & 0 < t < 1 \\ 0, & \text{ostalo } t \end{cases}$$



R

$$\begin{aligned} F(j\omega) &= \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt = \int_{-1}^0 e^{-j\omega t} dt - \int_0^1 e^{-j\omega t} dt = \frac{1}{-j\omega} e^{-j\omega t} \Big|_{-1}^0 - \frac{1}{-j\omega} e^{-j\omega t} \Big|_0^1 = \\ &= \frac{1}{-j\omega} (1 - e^{j\omega}) - \frac{1}{-j\omega} (e^{-j\omega} - 1) = 2 \frac{j}{\omega} (2 - (e^{j\omega} + e^{-j\omega})) = \frac{4j}{\omega} (1 - \cos \omega) \end{aligned}$$

4. Naći Furijeovu transformaciju funkcije $f(t) = e^{-a|t|}$, $a > 0$

R

$$|t| = \begin{cases} t, & t > 0 \\ -t, & t < 0 \end{cases}$$

$$F(j\omega) = \int_{-\infty}^0 e^{at} e^{-j\omega t} dt + \int_0^{+\infty} e^{-at} e^{-j\omega t} dt = \frac{2a}{a^2 + \omega^2}$$

5. Naći $f(t)$ ako je $F(j\omega) = \begin{cases} 1, & -1 < \omega < 1 \\ 0, & |\omega| > 1 \end{cases}$

R

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} F(j\omega) e^{j\omega t} d\omega = \frac{1}{2\pi} \int_{-1}^1 1 \cdot e^{j\omega t} d\omega = \frac{1}{2\pi} \frac{1}{jt} e^{j\omega t} \Big|_{-1}^1 = \frac{1}{2\pi} \frac{1}{jt} (e^{jt} - e^{-jt}) = \frac{1}{\pi} \frac{\sin t}{t}$$