

Vježbe III

Bulova algebra

$$\begin{array}{ll} A + 0 = A & A \times 0 = 0 \\ A + 1 = 1 & A \times 1 = A \\ A + A = A & A \times A = A \\ A + \bar{A} = 1 & A \times \bar{A} = 0 \end{array}$$





$$\overline{\overline{A}} = A$$

De Morganova teorema


$$\overline{A+B} = \bar{A} \times \bar{B}$$

$$\overline{A \times B} = \bar{A} + \bar{B}$$

Logički elementi

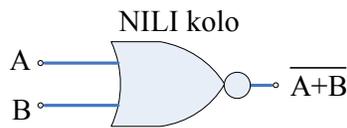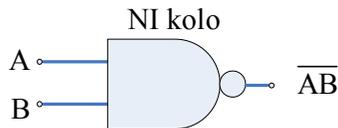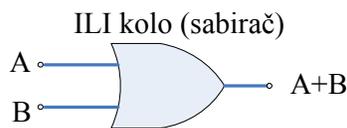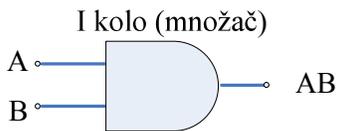

INVERTOR

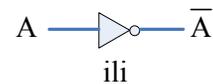

ili



napomena

Oznake za inverter su ekvivalentne i mogu se ravnopravno koristiti

1. Koristeći pravila Bulove algebre uprostiti izraze:

a) $AB + \bar{A}B$ b) $A+B+\bar{A}\bar{B}$ c) $\bar{A}\bar{C} \times \bar{A}\bar{B}\bar{C}$ d) $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$

a) $AB + \bar{A}B = B(A + \bar{A}) = B$



b) $A+B+\bar{A}\bar{B} = A+B+\bar{A}+\bar{B} = 1$



c) $\bar{A}\bar{C} \times \bar{A}\bar{B}\bar{C} = (\bar{A} + \bar{C}) \times (A + \bar{B} + \bar{C}) = \bar{A}A + \bar{A}\bar{B} + \bar{A}\bar{C} + A\bar{C} + \bar{C}\bar{B} + \bar{C}\bar{C} = \bar{A}\bar{B} + \bar{A}\bar{C} + A\bar{C} + \bar{C}\bar{B} + \bar{C} = \bar{A}\bar{B} + \bar{C}(\bar{A} + A + \bar{B} + 1) = \bar{A}\bar{B} + \bar{C}$

d) $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC = \bar{A}\bar{B}(C + \bar{C}) + \bar{A}B(C + \bar{C}) = \bar{A}\bar{B} + \bar{A}B = \bar{A}(\bar{B} + B) = \bar{A}$

2. Nacrtati šeme realizacije izraza:

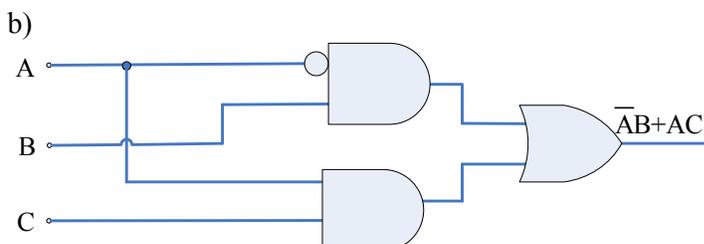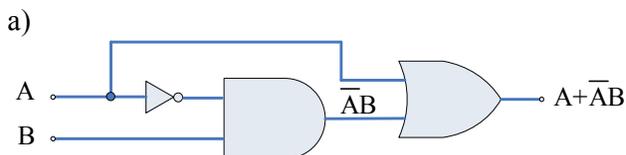
a) $A + \bar{A}B$ b) $\bar{A}B + AC$ c) $(A+B)(\bar{A}+C)$ d) $BC + ABD + A\bar{C}$



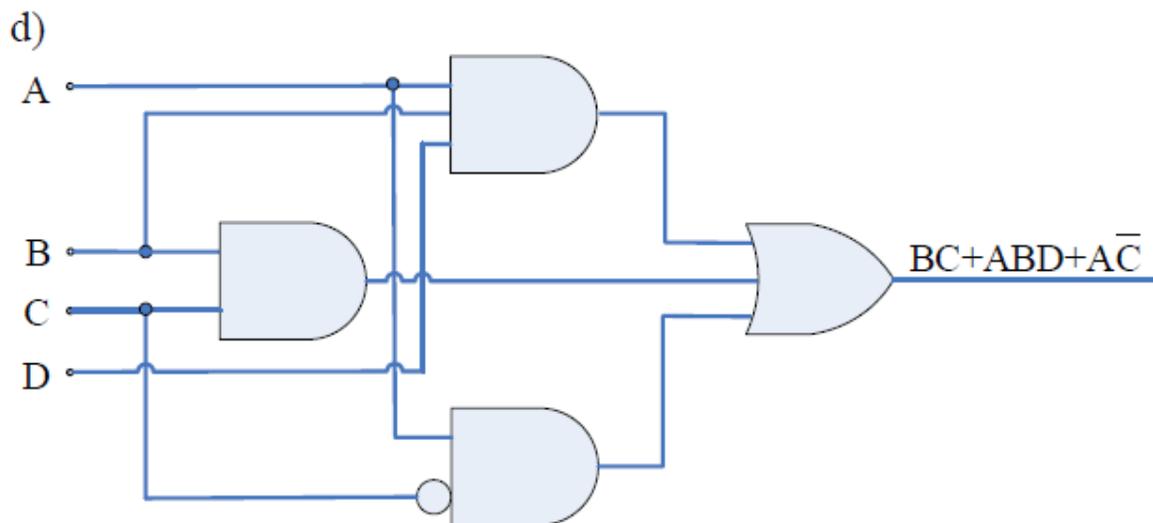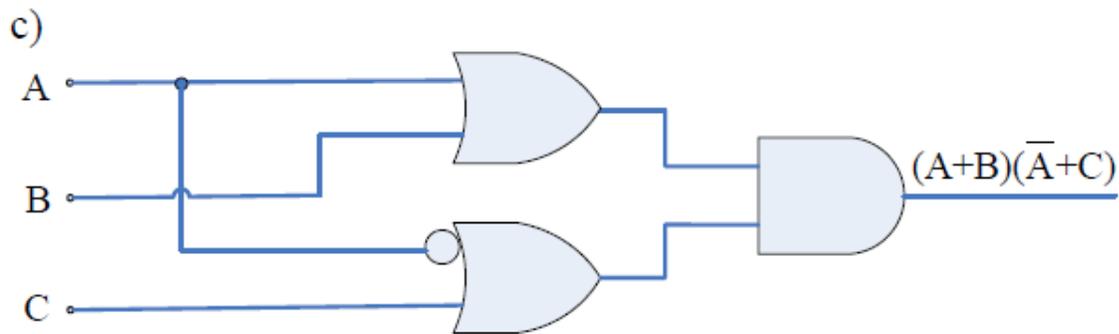

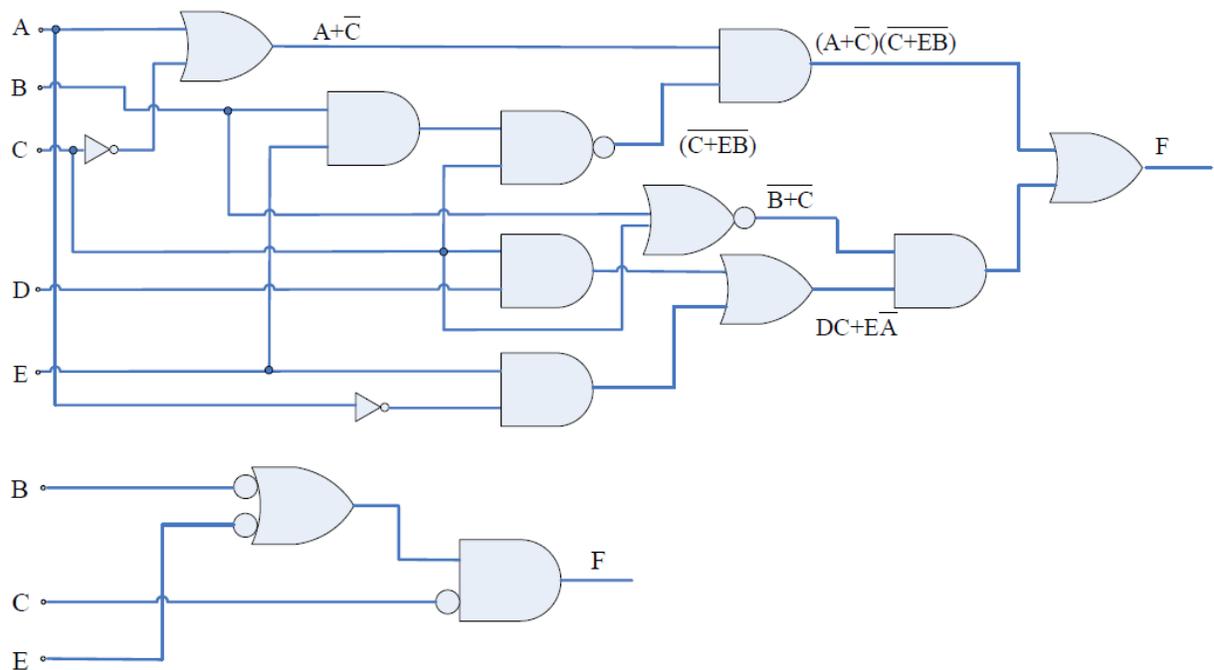3. Uprostiti, a zatim realizovati originalnu i uporšćenu funkciju.

$$\begin{aligned}
 F &= (A + \bar{C})(\overline{C + EB}) + (DC + E\bar{A})(\overline{B + C}) = (A + \bar{C})\bar{C}\bar{E}\bar{B} + (DC + E\bar{A})\bar{B}\bar{C} = (A + \bar{C})\bar{C}(\bar{E} + \bar{B}) + DC\bar{B}\bar{C} + E\bar{A}\bar{B}\bar{C} \\
 &= (\bar{A}\bar{C} + \bar{C}\bar{C})(\bar{E} + \bar{B}) + E\bar{A}\bar{B}\bar{C} = (\bar{A}\bar{C} + \bar{C})(\bar{E} + \bar{B}) + E\bar{A}\bar{B}\bar{C} = \bar{C}(A + 1)(\bar{E} + \bar{B}) + E\bar{A}\bar{B}\bar{C} = \bar{C}(\bar{E} + \bar{B}) + E\bar{A}\bar{B}\bar{C} \\
 &= \bar{C}\bar{E} + \bar{C}\bar{B} + E\bar{A}\bar{B}\bar{C} = \bar{C}\bar{E} + \bar{C}\bar{B}(1 + E\bar{A}) = \bar{C}\bar{E} + \bar{C}\bar{B} = \bar{C}(\bar{E} + \bar{B})
 \end{aligned}$$



4. Koristeći pravila Bulove algebre dokazati identitet $A \times \overline{AB} + B(\overline{A \times B}) = A$ i nacrtati obje šeme realizacije.

$$A \times \overline{AB} + B(\overline{A \times B}) = A \times (\overline{A} + \overline{B}) + B(A + \overline{B}) = A\overline{A} + A\overline{B} + AB + B\overline{B} = A(\overline{B} + B) = A$$

