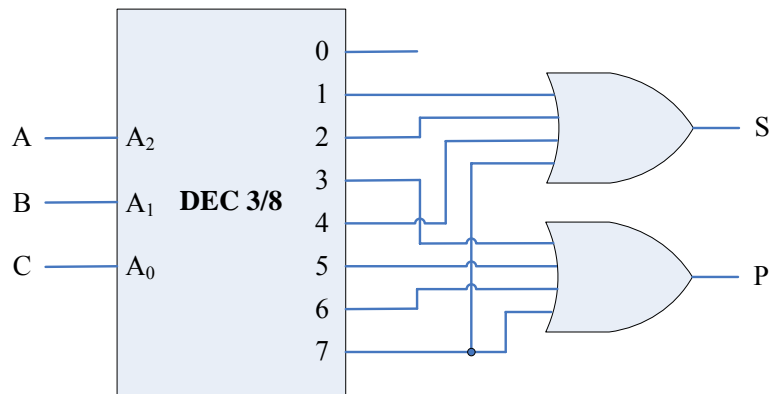


## Vježbe VI

### Dekoder

1. Realizovati potpuni sabirač koristeći dekodec DEC 3/8.

i	A	B	C	S	P
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1




$$S = \Sigma(1, 2, 4, 7); P = \Sigma(3, 5, 6, 7)$$

2. Realizovati funkciju  $F = \overline{A}BC + \overline{B}$  koristeći dekodec DEC 3/8.

$$F = \overline{A}BC + \overline{B} = \overline{A}BC + \overline{B}(A + \overline{A})(C + \overline{C}) = \overline{A}BC + \overline{B}(AC + A\overline{C} + \overline{A}C + \overline{A}\overline{C}) = \overline{A}BC + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} = \Sigma(0, 1, 3, 4, 5)$$

i	A	B	C	$\overline{\overline{A}BC}$
0	0	0	0	← $\overline{\overline{A}BC}$
1	0	0	1	← $\overline{\overline{A}BC}$
2	0	1	0	$\overline{\overline{A}BC}$
3	0	1	1	← $\overline{\overline{A}BC}$
4	1	0	0	← $\overline{\overline{A}BC}$
5	1	0	1	← $\overline{\overline{A}BC}$
6	1	1	0	$\overline{\overline{A}BC}$
7	1	1	1	$\overline{\overline{A}BC}$

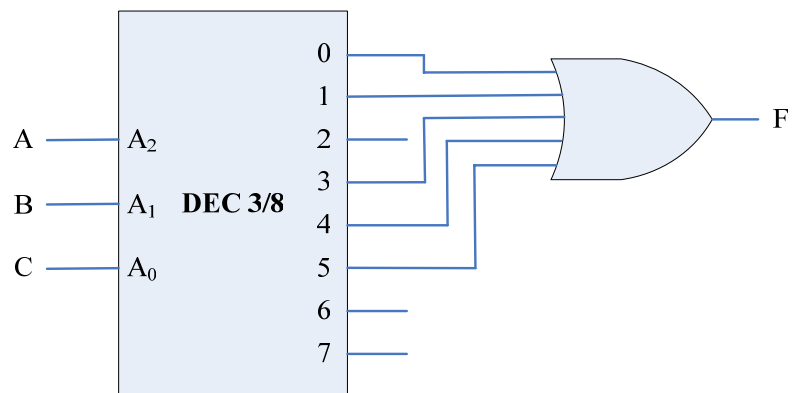

3. Realizovati i nacrtati kolo dekodera DEC 4/16 upotrebljavajući isključivo dekodere DEC 3/8 sa ENABLE priključkom.

