

## Vježbe III





### Bulova algebra

$$\begin{aligned}
 A + 0 &= A & A \times 0 &= 0 \\
 A + 1 &= 1 & A \times 1 &= A \\
 A + A &= A & A \times A &= A \\
 A + \bar{A} &= 1 & A \times \bar{A} &= 0 \\
 \bar{\bar{A}} &= A
 \end{aligned}$$

### De Morganova teorema

$$\begin{aligned}
 \overline{A+B} &= \bar{A} \times \bar{B} \\
 \overline{A \times B} &= \bar{A} + \bar{B}
 \end{aligned}$$

### Logički elementi

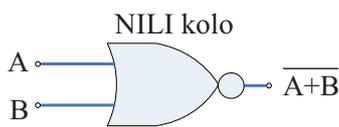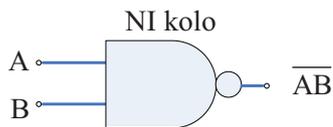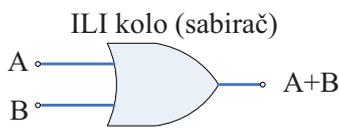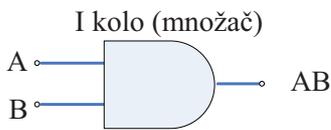

### INVERTOR



ili



\*\*\*napomena\*\*\*

Oznake za invertor su ekvivalentne i mogu se ravnopravno koristiti

1. Koristeći pravila Bulove algebre uprostiti izraze:

a)  $AB + \bar{A}B$       b)  $A+B+\bar{A}B$       c)  $\bar{A}C \times \bar{A}BC$       d)  $\bar{A}BC + \bar{A}BC + \bar{A}BC + \bar{A}BC$

a)  $AB + \bar{A}B = B(A + \bar{A}) = B$



b)  $A+B+\bar{A}B = A+B+\bar{A}B = 1$



c)  $\bar{A}C \times \bar{A}BC = (\bar{A} + C) \times (A + B + C) = \bar{A}A + \bar{A}B + \bar{A}C + AC + CB + CC = \bar{A}B + \bar{A}C + AC + CB + C = \bar{A}B + C(A + A + B + 1) = \bar{A}B + C$

d)  $\bar{A}BC + \bar{A}BC + \bar{A}BC + \bar{A}BC = \bar{A}B(C + C) + \bar{A}B(C + C) = \bar{A}B + \bar{A}B = \bar{A}(B + B) = \bar{A}$

2. Nacrtati šeme realizacije izraza:

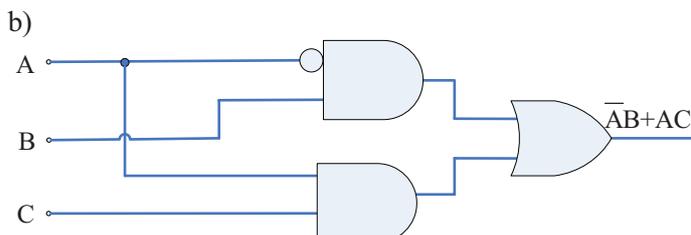
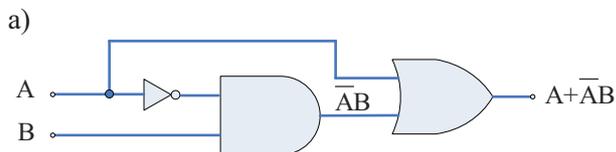
a)  $A + \bar{A}B$       b)  $\bar{A}B + AC$       c)  $(A+B)(\bar{A}+C)$       d)  $BC + ABD + \bar{A}C$



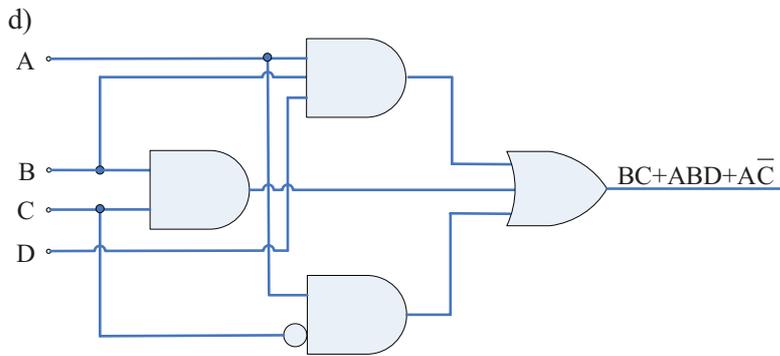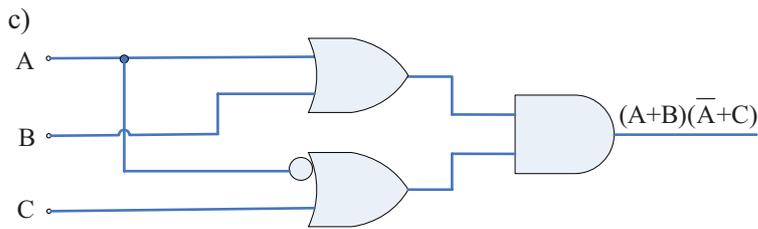

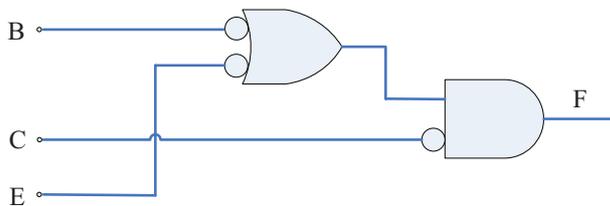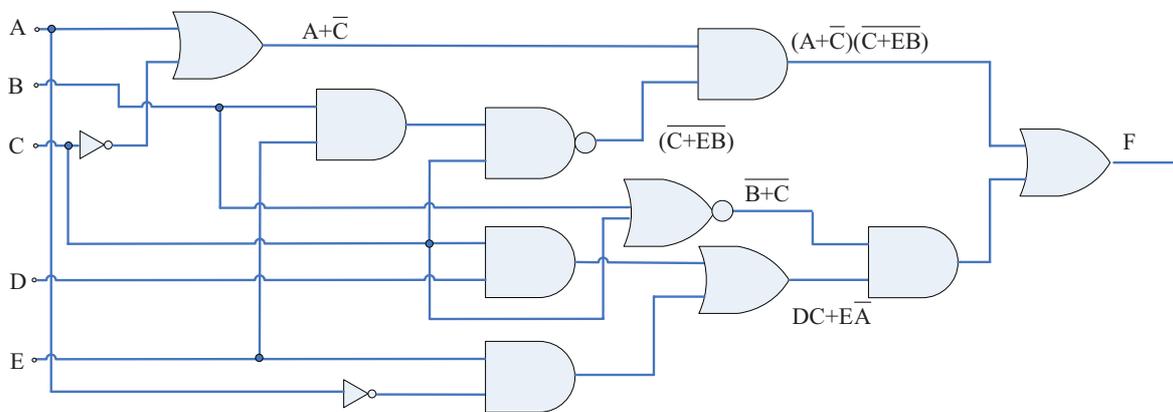
3. Uprostiti, a zatim realizovati originalnu i uprošćenu funkciju.

$$\begin{aligned}
 F &= (A+\bar{C})(\overline{C+EB})+(DC+E\bar{A})(\overline{B+C})=(A+\bar{C})\bar{C}\bar{E}\bar{B}+(DC+E\bar{A})\bar{B}\bar{C} = \\
 &= (A+\bar{C})\bar{C}(\bar{E}+\bar{B})+\bar{B}\bar{C}DC+\bar{B}\bar{C}E\bar{A} = (A\bar{C}+\bar{C}\bar{C})(\bar{E}+\bar{B})+\bar{B}\bar{C}E\bar{A} = \\
 &= \bar{C}(A+1)(\bar{E}+\bar{B})+\bar{B}\bar{C}E\bar{A} = \bar{C}(\bar{E}+\bar{B})+\bar{B}\bar{C}E\bar{A} = \bar{C}\bar{E}+\bar{C}\bar{B}+\bar{B}\bar{C}E\bar{A} = \\
 &= \bar{C}\bar{E}+\bar{B}\bar{C}(1+E\bar{A}) = \bar{C}\bar{E}+\bar{B}\bar{C} = \bar{C}(\bar{E}+\bar{B})
 \end{aligned}$$



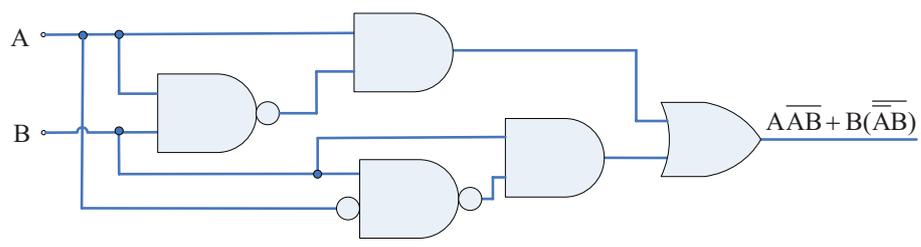4. Koristeći pravila Bulove algebre dokazati identitet  $A \times \overline{AB} + B(\overline{A \times B}) = A$  i nacrtati obje šeme realizacije.

$$A \times \overline{AB} + B(\overline{A \times B}) = A \times (\bar{A} + \bar{B}) + B(A + \bar{B}) = A\bar{A} + A\bar{B} + AB + B\bar{B} = A(\bar{B} + B) = A$$



A —