


# VJEŽBE 3

OSNOVE ELEKTRONIKE, ETR, IV SEMESTAR


DOC. DR MILENA ERCEG
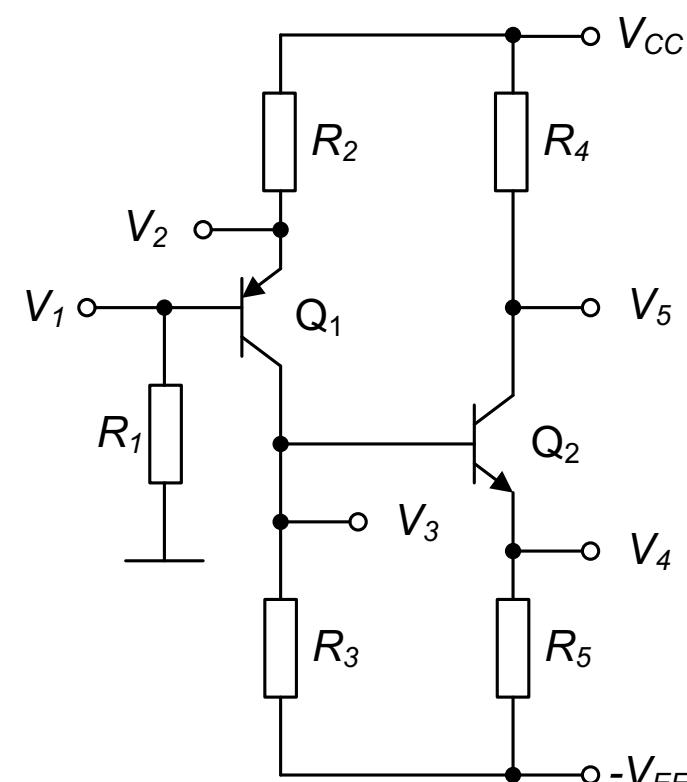
### ZADATAK 1

Za kolo prikazano na slici odrediti vrijednosti napona  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$  i  $V_5$ . Poznato je:  $V_{CC} = V_{EE} = 10$  V,  $V_{EB1} = V_{BE2} = 0.7$  V,  $V_{ECS1} = V_{CES2} = 0.2$  V,  $\beta = 100$ ,  $R_I = 100$  k $\Omega$ ,  $R_2 = 9.1$  k $\Omega$ ,  $R_3 = 9.1$  k $\Omega$ ,  $R_4 = 5.1$  k $\Omega$  i  $R_5 = 4.3$  k $\Omega$ .



## ZADATAK 1

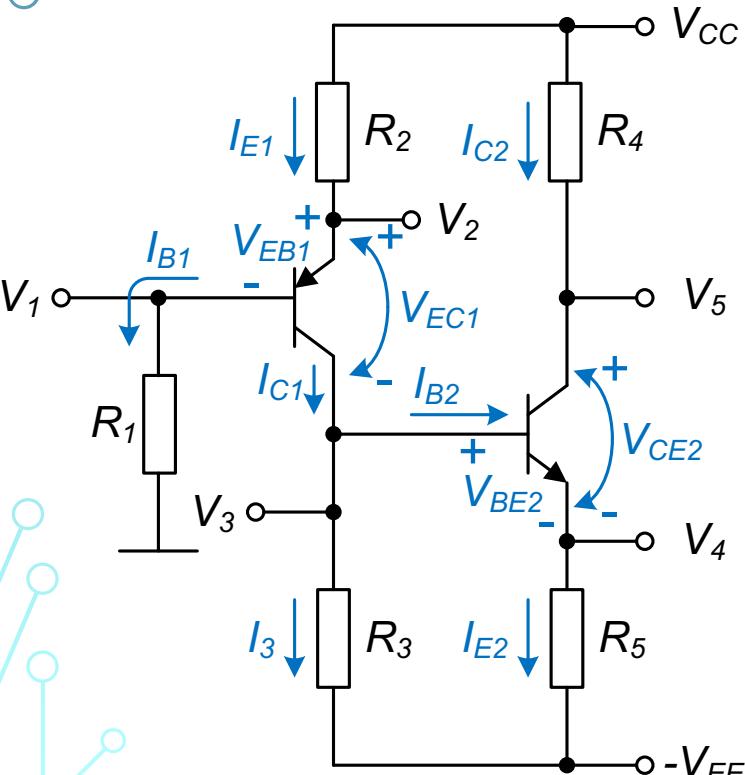

$$V_{CC} - R_2 I_{E1} - V_{EB1} - R_1 I_{B1} = 0$$

$$V_{CC} - R_2(\beta + 1) I_{B1} - V_{EB1} - R_1 I_{B1} = 0$$

$$I_{B1} = \frac{V_{CC} - V_{EB1}}{(\beta + 1)R_2 + R_1} = 9.125 \mu\text{A}$$

$$I_{C1} = \beta I_{B1} = 0.913 \text{ mA}$$

$$I_{E1} = (\beta + 1) I_{B1} = 0.922 \text{ mA}$$


$$V_{BE2} + R_5 I_{E2} - R_3 I_3 = 0$$

$$V_{BE2} + R_5(\beta + 1) I_{B2} - R_3(I_{C1} - I_{B2}) = 0$$

$$V_{BE2} - R_3 I_{C1} + [(\beta + 1)R_5 + R_3] I_{B2} = 0$$

$$I_{B2} = \frac{-V_{BE2} + R_3 I_{C1}}{(\beta + 1)R_5 + R_3} = 17.14 \mu\text{A}$$

## ZADATAK 1

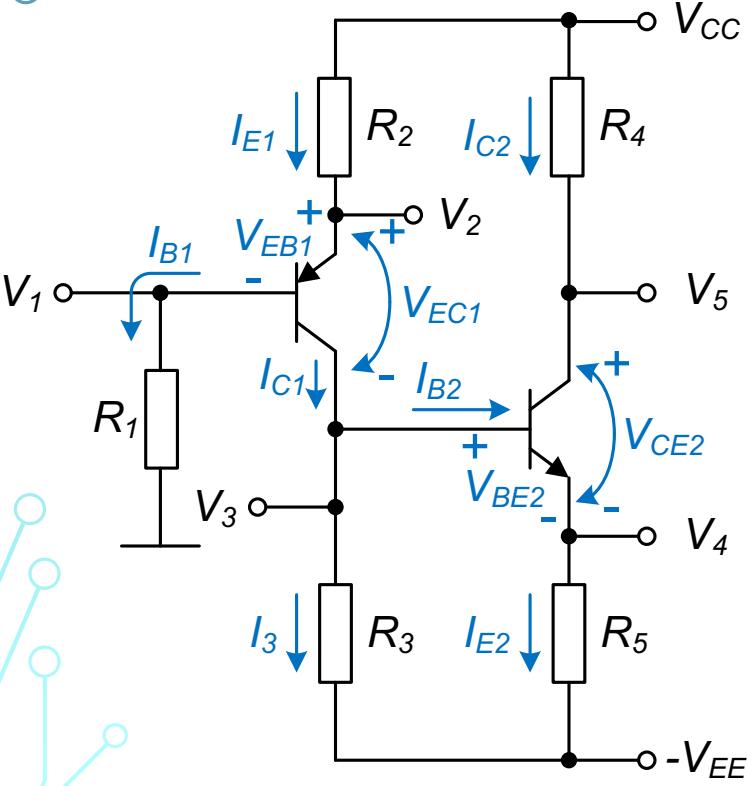

$$I_{C2} = \beta I_{B2} = 1.714 \text{ mA}$$

$$I_{E2} = (\beta + 1)I_{B2} = 1.732 \text{ mA}$$

$$V_{EC1} = V_{CC} - R_2 I_{E1} - R_3 I_3 + V_{EE} = 3.466 \text{ V} > V_{ECS1} = 0.2 \text{ V}$$

$$V_{CE2} = V_{CC} - R_4 I_{C2} - R_5 I_{E2} + V_{EE} = 3.811 \text{ V} > V_{CES2} = 0.2 \text{ V}$$

Slijedi da je pretpostavka o DAR-u tačna.

$$V_1 = R_1 I_{B1} = 0.913 \text{ V}$$

$$V_2 = V_{CC} - R_2 I_{E1} = 1.613 \text{ V}$$


$$V_3 = -V_{EE} + R_3 I_3 = -1.853 \text{ V}$$

$$V_4 = -V_{EE} + R_5 I_{E2} = -2.552 \text{ V}$$

$$V_5 = V_{CC} - R_4 I_{C2} = 1.259 \text{ V}$$

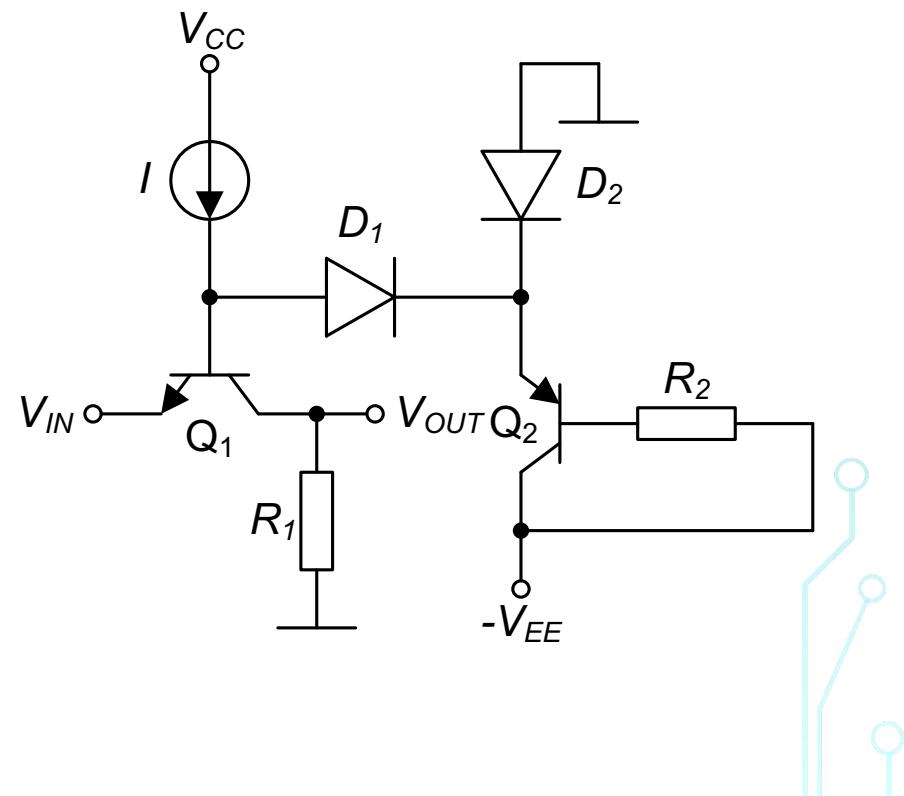
## ZADATAK 2

Za kolo prikazano na slici 3 odrediti zavisnost izlaznog napona  $V_{OUT}$  od ulaznog napona  $V_{IN}$ , za opseg ulaznog napna –  $V_{EE} < V_{IN} < V_{CC}$ . Poznato je:  $V_{CC}=V_{EE}=3.3$  V,  $V_{DI}=V_{D2}=0.7$  V,  $V_{BE1}=V_{EB2}=0.7$  V,  $V_{CES1}=V_{ECS2}=0.2$  V,  $\beta_1=\beta_2=\beta=100$ ,  $R_I=2$  k $\Omega$ ,  $R_2=100$  k $\Omega$ ,  $I=10$   $\mu$ A.


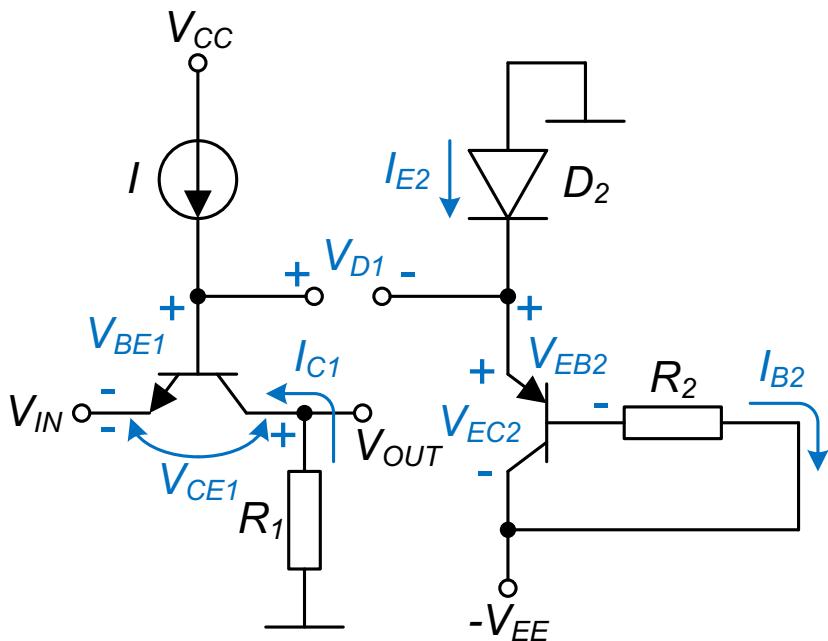
## ZADATAK 2

1° Uvodi se pretpostavka da su oba BJT-a u DAR-u, dioda D<sub>1</sub> ne provodi, dok dioda D<sub>2</sub> provodi.



$$V_{OUT} = -R_1 I_{C1} = -R_1 \beta I = -2 \text{ V}$$

$$V_{CE1} = V_{OUT} - V_{IN} > V_{CES1}$$

$$V_{IN} < V_{OUT} - V_{CES1} = -2.2 \text{ V}$$

$$V_{D1} = V_{IN} + V_{BE1} + E_{D2} < E_{D1}$$

$$V_{IN} < E_{D1} - V_{BE1} - E_{D2} = -0.7 \text{ V}$$


$$I_{B2} = \frac{-E_{D2} - V_{EB2} + V_{EE}}{R_2} = 19 \mu\text{A}$$

$$I_{D2} = (\beta + 1)I_{B2} = 1.919 \text{ mA} > 0$$

$$V_{EC2} = -V_{D2} + V_{EE} = 2.6 \text{ V}$$
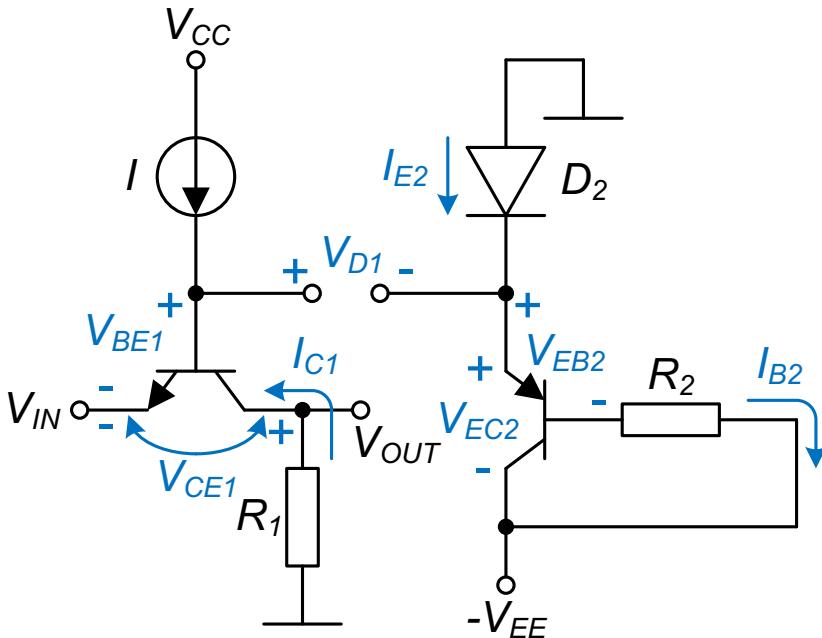
## ZADATAK 2

2<sup>o</sup> Uvodi se pretpostavka da je BJT Q<sub>1</sub> u zasićenju, BJT Q<sub>2</sub> u DAR-u, dioda D<sub>1</sub> ne provodi, dok dioda D<sub>2</sub> provodi.



$$V_{OUT} = V_{IN} + V_{CES1}$$

$$I_{C1} = -\frac{V_{OUT}}{R_1} = -\frac{V_{IN} + V_{CES1}}{R_1} < \beta I$$

$$V_{IN} > -\beta IR_1 - V_{CES1} = -2.2 \text{ V}$$


$$V_{D1} = V_{IN} + V_{BE1} + E_{D2} < E_{D1}$$

$$V_{IN} < E_{D1} - V_{BE1} - E_{D2} = -0.7 \text{ V}$$

$$-2.2 \text{ V} < V_{IN} < -0.7 \text{ V}$$
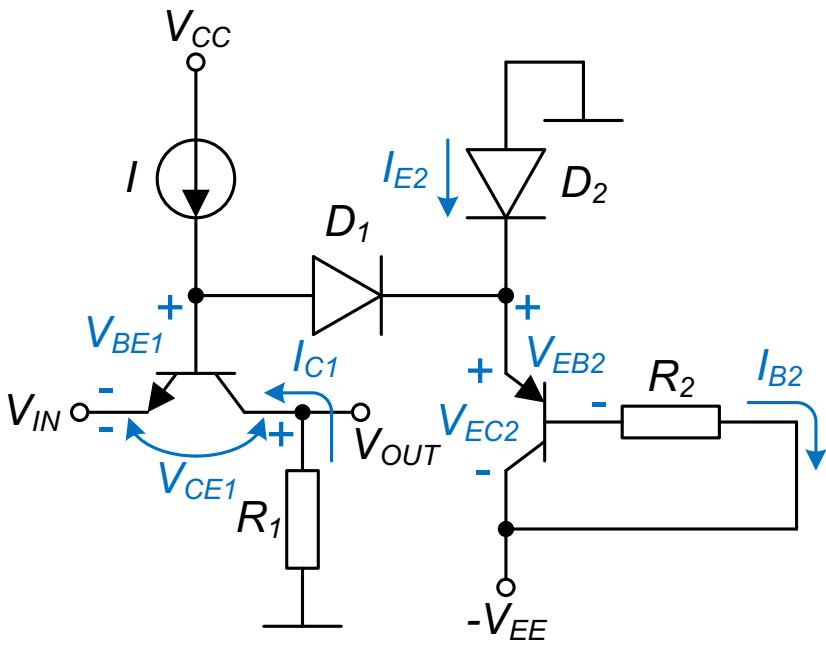
## ZADATAK 2

3º Uvodi se pretpostavka da je BJT Q<sub>1</sub> u zasićenju, BJT Q<sub>2</sub> u DAR-u, i obje diode provode.



$$V_{OUT} = V_{IN} + V_{CES1}$$


$$V_{IN} + V_{BE1} - E_{D1} + E_{D2} = 0$$

$$V_{IN} = -0.7 \text{ V}$$

$$V_{OUT} = -0.5 \text{ V}$$
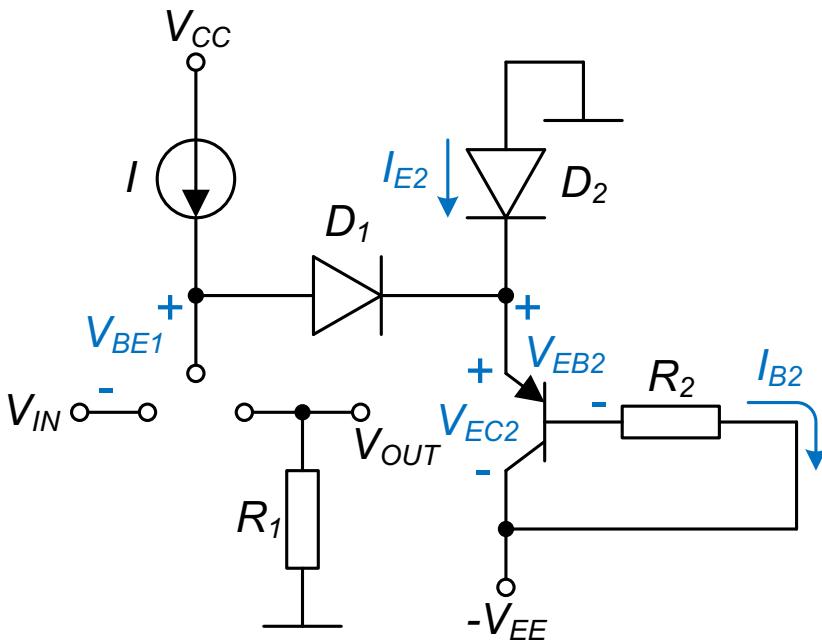
## ZADATAK 2

4º Uvodi se pretpostavka da je BJT Q<sub>1</sub> zakočen, BJT Q<sub>2</sub> u DAR-u, i obje diode provode.



$$V_{OUT} = 0 \text{ V}$$


$$V_{BE1} = E_{D1} - E_{D2} - V_{IN} < 0.7 \text{ V}$$

$$V_{IN} > -0.7 \text{ V}$$

$$I_{D1} = I > 0$$

$$I_{D2} = (\beta + 1)I_{B2} - I_{D1} = 1.909 \text{ mA} > 0$$

## ZADATAK 2

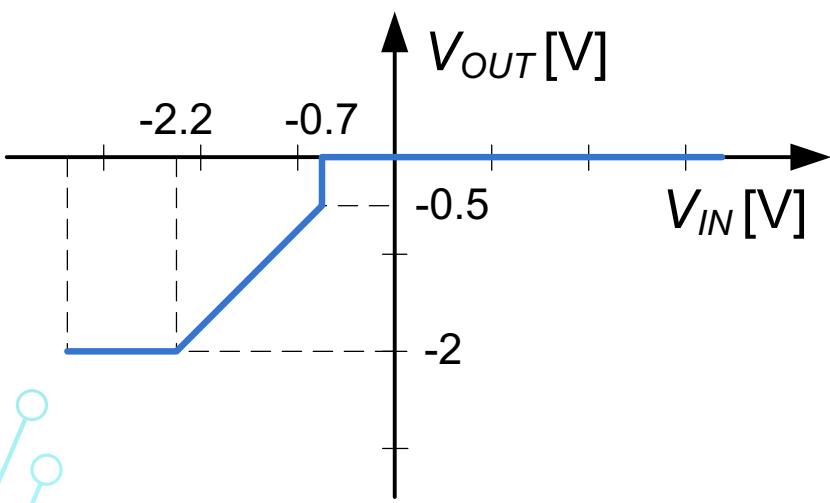

$$V_{IN} < -2.2 \text{ V: } V_{OUT} = -2 \text{ V}$$


$$-2.2 \text{ V} < V_{IN} < -0.7 \text{ V: } V_{OUT} = V_{IN} + V_{CES1}$$

$$V_{IN} = -0.7 \text{ V: } V_{OUT} = -0.5 \text{ V}$$

$$V_{IN} > -0.7 \text{ V: } V_{OUT} = 0 \text{ V}$$

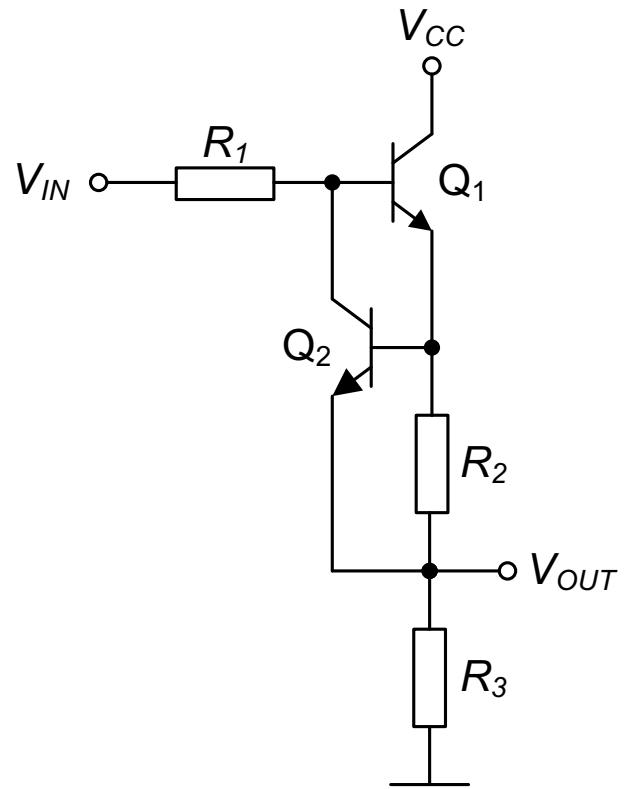
## ZADATAK 2

Za kolo prikazano na slici odrediti zavisnost izlaznog napona  $V_{OUT}$  od ulaznog napona  $V_{IN}$ , za opseg ulaznog napna  $0 < V_{IN} < V_{CC}$ . Poznato je:  
 $V_{CC}=10 \text{ V}$ ,  $V_{BE1}=V_{BE2}=0.7 \text{ V}$ ,  
 $V_{CES1}=V_{CES2}=0.2 \text{ V}$ ,  $\beta_1=\beta_2=\beta=99$ ,  
 $R_1=5 \text{ k}\Omega$ ,  $R_2=200 \Omega$  i  $R_3=1.6 \text{ k}\Omega$ .


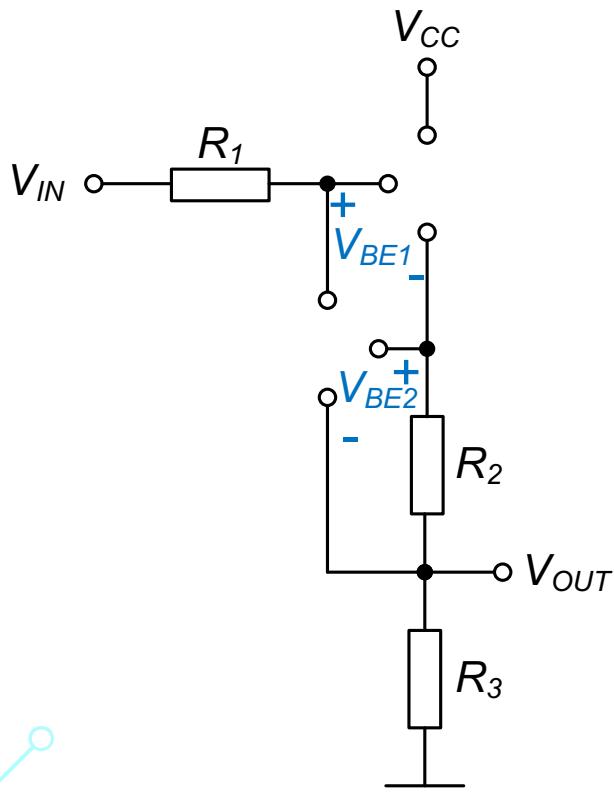
### ZADATAK 3

1° Uvodi se pretpostavka da su oba BJT-a zakočena.




$$V_{OUT} = 0$$

$$V_{BE1} = V_{IN} < 0.7 \text{ V}$$

$$V_{BE2} = 0 \text{ V}$$
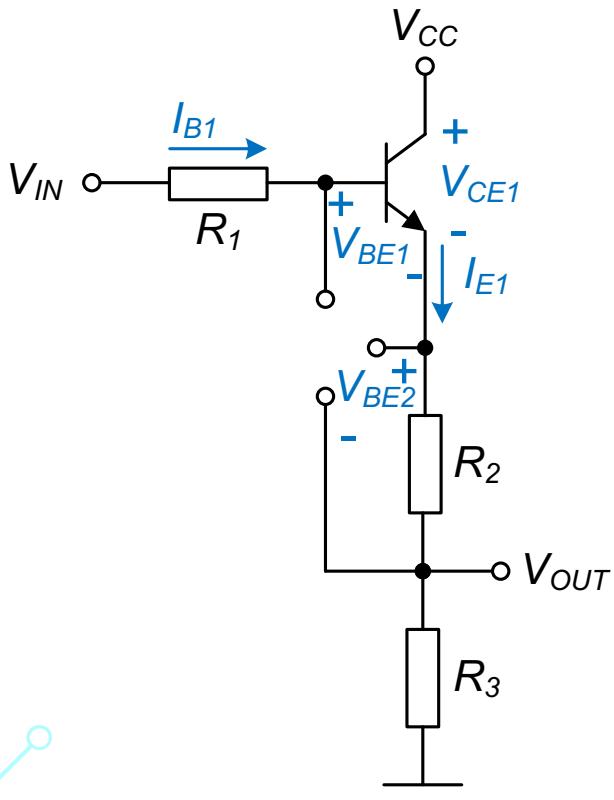
### ZADATAK 3

2º Uvodi se pretpostavka da BJT Q<sub>1</sub> provodi u DAR-u, dok je Q<sub>2</sub> zakočen.



$$V_{IN} - R_1 I_{B1} - V_{BE1} - (R_2 + R_3) I_{E1} = 0$$

$$V_{IN} - R_1 I_{B1} - V_{BE1} - (R_2 + R_3)(\beta + 1) I_{B1} = 0$$

$$I_{B1} = \frac{V_{IN} - V_{BE1}}{R_1 + (R_2 + R_3)(\beta + 1)} > 0$$


$$V_{IN} > V_{BE1}$$

$$V_{OUT} = R_3 I_{E1} = R_3 (\beta + 1) \frac{V_{IN} - V_{BE1}}{R_1 + (R_2 + R_3)(\beta + 1)}$$

$$V_{OUT} = \frac{R_3 (\beta + 1)}{R_1 + (R_2 + R_3)(\beta + 1)} (V_{IN} - V_{BE1})$$
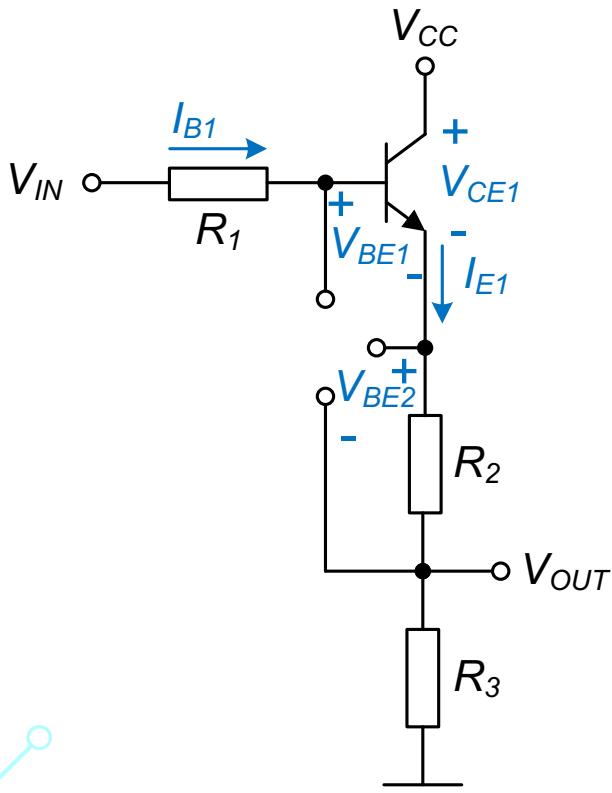
### ZADATAK 3

2º Uvodi se pretpostavka da BJT Q<sub>1</sub> provodi u DAR-u, dok je Q<sub>2</sub> zakočen.



$$V_{OUT} = 0.865(V_{IN} - V_{BE1})$$

$$V_{CE1} = V_{CC} - (R_2 + R_3)(\beta + 1)I_{B1}$$


$$= V_{CC} - (R_2 + R_3)(\beta + 1) \frac{V_{IN} - V_{BE1}}{R_1 + (R_2 + R_3)(\beta + 1)} > V_{CES1}$$

$$\frac{V_{IN} - V_{BE1}}{R_1 + (R_2 + R_3)(\beta + 1)} < \frac{V_{CC} - V_{CES1}}{(R_2 + R_3)(\beta + 1)}$$

$$V_{IN} < \frac{R_1 + (R_2 + R_3)(\beta + 1)}{(R_2 + R_3)(\beta + 1)} (V_{CC} - V_{CES1}) + V_{BE1} = 10.77 \text{ V}$$
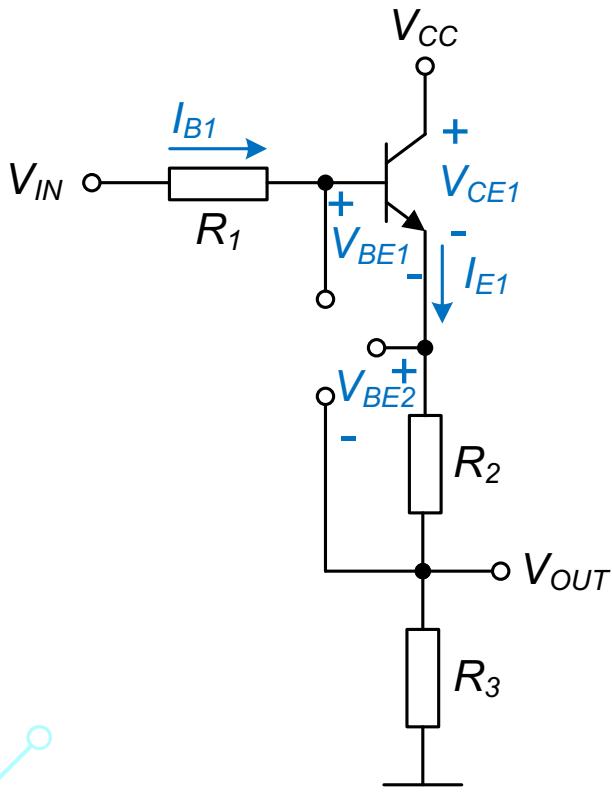
### ZADATAK 3

2º Uvodi se pretpostavka da BJT Q<sub>1</sub> provodi u DAR-u, dok je Q<sub>2</sub> zakočen.




$$V_{BE2} = R_2(\beta + 1)I_{B1} = R_2(\beta + 1) \frac{V_{IN} - V_{BE1}}{R_1 + (R_2 + R_3)(\beta + 1)} < 0.7 \text{ V}$$

$$V_{IN} < \frac{R_1 + (R_2 + R_3)(\beta + 1)}{R_2(\beta + 1)} 0.7 \text{ V} + V_{BE1} = 7.175 \text{ V}$$

$$V_{OUT}(V_{IN} = 7.175 \text{ V}) = 5.6 \text{ V}$$
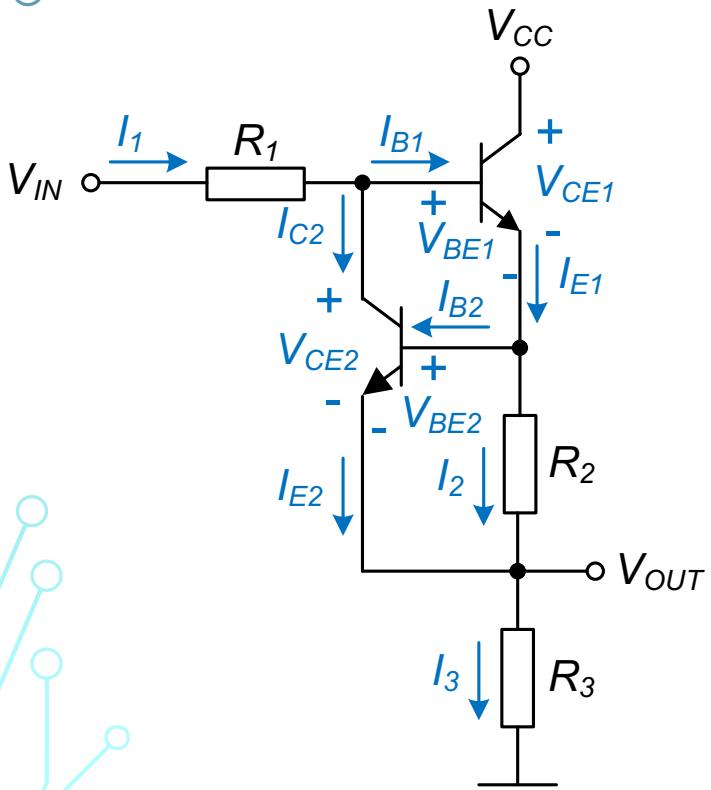
### ZADATAK 3

3º Uvodi se pretpostavka da su oba BJT-a u DAR-u.



$$V_{OUT} = R_3 I_3$$

$$I_3 = I_{E2} + I_2$$

$$I_2 = \frac{V_{BE2}}{R_2} = 3.5 \text{ mA}$$

$$I_{E2} = (\beta + 1) I_{B2}$$


$$I_{B2} = I_{E1} - I_2$$

$$I_{E1} = (\beta + 1) I_{B1}$$

$$I_{B1} = I_1 - I_{C2} = I_1 - \beta I_{B2} = I_1 - \beta(I_{E1} - I_2)$$
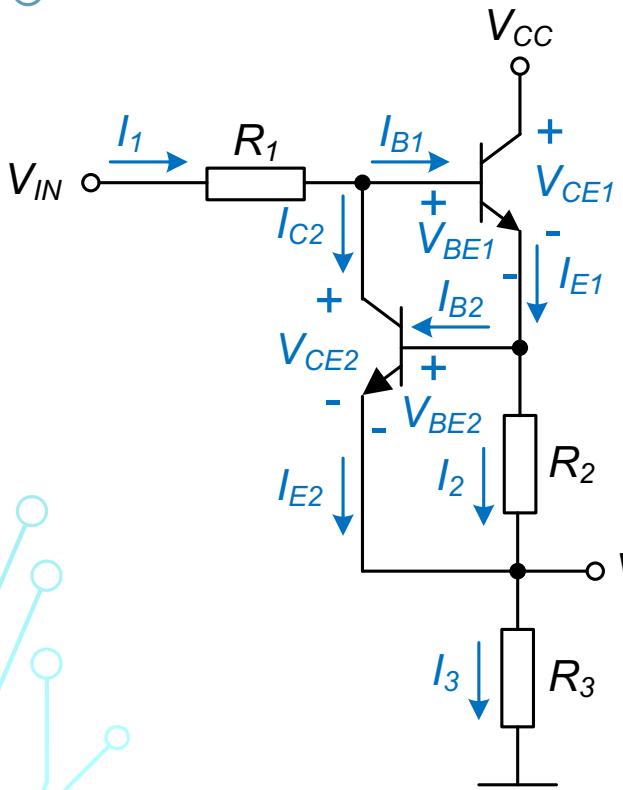
### ZADATAK 3

3º Uvodi se pretpostavka da su oba BJT-a u DAR-u.



$$I_{B1} = I_1 - I_{C2} = I_1 - \beta I_{B2} = I_1 - \beta(I_{E1} - I_2)$$

$$[1 + \beta(\beta + 1)]I_{B1} = I_1 + \beta I_2$$

$$I_{B1} = \frac{I_1 + \beta I_2}{1 + \beta(\beta + 1)}$$

$$I_1 = \frac{V_{IN} - V_{BE1} - V_{BE2} - V_{OUT}}{R_1}$$


$$V_{OUT} = R_3(I_{E2} + I_2) = R_3[(\beta + 1)I_{B2} + I_2] = R_3[(\beta + 1)(I_{E1} - I_2) + I_2]$$

$$V_{OUT} = R_3\{(\beta + 1)[(\beta + 1)I_{B1} - I_2] + I_2\}$$

$$V_{OUT} = R_3 \left\{ (\beta + 1) \left[ (\beta + 1) \frac{I_1 + \beta I_2}{1 + \beta(\beta + 1)} - I_2 \right] + I_2 \right\}$$
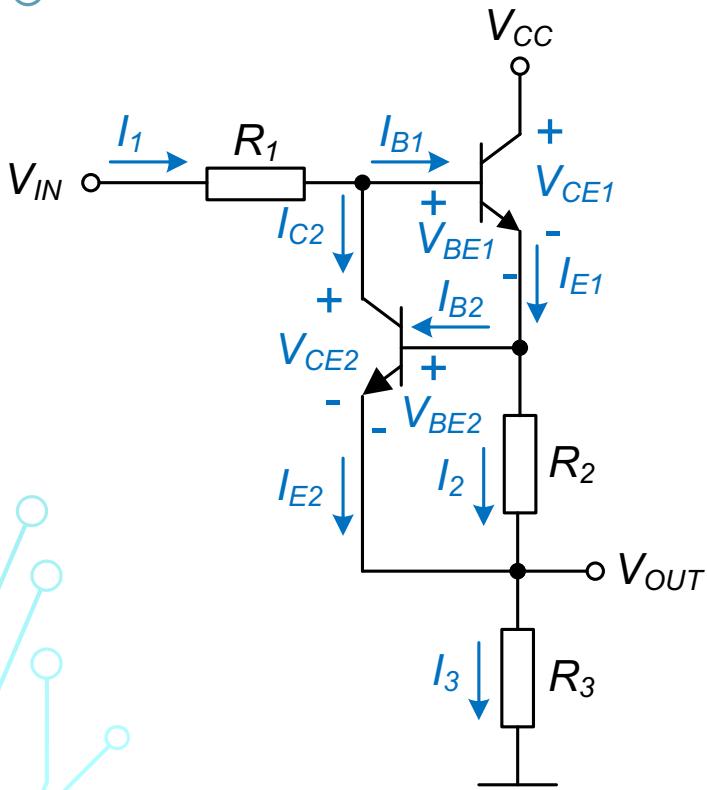
### ZADATAK 3

3º Uvodi se pretpostavka da su oba BJT-a u DAR-u.



$$V_{OUT} = R_3 \left\{ (\beta + 1) \left[ (\beta + 1) \frac{\frac{V_{IN} - V_{BE1} - V_{BE2} - V_{OUT}}{R_1} + \beta I_2}{1 + \beta(\beta + 1)} - I_2 \right] + I_2 \right\}$$

$$V_{OUT} = R_3 \left[ (\beta + 1)^2 \frac{\frac{V_{IN} - V_{BE1} - V_{BE2} - V_{OUT}}{R_1} + \beta I_2}{1 + \beta(\beta + 1)} - (\beta + 1)I_2 + I_2 \right]$$


$$V_{OUT} = R_3 \left[ (\beta + 1)^2 \frac{V_{IN} - V_{BE1} - V_{BE2} - V_{OUT} + \beta R_1 I_2}{[1 + \beta(\beta + 1)]R_1} - (\beta + 1)I_2 + I_2 \right]$$

$$\left[ 1 + R_3 \frac{(\beta + 1)^2}{[1 + \beta(\beta + 1)]R_1} \right] V_{OUT}$$

$$= R_3 \frac{(\beta + 1)^2}{[1 + \beta(\beta + 1)]R_1} V_{IN} + R_3 \left[ (\beta + 1)^2 \frac{-V_{BE1} - V_{BE2} + \beta R_1 I_2}{[1 + \beta(\beta + 1)]R_1} - (\beta + 1)I_2 + I_2 \right]$$
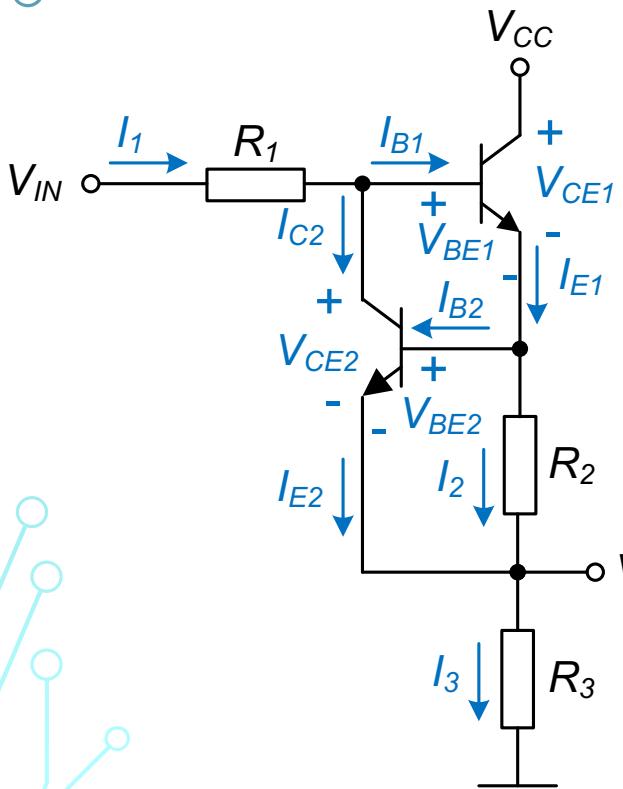
### ZADATAK 3

3º Uvodi se pretpostavka da su oba BJT-a u DAR-u.



$$\left[1 + \frac{R_3}{R_1}\right] V_{OUT} \approx \frac{R_3}{R_1} V_{IN} + R_3 \left[ \frac{-V_{BE1} - V_{BE2}}{R_1} + \frac{(\beta + 1)^2 \beta}{[1 + \beta(\beta + 1)]} I_2 - (\beta + 1)I_2 + I_2 \right]$$

$$V_{OUT} \approx \frac{R_3}{R_1 + R_3} V_{IN} + \frac{R_3}{R_1 + R_3} \left[ -V_{BE1} - V_{BE2} + \frac{(\beta + 1)^2 \beta}{[1 + \beta(\beta + 1)]} R_1 I_2 - \beta R_1 I_2 \right]$$

$$V_{OUT} \approx \frac{R_3}{R_1 + R_3} V_{IN} + \frac{R_3}{R_1 + R_3} [-V_{BE1} - V_{BE2} + 0.99 R_1 I_2]$$


$$V_{OUT} \approx 0.242 V_{IN} + 3.854 \text{ V}$$

$$V_{OUT}(V_{IN} = 7.175 \text{ V}) \approx 5.590 \text{ V}$$

$$V_{OUT}(V_{IN} = 10 \text{ V}) \approx 6.316 \text{ V}$$
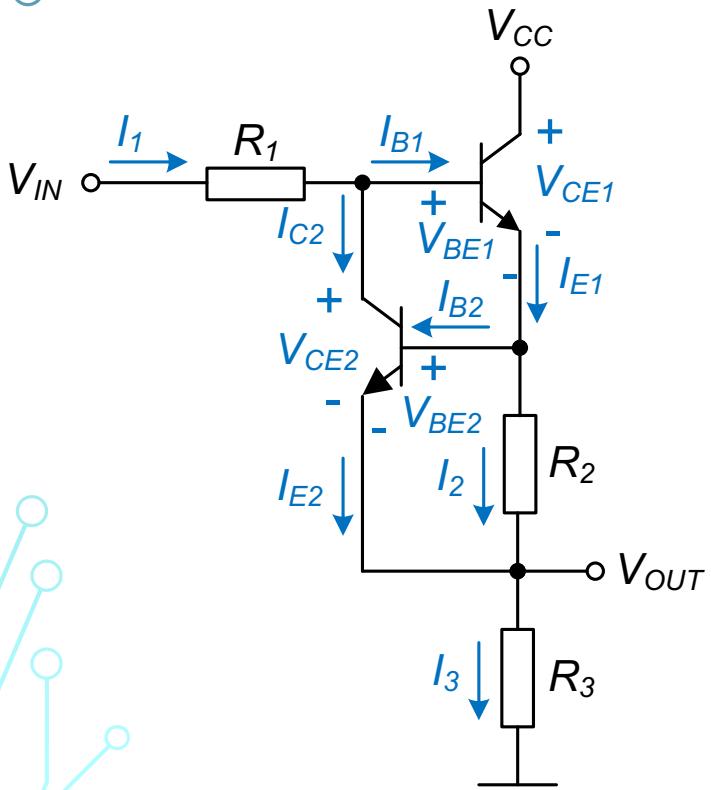
### ZADATAK 3

3º Uvodi se pretpostavka da su oba BJT-a u DAR-u.



$$V_{CE1} = V_{CC} - V_{BE2} - V_{OUT} > V_{CES1}$$

$$10 \text{ V} - 0.7 \text{ V} - 0.242 V_{IN} - 3.854 \text{ V} > 0.2 \text{ V}$$

$$V_{IN} < 21.68 \text{ V}$$

$$V_{CE2} = V_{BE1} + V_{BE2} = 1.4 \text{ V} > V_{CES2}$$

### ZADATAK 3

