




# VJEŽBE 4

OSNOVE ELEKTRONIKE, ETR, IV SEMESTAR

DOC. DR MILENA ERCEG

UVOD

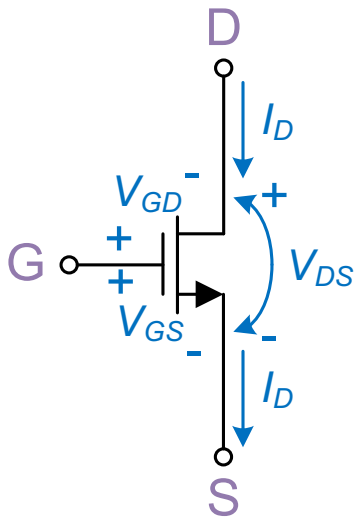

1° MOSFET ne vodi

$$V_{GS} < V_t, V_t > 0$$

$$I_D = 0$$

2° MOSFET vodi

a) omski režim

$$V_{GD} > V_t > 0$$


$$I_D = \beta \left[ (V_{GS} - V_t)V_{DS} - \frac{V_{DS}^2}{2} \right]$$

b) zasićenje

$$V_{GD} < V_t, V_t > 0$$

$$I_D = \frac{1}{2} \beta (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

UVOD

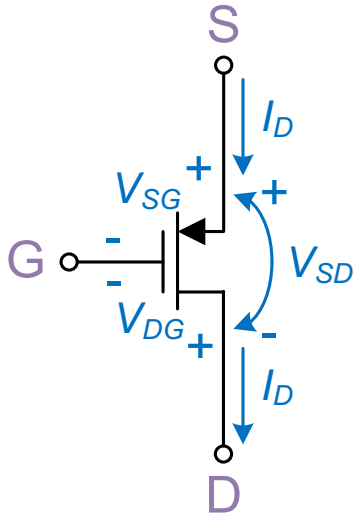

1° MOSFET ne vodi

$$V_{SG} < -V_t, V_t < 0$$

$$I_D = 0$$

2° MOSFET vodi

a) omski režim

$$V_{DG} > -V_t, V_t < 0$$

$$I_D = \beta \left[ (V_{SG} + V_t)V_{SD} - \frac{V_{SD}^2}{2} \right]$$


b) zasićenje

$$V_{DG} < -V_t, V_t < 0$$


$$I_D = \frac{1}{2} \beta (V_{SG} + V_t)^2 (1 + \lambda V_{SD})$$
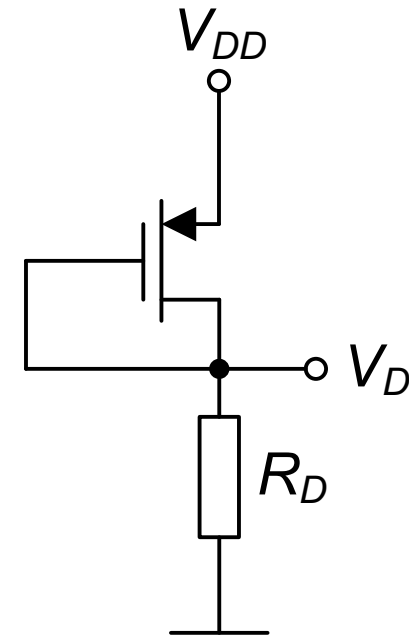
### ZADATAK 1

Za kolo prikazano na slici odrediti širinu kanala  $W$  MOSFET-a kao i otpornost  $R_D$ . Poznato je:  $V_{DD}=10$  V,  $V_t=-2$  V,  $\mu_p C_{ox}'=8$   $\mu\text{A}/\text{V}^2$ , dužina kanala  $L=10$   $\mu\text{m}$ , koeficijent modulacije dužine kanala  $\lambda \rightarrow 0$ ,  $I_D=0.1$  mA,  $V_D=7$  V.



## ZADATAK 1

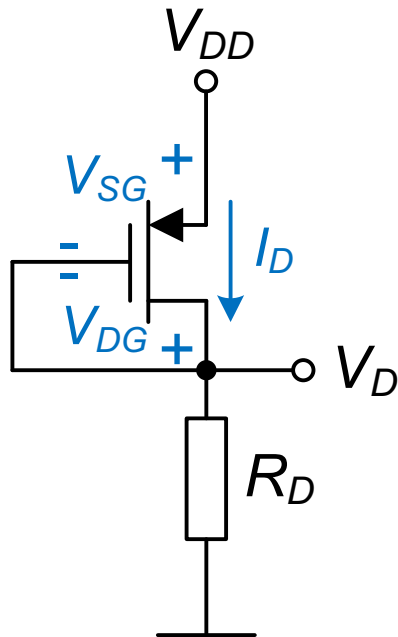

$$V_{DG} = 0 \text{ V} < -V_t$$

Slijedi da je MOSFET u zasićenju.

$$I_D = \frac{1}{2} \beta (V_{SG} + V_t)^2 (1 + \lambda V_{SD}) \approx \frac{1}{2} \beta (V_{SG} + V_t)^2$$

$$= \frac{1}{2} \mu_p C'_{ox} \frac{W}{L} (V_{SG} + V_t)^2$$


$$V_{SG} = V_{DD} - V_D$$

$$W \approx \frac{2LI_D}{\mu_p C'_{ox} (V_{DD} - V_D + V_t)^2} = 250 \text{ } \mu\text{m}$$


$$R_D = \frac{V_D}{I_D} = 70 \text{ k}\Omega$$
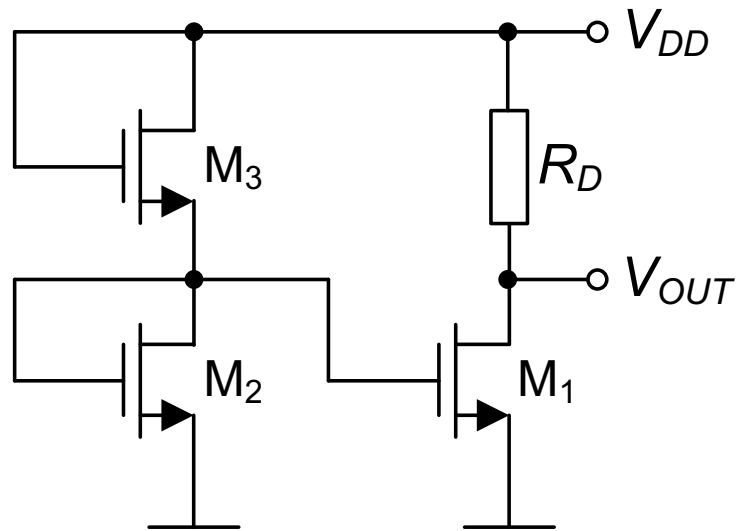
## ZADATAK 2

Za kolo prikazano na slici odrediti napon  $V_{OUT}$ . Poznato je:  $V_{DD}=12$  V,  $V_t=2$  V,  $\beta=100 \mu\text{A}/\text{V}^2$ ,  $R_D=25$  k $\Omega$ , koeficijent modulacije dužine kanala  $\lambda \rightarrow 0$ .



## ZADATAK 2

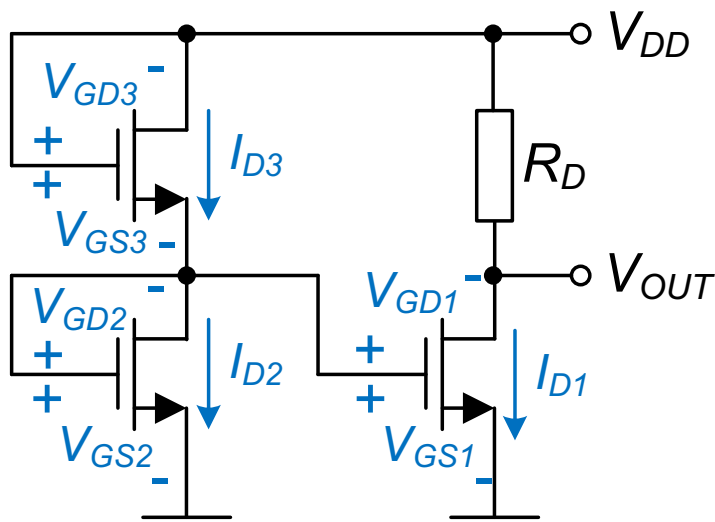

$$V_{GD2} = 0 \text{ V}$$

$$V_{GD3} = 0 \text{ V}$$

Slijedi da su MOSFET-ovi M<sub>2</sub> i M<sub>3</sub> u zasićenju.

$$I_{D2} = I_{D3}$$

$V_{GS2} = V_{GS3}$  (MOSFET-ovi su identičnih karakteristika)


$$V_{GS2} + V_{GS3} = V_{DD}$$

$$V_{GS2} = V_{GS3} = \frac{V_{DD}}{2} = 6 \text{ V}$$

Uvodi se pretpostavka da je i MOSFET M<sub>1</sub> u zasićenju.

$$I_{D1} = \frac{1}{2} \beta (V_{GS1} - V_t)^2 = 0.8 \text{ mA}$$

## ZADATAK 2

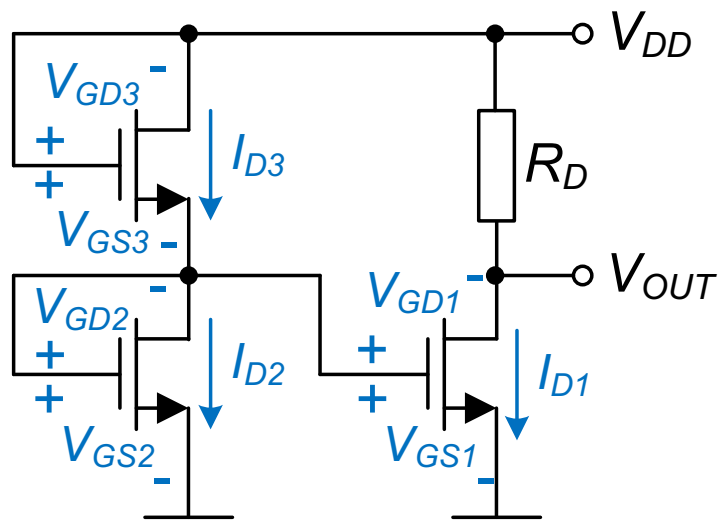

$$V_{OUT} = V_{DD} - R_D I_D = 10 \text{ V}$$


$$V_{GD1} = V_{GS1} - V_{OUT} = -4 \text{ V} < V_t$$

Pretpostavka o zasićenju MOSFET-a  $M_1$  je tačna.



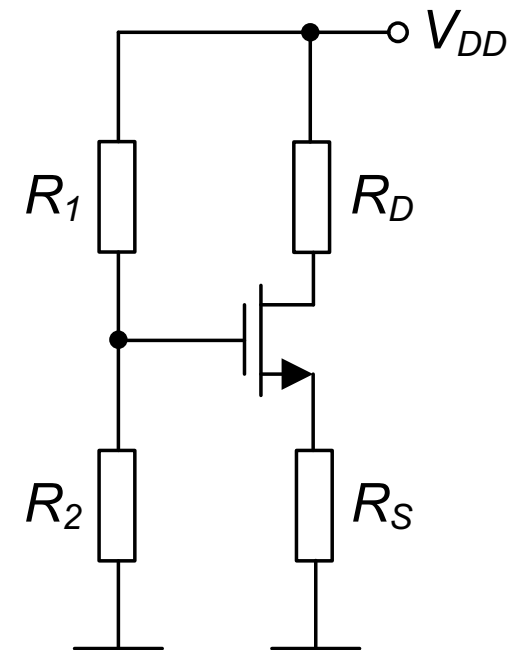
### ZADATAK 3

Za kolo prikazano na slici odrediti vrijednosti napona  $V_{GS}$ ,  $V_{GD}$ ,  $V_{DS}$  kao i vrijednost struje  $I_D$ . Poznato je:  $V_{DD}=12$  V,  $V_t=1$  V,  $\beta=1$  mA/V<sup>2</sup>,  $\lambda \rightarrow 0$ ,  $R_1=R_2=1$  M $\Omega$ ,  $R_D=2$  k $\Omega$  i  $R_S=3$  k $\Omega$ .



### ZADATAK 3

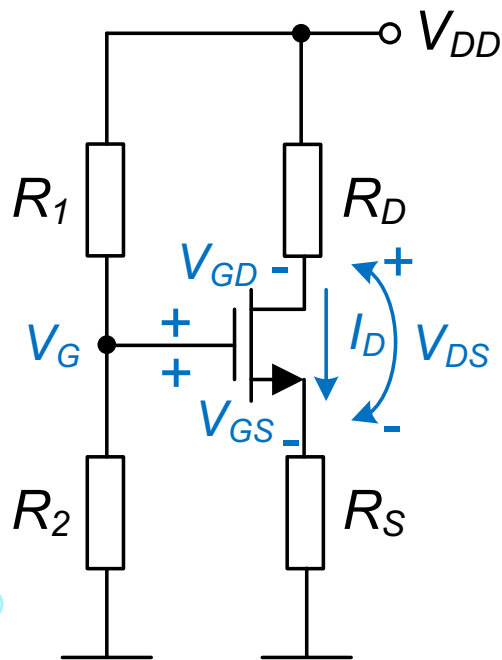

Uvodi se pretpostavka da je MOSFET u zasićenju.

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = 5 \text{ V}$$

$$V_{GS} = V_G - R_S I_D$$


$$I_D = \frac{1}{2} \beta (V_{GS} - V_t)^2 = \frac{1}{2} \beta (V_G - R_S I_D - V_t)^2$$

$$I_D = \frac{1}{2} \beta [(V_G - V_t)^2 - 2R_S I_D (V_G - V_t) + R_S^2 I_D^2]$$

$$\frac{\beta}{2} R_S^2 I_D^2 - [1 + \beta R_S (V_G - V_t)] I_D + \frac{\beta}{2} (V_G - V_t)^2 = 0$$

$$I_{D1,2} = \frac{1 + \beta R_S (V_G - V_t) \pm \sqrt{[1 + \beta R_S (V_G - V_t)]^2 - \beta^2 R_S^2 (V_G - V_t)^2}}{\beta R_S^2}$$

### ZADATAK 3

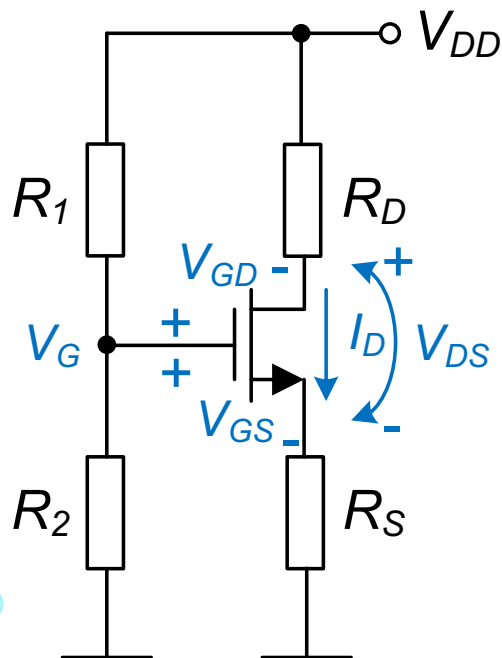

$$I_{D1,2} = \frac{1 + \beta R_S (V_G - V_t) \pm \sqrt{[1 + \beta R_S (V_G - V_t)]^2 - \beta^2 R_S^2 (V_G - V_t)^2}}{\beta R_S^2}$$

$$I_{D1,2} = \frac{1 + \beta R_S (V_G - V_t) \pm \sqrt{1 + 2\beta R_S (V_G - V_t)}}{\beta R_S^2}$$

$$I_{D1} = 2 \text{ mA}$$

$$I_{D2} = 0.89 \text{ mA}$$

$$V_{GS}(I_D = 2 \text{ mA}) = V_G - R_S I_D = -1 \text{ V} < V_t$$

$$V_{GS}(I_D = 0.89 \text{ mA}) = V_G - R_S I_D = 2.33 \text{ V} > V_t$$

$$I_D = 0.89 \text{ mA}$$


$$V_{GD} = V_G + R_D I_D - V_{DD} = -3.22 \text{ V} < V_t$$

Slijedi da je pretpostavka o zasićenju MOSFET-a tačna.


$$V_{DS} = V_{DD} - R_D I_D - R_S I_D = 5.56 \text{ V}$$
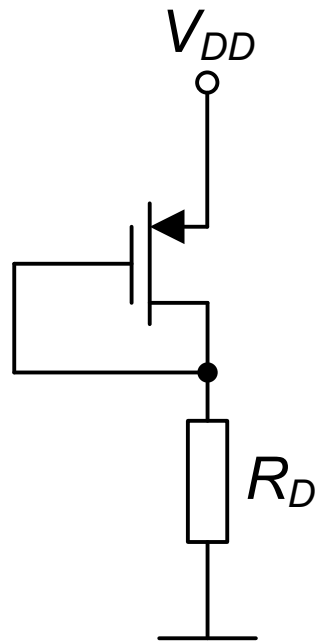
#### ZADATAK 4

Za kolo prikazano na slici odrediti struju  $I_D$  kao i napon  $V_{SG}$ . Poznato je:  $V_{DD}=10\text{ V}$ ,  $V_t=-2\text{ V}$ ,  $\beta=0.2\text{ mA/V}^2$ ,  $\lambda\rightarrow 0$ ,  $R_D=70\text{ k}\Omega$ .



#### ZADATAK 4

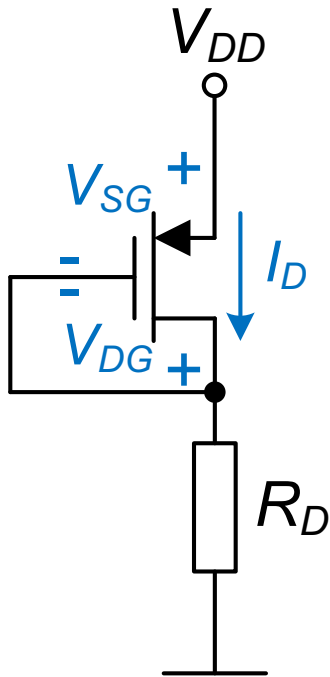

$$V_{DG} = 0 \text{ V} < -V_t$$

Slijedi da je MOSFET u zasićenju.

$$I_D = \frac{1}{2} \beta (V_{SG} + V_t)^2$$

$$V_{SG} = V_{DD} - R_D I_D$$


$$I_D = \frac{1}{2} \beta (V_{DD} - R_D I_D + V_t)^2$$

$$I_D = \frac{1}{2} \beta [(V_{DD} + V_t)^2 - 2R_D I_D (V_{DD} + V_t) + R_D^2 I_D^2]$$

$$\frac{\beta}{2} R_D^2 I_D^2 - [1 + \beta R_D (V_{DD} + V_t)] I_D + \frac{\beta}{2} (V_{DD} + V_t)^2 = 0$$

$$I_{D1,2} = \frac{1 + \beta R_D (V_{DD} + V_t) \pm \sqrt{[1 + \beta R_D (V_{DD} + V_t)]^2 - \beta^2 R_D^2 (V_{DD} + V_t)^2}}{\beta R_D^2}$$

ZADATAK 4

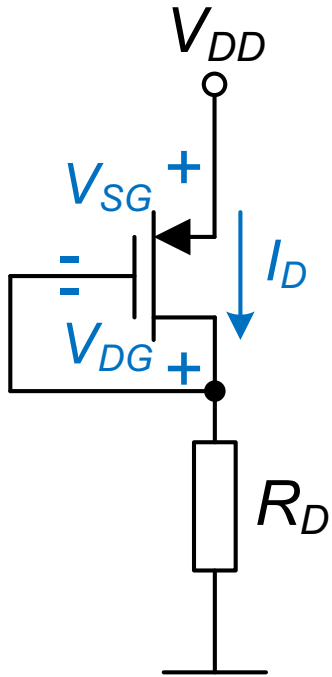

$$I_{D1,2} = \frac{1 + \beta R_D (V_{DD} + V_t) \pm \sqrt{[1 + \beta R_D (V_{DD} + V_t)]^2 - \beta^2 R_D^2 (V_{DD} + V_t)^2}}{\beta R_D^2}$$

$$I_{D1,2} = \frac{1 + \beta R_D (V_{DD} + V_t) \pm \sqrt{1 + 2\beta R_D (V_{DD} + V_t)}}{\beta R_D^2}$$

$$I_{D1} = 0.13 \text{ mA}$$

$$I_{D2} = 0.1 \text{ mA}$$

$$V_{SG}(I_D = 0.13 \text{ mA}) = V_{DD} - R_D I_D = 0.9 \text{ V} < V_t$$


$$V_{SG}(I_D = 0.1 \text{ mA}) = V_{DD} - R_D I_D = 3 \text{ V} > V_t$$

$$I_D = 0.1 \text{ mA}$$


$$V_{SG} = 3 \text{ V}$$
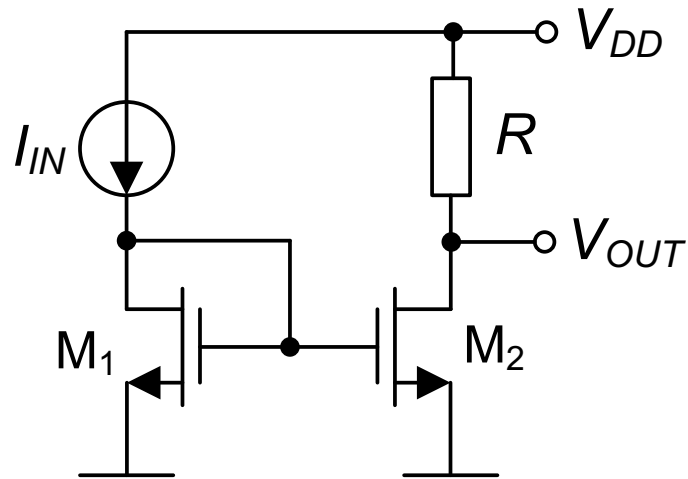
## ZADATAK 5

Za kolo prikazano na slici odrediti zavisnost napona  $V_{OUT}$  od ulazne struje  $I_{IN}$ , za opseg ulazne struje  $0 < I_{IN} < 2$  mA. Poznato je:  $V_{DD} = 1.5$  V,  $V_{t1} = V_{t2}$ ,  $\beta_1 = \beta_2 = 5$  mA/V<sup>2</sup>,  $\lambda_1 \rightarrow 0$ ,  $\lambda_2 \rightarrow 0$  i  $R = 1$  k $\Omega$ .



## ZADATAK 5

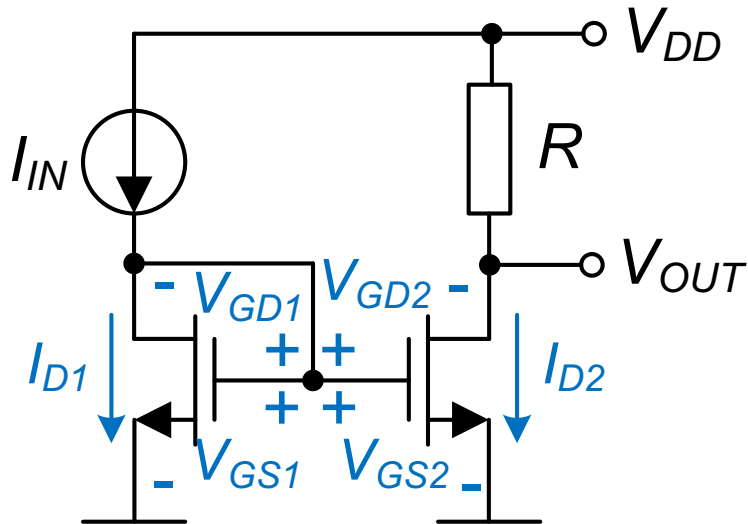

$$V_{GD1} = 0 < V_{t1}$$

Slijedi da je MOSFET  $M_1$  u zasićenju.

1° Uvodi se pretpostavka da je i MOSFET  $M_2$  u zasićenju.

$$V_{GS1} = V_{GS2} \Rightarrow I_{D2} = I_{IN}$$

$$I_{IN} = \frac{\beta_1}{2} (V_{GS1} - V_{t1})^2 \Rightarrow V_{GS1} = \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1} > V_{t1}, I_{IN} > 0$$


$$V_{GS2} = V_{GS1} = \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1}$$

$$V_{OUT} = V_{DD} - RI_{D2} = V_{DD} - RI_{IN}$$

$$V_{GD2} = V_{GS2} - V_{OUT} = \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1} - V_{DD} + RI_{IN} < V_{t2}$$



ZADATAK 5

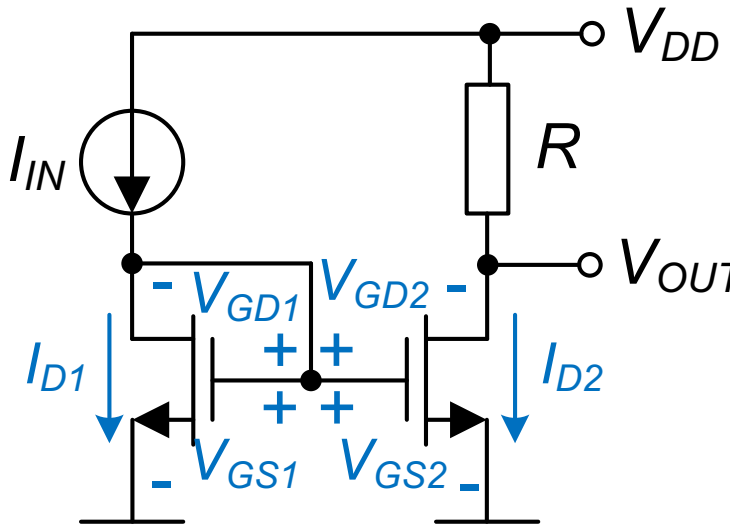

$$V_{GD2} = V_{GS2} - V_{OUT} = \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1} - V_{DD} + RI_{IN} < V_{t2}$$

$$\sqrt{\frac{2I_{IN}}{\beta_1}} - V_{DD} + RI_{IN} < 0$$


$$R(\sqrt{I_{IN}})^2 + \sqrt{\frac{2I_{IN}}{\beta_1}} - V_{DD} < 0$$

$$\sqrt{I_{IN_{1,2}}} = \frac{-\sqrt{\frac{2}{\beta_1}} \pm \sqrt{\frac{2}{\beta_1} + 4RV_{DD}}}{2R}$$

$$\sqrt{I_{IN_1}} = 0.03\sqrt{A}$$

$$\sqrt{I_{IN_2}} = -0.05\sqrt{A}$$

## ZADATAK 5

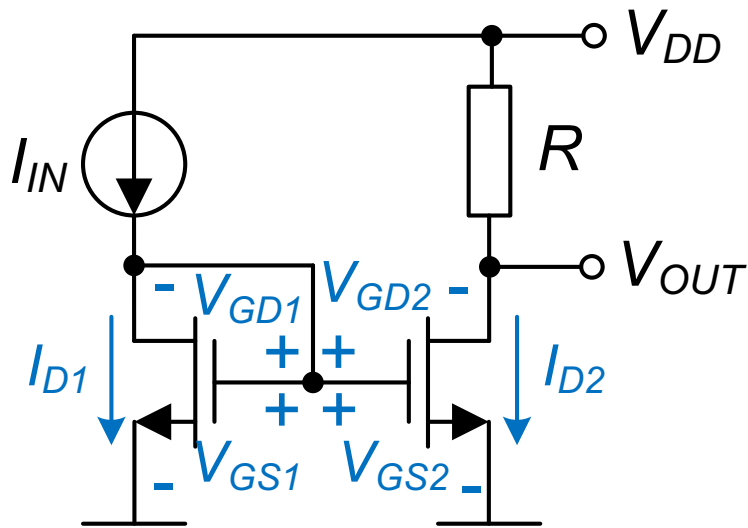

$$0 < \sqrt{I_{IN}} < 0.03\sqrt{A}$$

$$0 < I_{IN} < 0.9 \text{ mA}$$


$$V_{OUT}(I_{IN} = 0.9 \text{ mA}) = V_{DD} - RI_{IN} = 0.6 \text{ V}$$

$$V_{GS1}(I_{IN} = 0.9 \text{ mA}) = \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1} = 0.6 \text{ V} + V_{t1}$$

$$V_{GD2}(I_{IN} = 0.9 \text{ mA}) = V_{GS2} - V_{OUT} = V_{t1}$$

Daljim padom napona  $V_{OUT}$ , MOSFET  $M_2$  prelazi u omski režim rada.

## ZADATAK 5

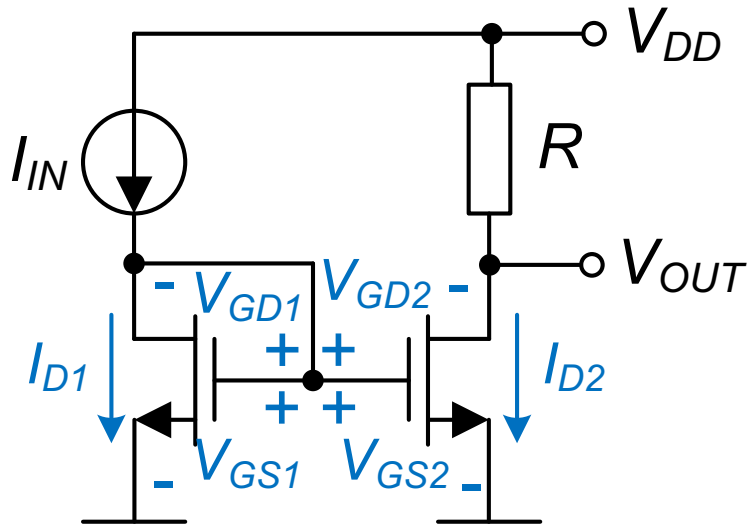

2° Uvodi se pretpostavka da je MOSFET  $M_2$  u omskom režimu.

$$I_{D2} = \beta_2 \left[ (V_{GS2} - V_{t2})V_{DS2} - \frac{V_{DS2}^2}{2} \right]$$


$$I_{D2} = \beta_2 \left[ \left( \sqrt{\frac{2I_{IN}}{\beta_1}} + V_{t1} - V_{t2} \right) V_{OUT} - \frac{V_{OUT}^2}{2} \right]$$

$$V_{OUT} = \beta_2 \left( \sqrt{\frac{2I_{IN}}{\beta_1}} V_{OUT} - \frac{V_{OUT}^2}{2} \right)$$

$$V_{OUT} = V_{DD} - RI_{D2} = V_{DD} - R\beta_2 \left( \sqrt{\frac{2I_{IN}}{\beta_1}} V_{OUT} - \frac{V_{OUT}^2}{2} \right)$$

$$\frac{R\beta_2}{2} V_{OUT}^2 - \left( 1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} \right) V_{OUT} + V_{DD} = 0$$

ZADATAK 5

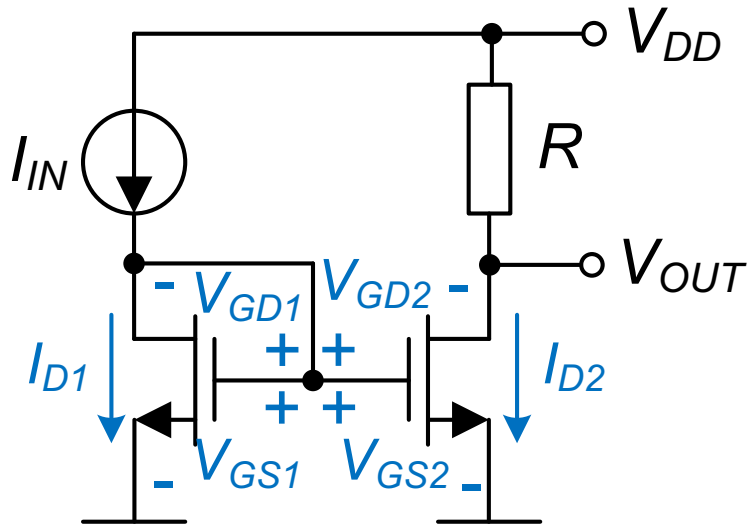

$$\frac{R\beta_2}{2} V_{OUT}^2 - \left( 1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} \right) V_{OUT} + V_{DD} = 0$$


$$V_{OUT1,2} = \frac{1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} \pm \sqrt{\left( 1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} \right)^2 - 2R\beta_2 V_{DD}}}{R\beta_2}$$

$$V_{OUT} = \frac{1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} - \sqrt{\left( 1 + R\beta_2 \sqrt{\frac{2I_{IN}}{\beta_1}} \right)^2 - 2R\beta_2 V_{DD}}}{R\beta_2}$$

$$V_{OUT}(I_{IN} = 0.9 \text{ mA}) = 0.6 \text{ V}$$

$$V_{OUT}(I_{IN} = 2 \text{ mA}) = 0.32 \text{ V}$$

ZADATAK 5

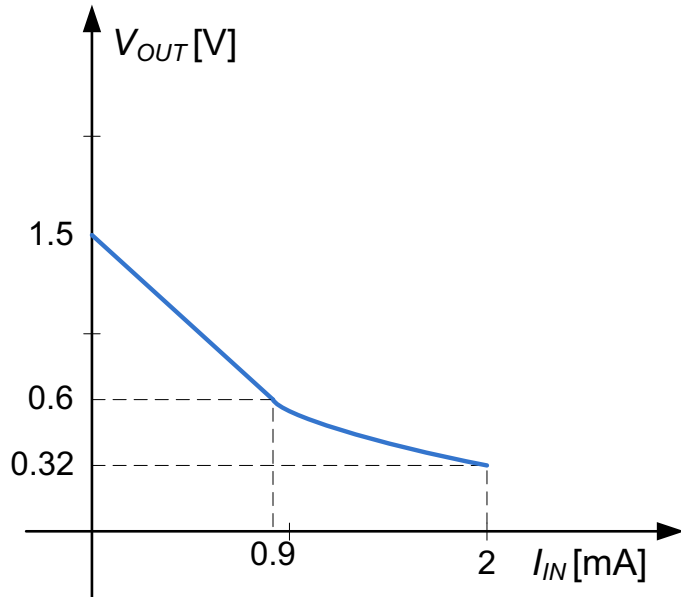

$0 < I_{IN} < 0.9 \text{ mA}$ :

$$V_{OUT} = V_{DD} - RI_{IN}$$

$0.9 \text{ mA} < I_{IN} < 2 \text{ mA}$ :

$$V_{OUT} = \frac{1 + R\beta_2\sqrt{\frac{2I_{IN}}{\beta_1}} - \sqrt{\left(1 + R\beta_2\sqrt{\frac{2I_{IN}}{\beta_1}}\right)^2 - 2R\beta_2V_{DD}}}{R\beta_2}$$