




VJEŽBE 6

OSNOVE ELEKTRONIKE, ETR, IV SEMESTAR



DOC. DR. MILENA ERCEG

ZADATAK 1


Za kolo prikazano na slici izračunati naponsko pojačanje A_v i izlaznu otpornost R_{out} . Poznato je: napon napajanja kola $V_{DD}=5$ V, otpornosti $R_1=100$ k Ω , $R_2=47$ k Ω , $R_D=3.3$ k Ω , otpornost potrošača $R_L=10$ k Ω , unutrašnja otpornost generatora $R_g=1$ k Ω , napon praga MOSFET-a $V_t=1.2$ V, $\beta=1$ mA/V², koeficijent modulacije dužine kanala $\lambda=0.02$ V⁻¹.

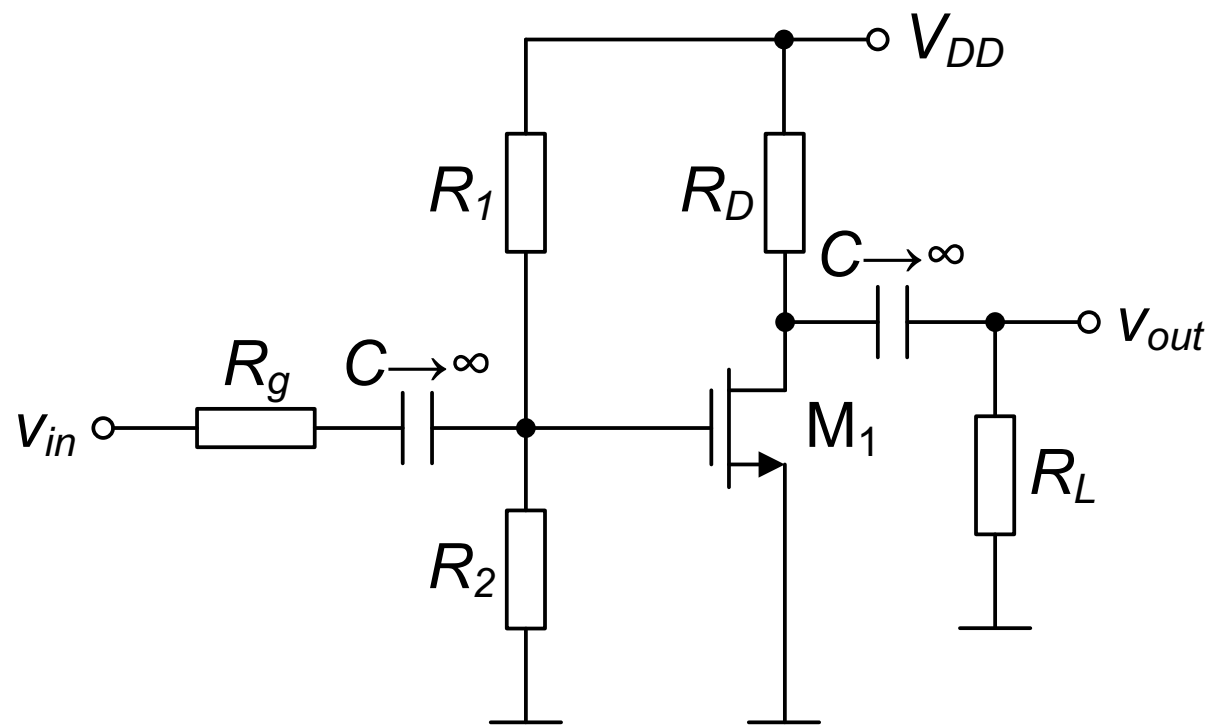

ZADATAK 1

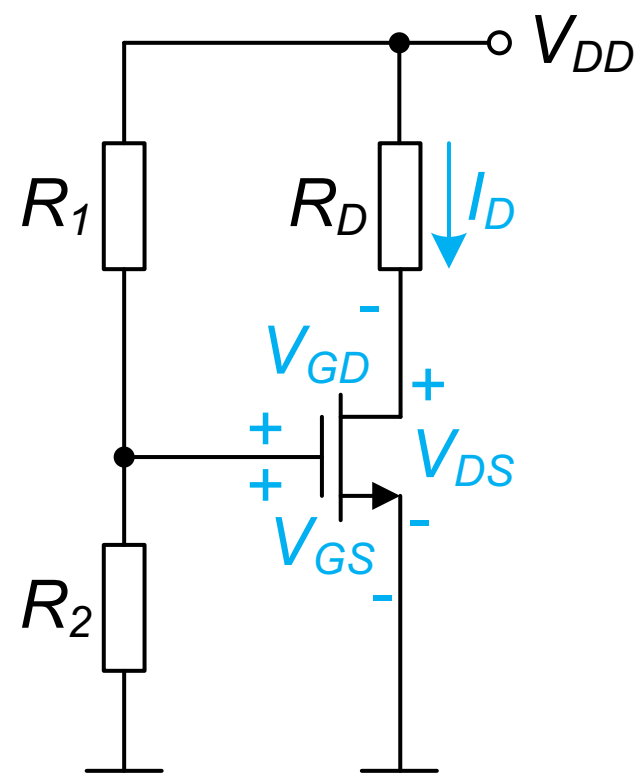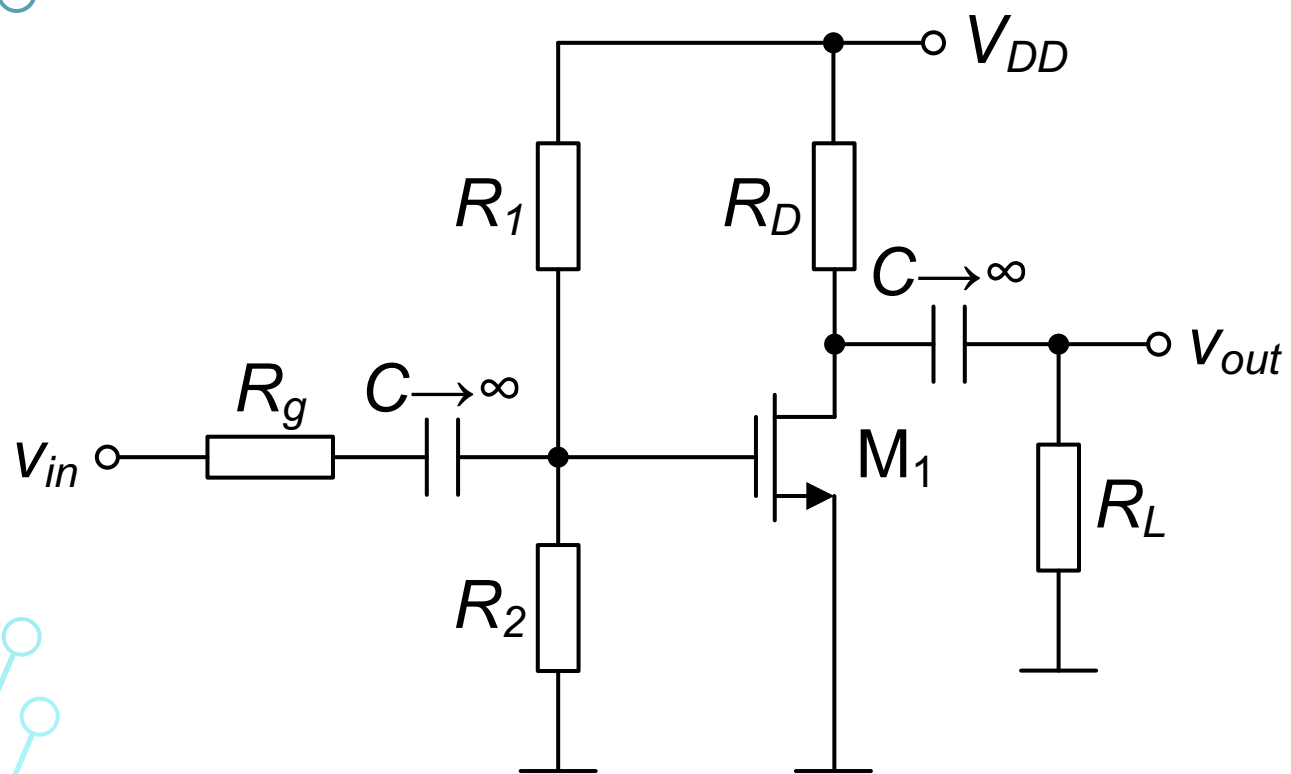

ZADATAK 1- DC ANALIZA

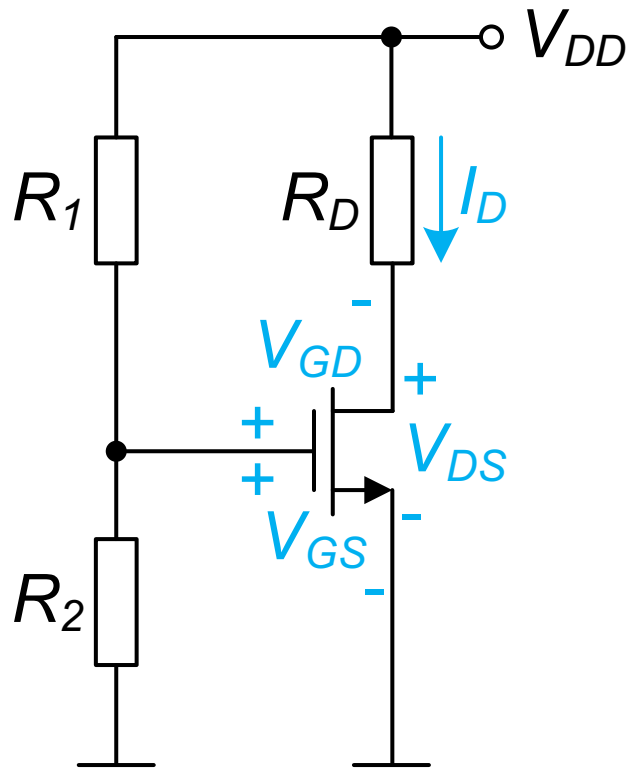

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} = 1.6 \text{ V} > V_t$$



Uvodi se pretpostavka da je MOSFET M_1 u zasićenju.

$$I_D = \frac{1}{2} \beta (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \approx \frac{1}{2} \beta (V_{GS} - V_t)^2 = 80 \mu\text{A}$$

$$V_{GD} = V_{GS} + R_D I_D - V_{DD} = -3.136 \text{ V} < V_t$$

Slijedi da je pretpostavka o zasićenju tačna.

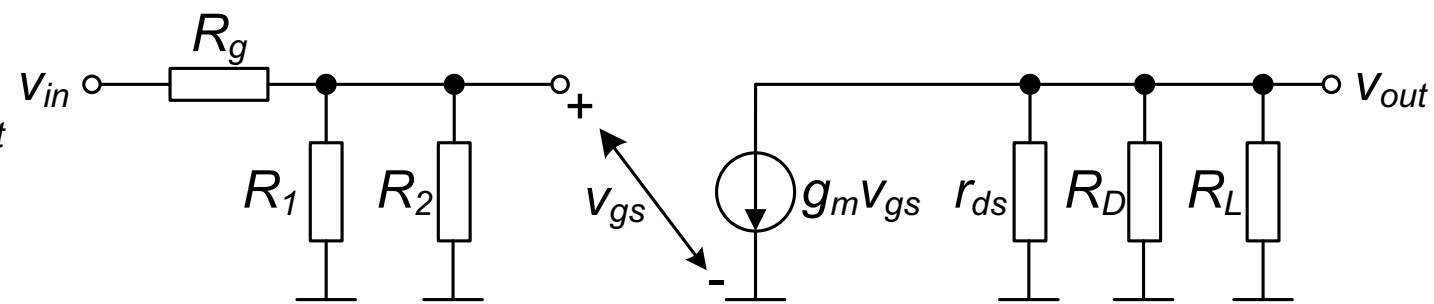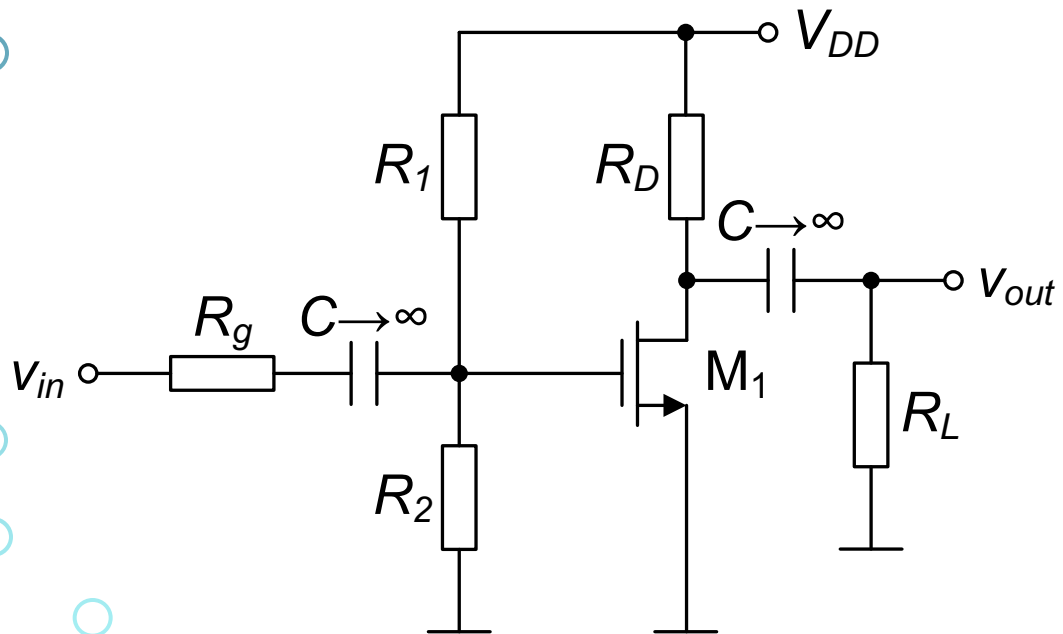
ZADATAK 1 – ODREĐIVANJE NAPONSKOG POJAČANJA



$$g_m = \sqrt{2\beta I_D} = 0.4 \text{ mS}$$

$$r_{ds} = \frac{1}{\lambda I_D} = 625 \text{ k}\Omega$$

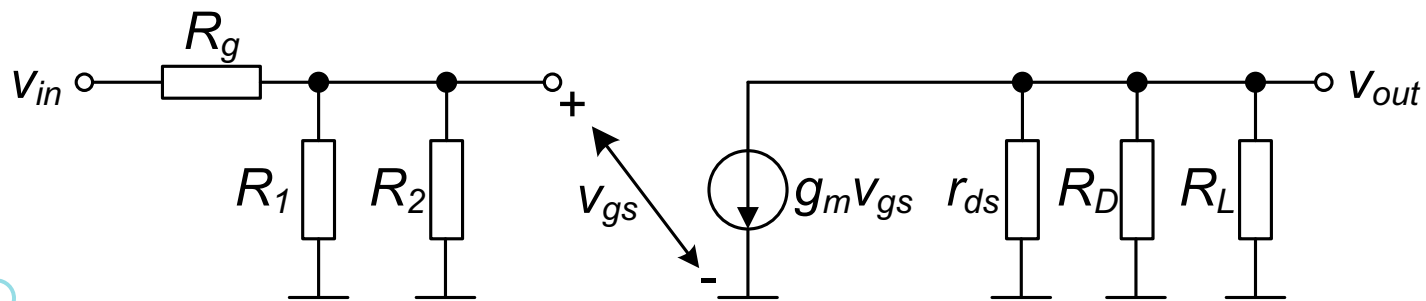ZADATAK 1 - ODREĐIVANJE NAPONSKOG POJAČANJA



$$R_{e1} = \frac{R_1 R_2}{R_1 + R_2} = 31.97 \text{ k}\Omega$$



$$R_{e2} = \frac{1}{\frac{1}{r_{ds}} + \frac{1}{R_D} + \frac{1}{R_L}} = 2.47 \text{ k}\Omega$$

$$v_{gs} = \frac{R_{e1}}{R_g + R_{e1}} v_{in}$$


$$g_m v_{gs} + \frac{v_{out}}{R_{e2}} = 0$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m \frac{R_{e1} R_{e2}}{R_g + R_{e1}} = -0.96$$

ZADATAK 1 – ODREĐIVANJE IZLAZNE OTPORNOSTI

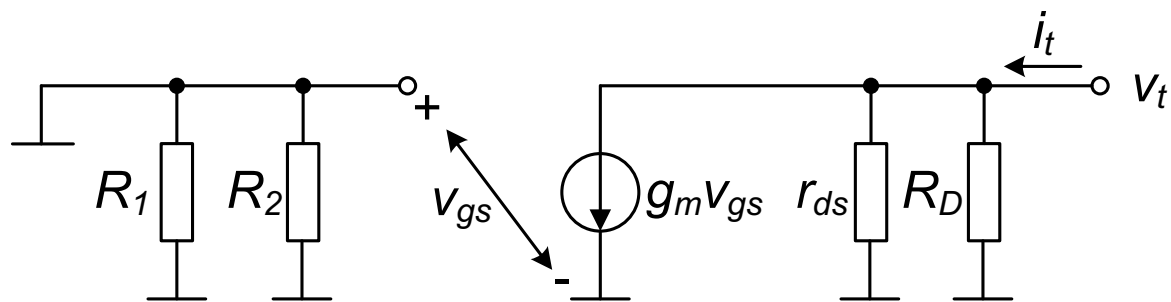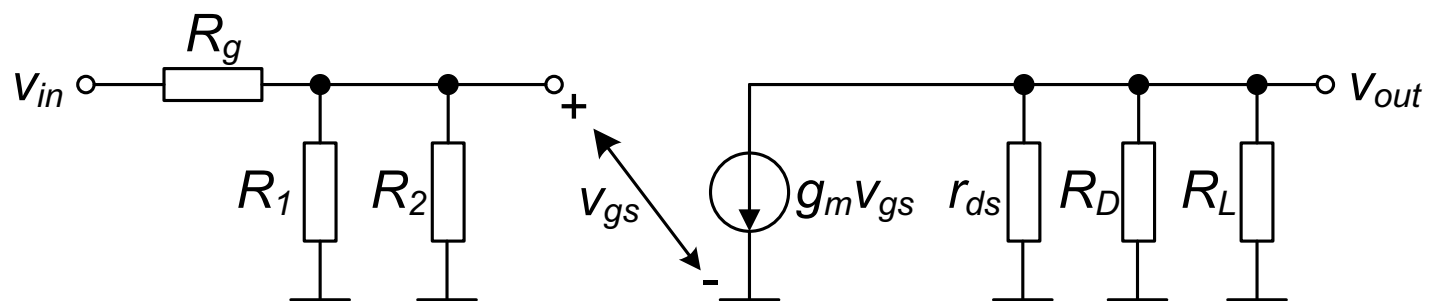

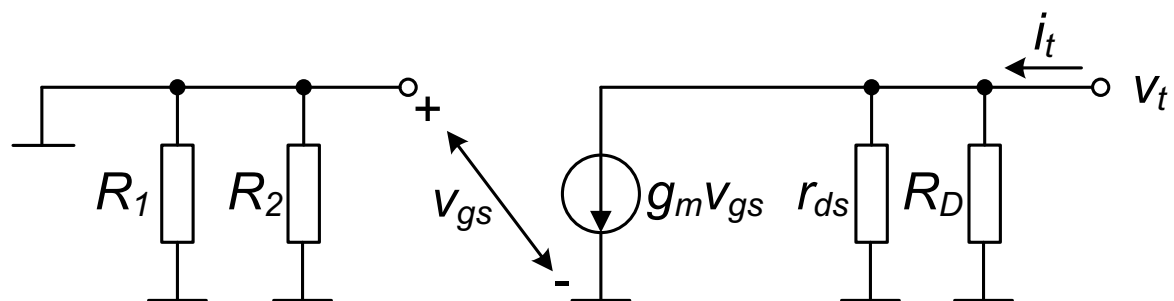ZADATAK 1 – ODREĐIVANJE IZLAZNE OTPORNOSTI




$$v_{gs} = 0$$



$$R_{out} = \frac{v_t}{i_t} = \frac{r_{ds} R_D}{r_{ds} + R_D} = 3.28 \text{ k}\Omega$$

ZADATAK 2


Za kolo prikazano na slici izračunati naponsko pojačanje A_v i izlaznu otpornost R_{out} . Poznato je: napon napajanja kola $V_{DD}=10$ V, otpornosti $R_1=54.4$ k Ω , $R_2=100$ k Ω , $R_S=2$ k Ω , otpornost potrošača $R_L=2$ k Ω , napon praga MOSFET-a $V_t=2$ V, $\beta=2$ mA/V², koeficijent modulacije dužine kanala $\lambda=0.001$ V⁻¹.

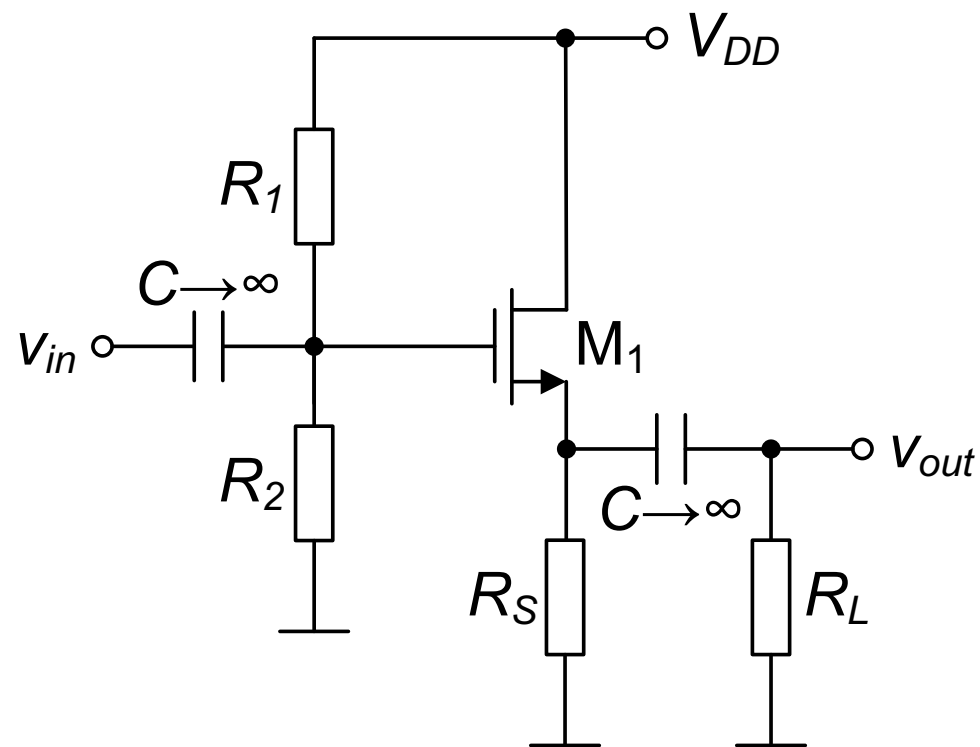

ZADATAK 2

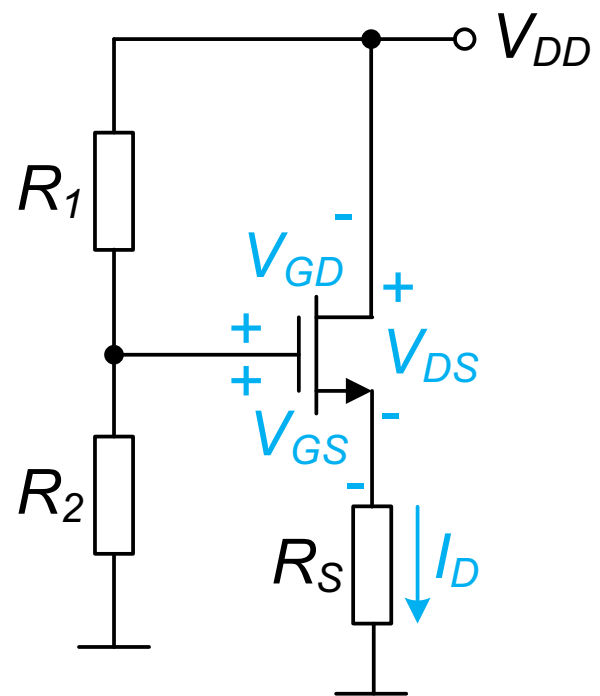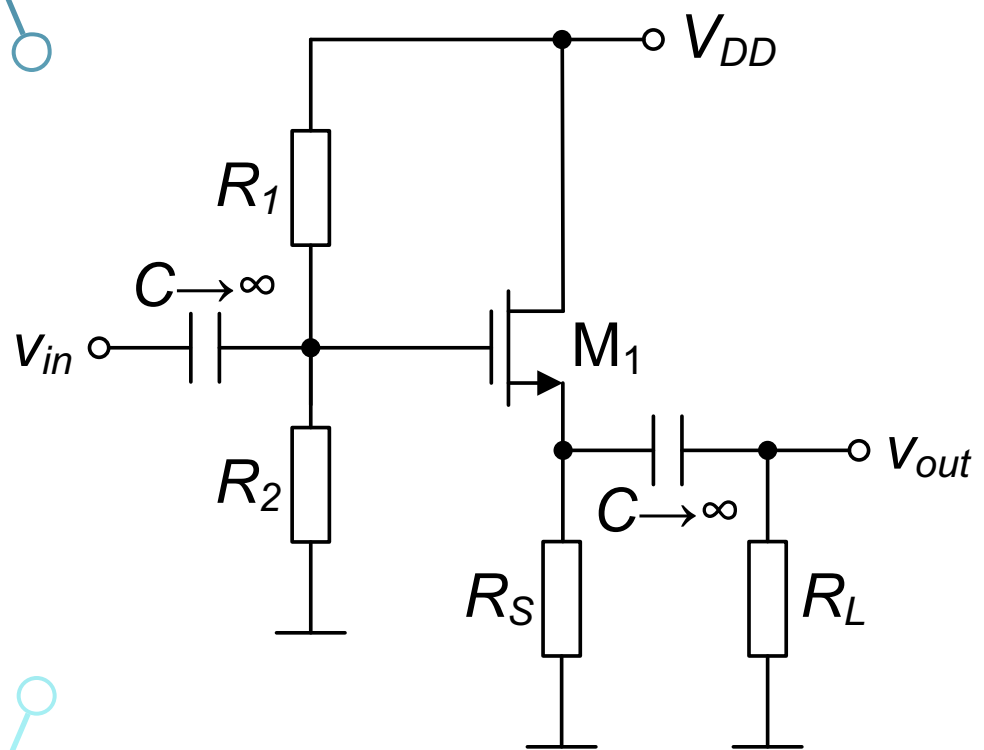

ZADATAK 2 – DC ANALIZA

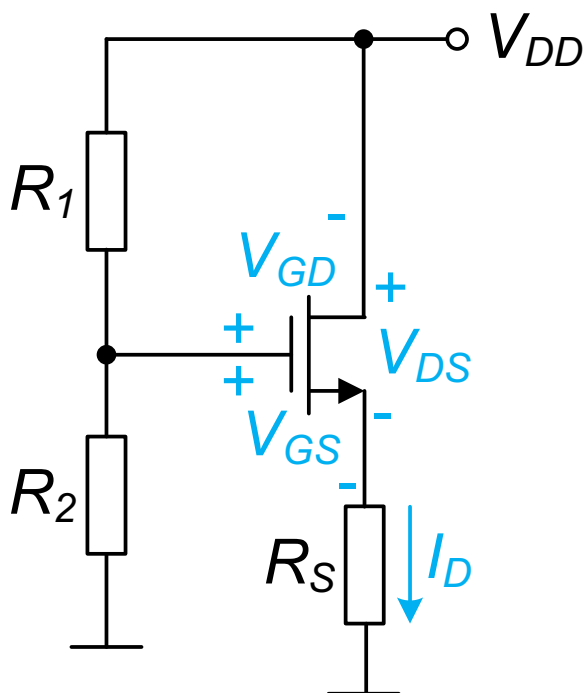

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = 6.47 \text{ V}$$

$$V_{GD} = V_G - V_{DD} = -3.53 \text{ V} < V_t$$

Slijedi da je MOSFET M_1 u zasićenju.

$$\begin{aligned} I_D &= \frac{1}{2} \beta (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \approx \frac{1}{2} \beta (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \beta (V_G - R_S I_D - V_t)^2 \end{aligned}$$

$$I_{D1} = 3.12 \text{ mA} \text{ i } I_{D2} = 1.6 \text{ mA}$$



$$V_{GS}(I_D = I_{D1}) = V_G - R_S I_{D1} = 0.23 \text{ V} < V_t$$

Ovo rješenje nije prihvatljivo.

$$V_{GS}(I_D = I_{D2}) = V_G - R_S I_{D2} = 3.27 \text{ V} > V_t$$

$$\Rightarrow I_D = 1.6 \text{ mA}$$

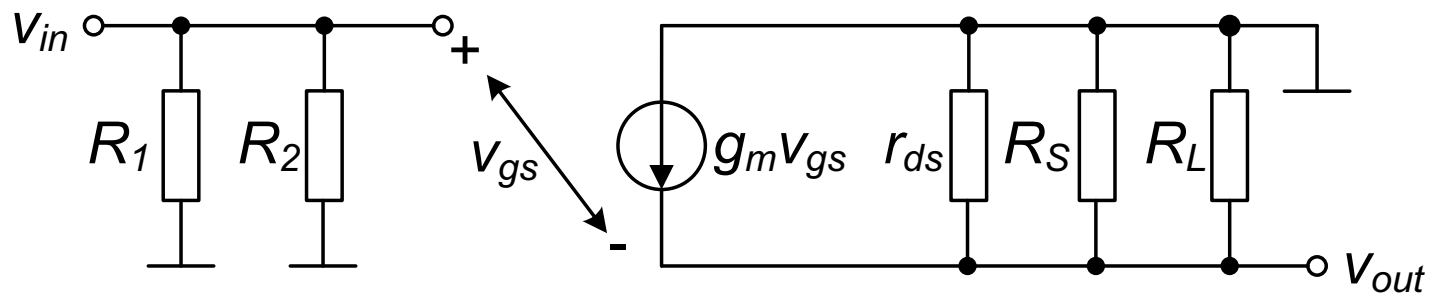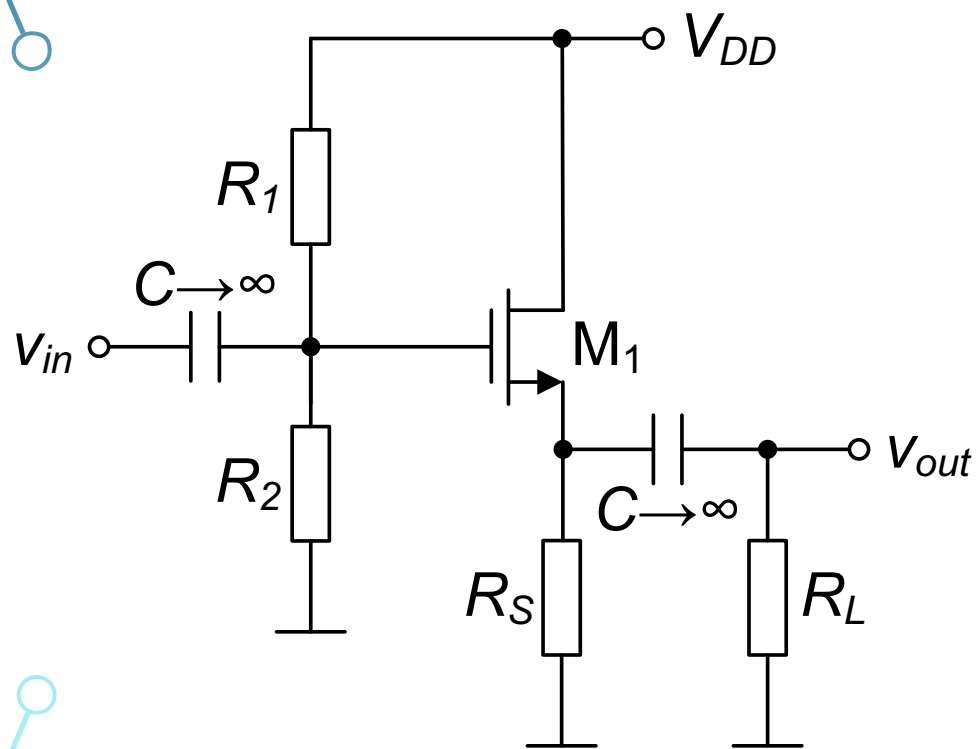
ZADATAK 2 – ODREĐIVANJE NAPONSKOG POJAČANJA



$$g_m = \sqrt{2\beta I_D} = 2.53 \text{ mS}$$

$$r_{ds} = \frac{1}{\lambda I_D} = 62.5 \text{ k}\Omega$$

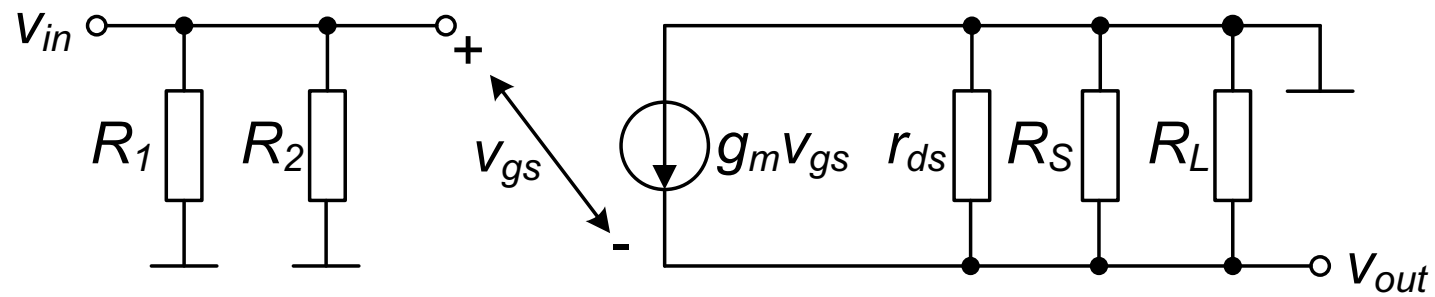ZADATAK 2 – ODREĐIVANJE NAPONSKOG POJAČANJA





$$R_{e1} = \frac{1}{\frac{1}{r_{ds}} + \frac{1}{R_S} + \frac{1}{R_L}} = 0.98 \text{ k}\Omega$$

$$v_{gs} = v_{in} - v_{out}$$


$$g_m v_{gs} - \frac{v_{out}}{R_{e1}} = 0$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{g_m R_{e1}}{1 + g_m R_{e1}} = 0.71$$

ZADATAK 2 – ODREĐIVANJE IZLAZNE OTPORNOSTI

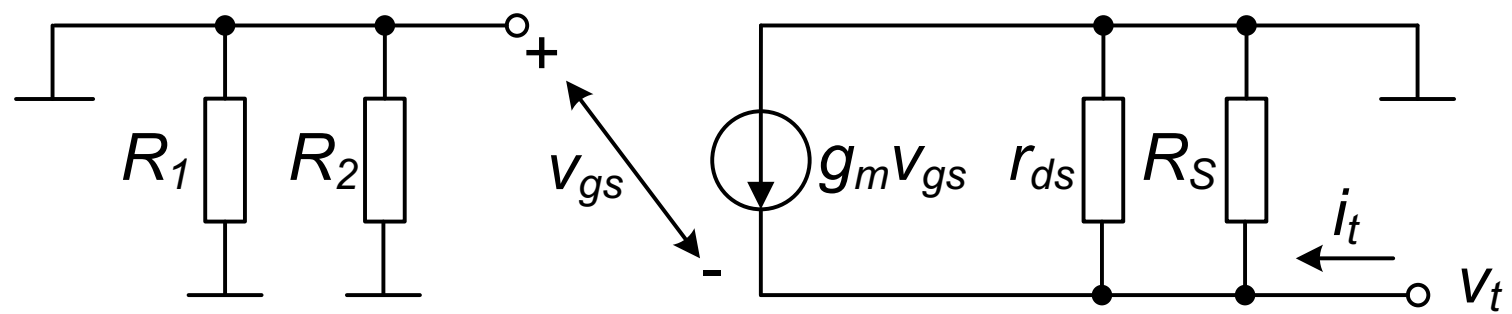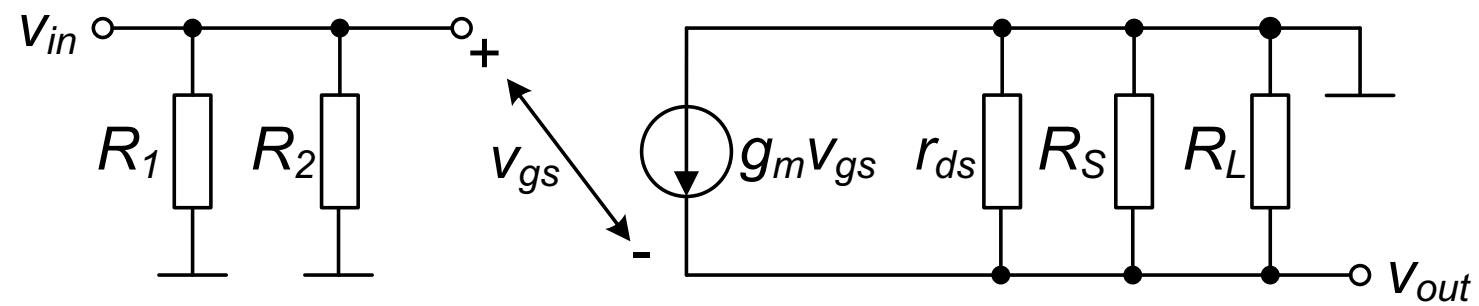

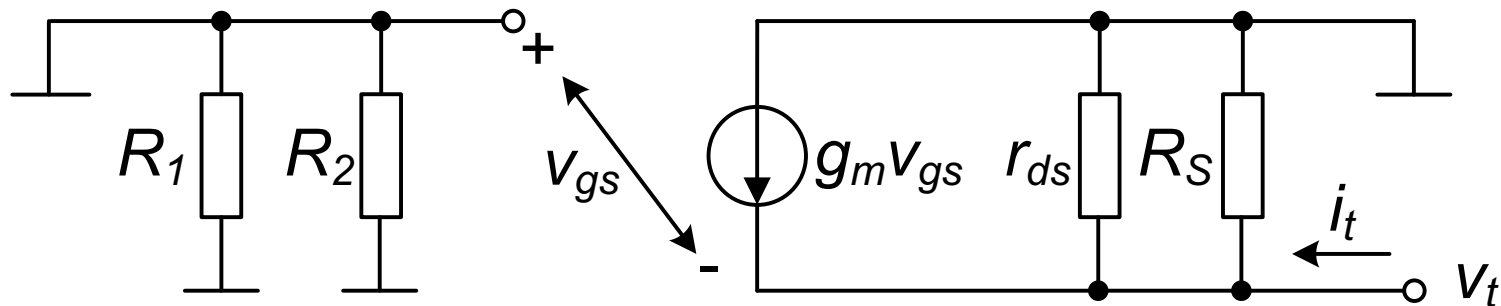ZADATAK 2 – ODREĐIVANJE IZLAZNE OTPORNOSTI




$$v_{gs} = -v_t$$

$$g_m v_{gs} + i_t - v_t \left(\frac{1}{r_{ds}} + \frac{1}{R_S} \right) = 0$$



$$R_{out} = \frac{v_t}{i_t} = \frac{r_{ds} R_S}{r_{ds} + (1 + g_m r_{ds}) R_S} = 328.3 \, \Omega$$

ZADATAK 3


Za kolo prikazano na slici izračunati odnos otpornosti $x=R_1/R_2$ tako da jednosmjerni napon na izlazu kola iznosi $V_{OUT}=2.5$ V. Poznato je: napon napajanja kola $V_{DD}=5$ V, otpornosti $R_S=1$ k Ω i $R_L=1$ k Ω , napon praga MOSFET-a $V_t=0.8$ V, faktor $\beta_M=11$ mA/V² MOSFET-a, koeficijent modulacije dužine kanala MOSFET-a $\lambda_M=0.05$ V⁻¹, strujno pojačanje BJT-a $\beta_B=100$, napon baza-emitor BJT-a kada provodi $V_{BE}=0.7$ V, napon kolektor-emitor BJT-a u zasićenju $V_{CES}=0.2$ V, termički napon $V_T=25$ mV, *Early*-jev napon $V_A=20$ V. Izračunati naponsko pojačanje A_v .

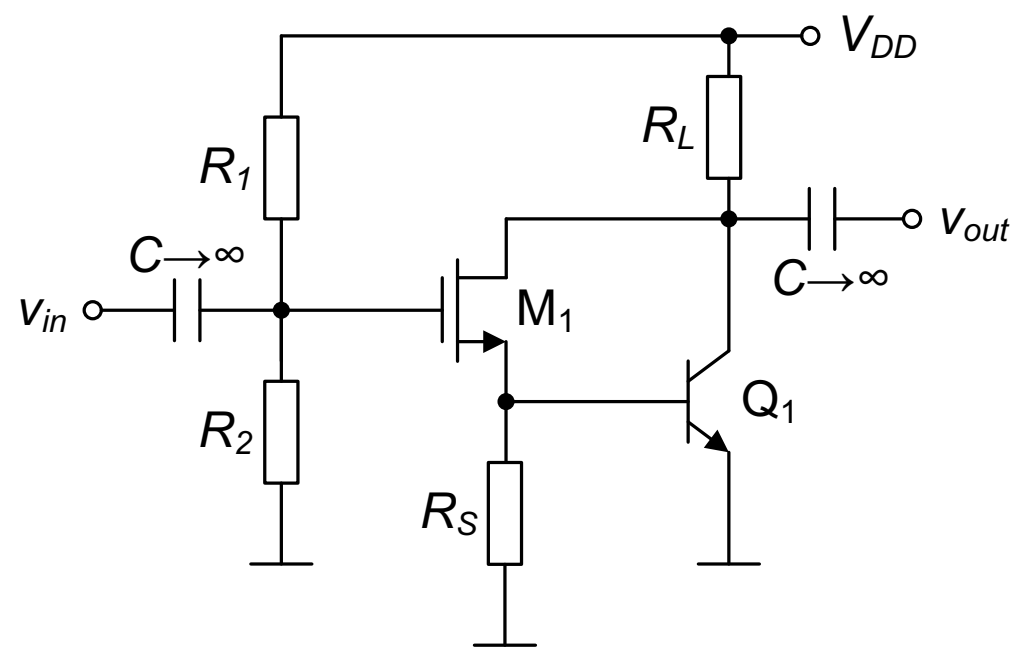

ZADATAK 3 – DC ANALIZA

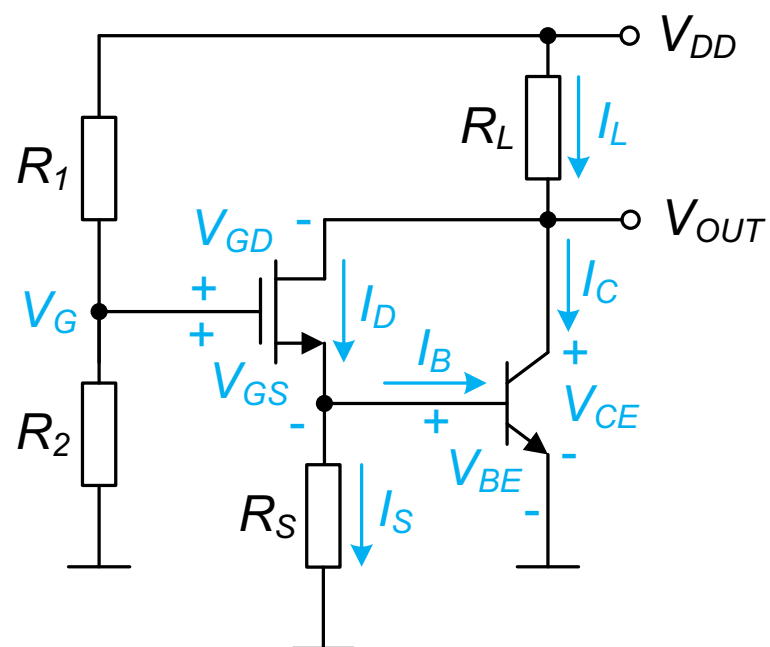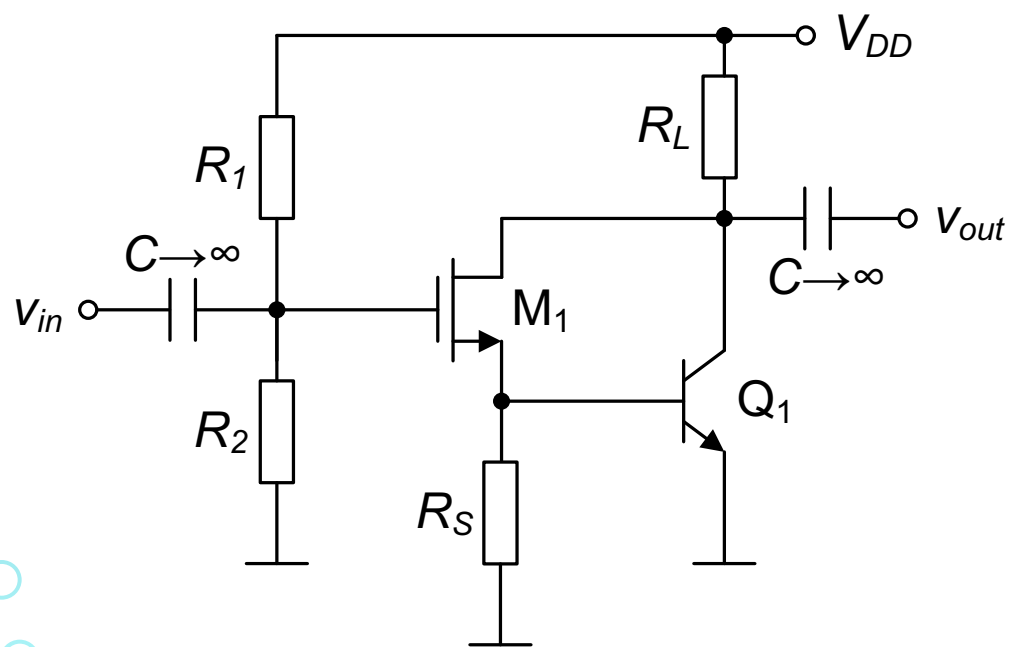

ZADATAK 3 – DC ANALIZA

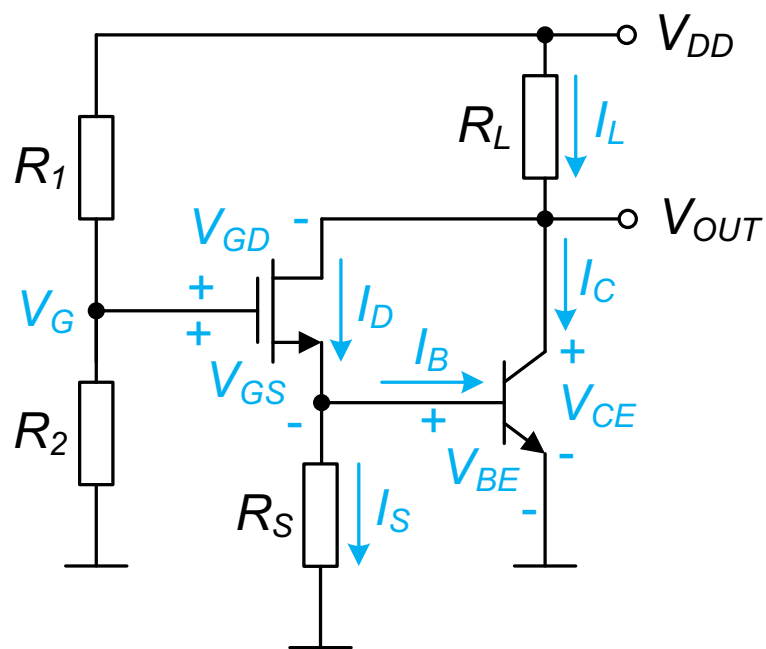

Uvodi se pretpostavka da je MOSFET u zasićenju.

$$V_{CE} = V_{OUT} > V_{CES}$$

Slijedi da je BJT u DAR-u.

$$I_L = \frac{V_{DD} - V_{OUT}}{R_L} = 2.5 \text{ mA}$$

$$I_S = \frac{V_{BE}}{R_S} = 0.7 \text{ mA}$$


$$I_L = I_D + I_C$$

$$I_D = I_S + I_B$$

$$I_C = \beta_B I_B$$

$$\Rightarrow I_D = \frac{\beta_B I_S + I_L}{\beta_B + 1}$$

ZADATAK 3 – DC ANALIZA

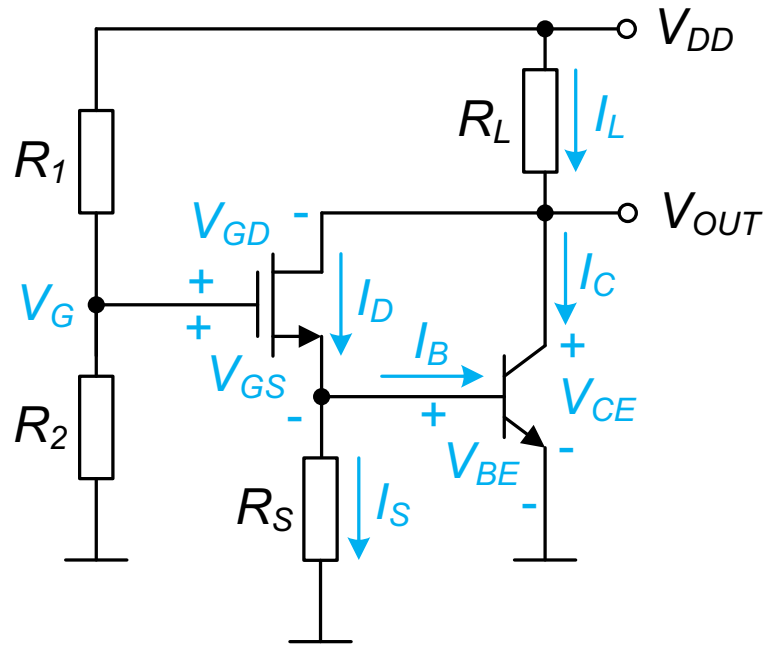

$$I_D = \frac{1}{2} \beta_M (V_{GS} - V_t)^2 (1 + \lambda_M V_{DS}) \approx \frac{1}{2} \beta_M (V_{GS} - V_t)^2$$

$$V_{GS} = V_G - V_{BE}$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{1}{x + 1} V_{DD}$$

$$x = \frac{R_1}{R_2} \approx \frac{V_{DD}}{\sqrt{\frac{2}{\beta_M} \frac{I_L + \beta_B I_S}{\beta_B + 1}} + V_{BE} + V_t} - 1 = 1.69$$



$$V_{GS} = 1.16 \text{ V}$$

$$I_D = 0.71 \text{ mA}$$

$$V_{GD} = V_G - V_{OUT} = -0.64 \text{ V} < V_t$$

Slijedi da je pretpostavka o zasićenju MOSFET-a tačna.

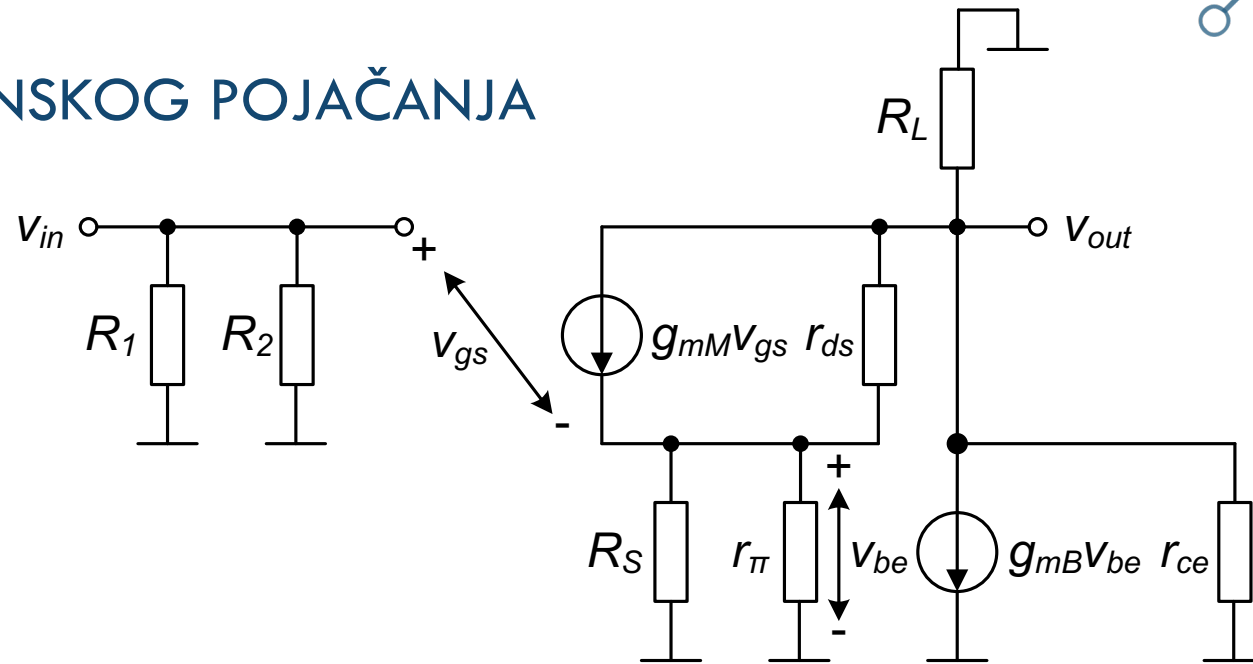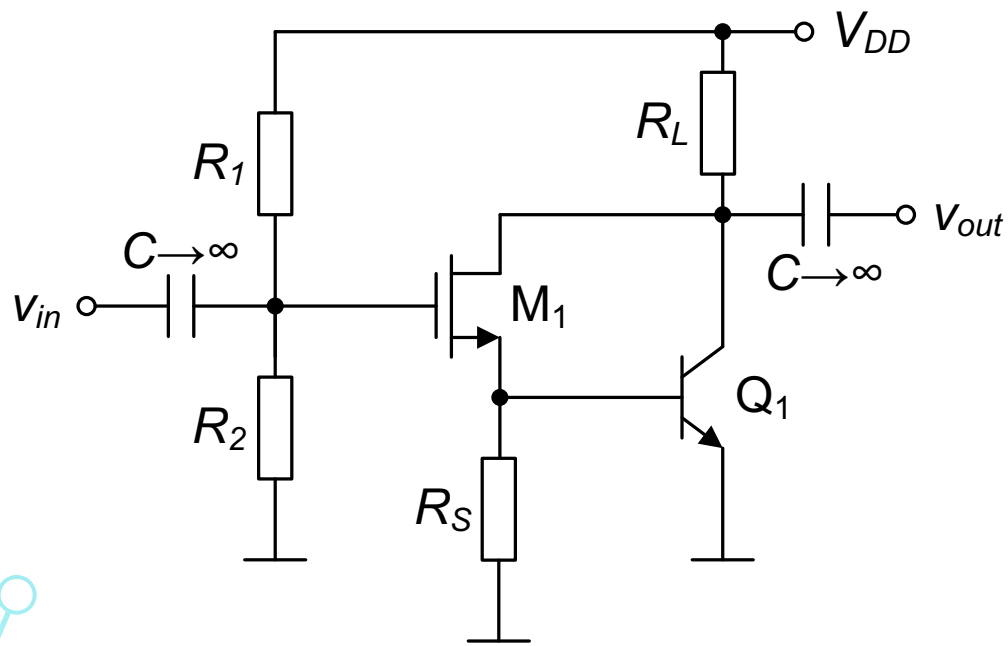ZADATAK 3 – ODREĐIVANJE NAPONSKOG POJAČANJA



$$g_{mM} = \sqrt{2\beta_M I_D} = 3.98 \text{ mS}$$



$$r_{ds} = \frac{1}{\lambda I_D} = 27.78 \text{ k}\Omega$$

$$g_{mB} = \frac{I_C}{V_T} = 80 \text{ mS}$$


$$r_{ce} = \frac{V_A}{I_C} = 10 \text{ k}\Omega$$

$$r_{\pi} = \frac{\beta_B}{g_{mB}} = 1.25 \text{ k}\Omega$$

ZADATAK 3 – ODREĐIVANJE NAPONSKOG POJAČANJA

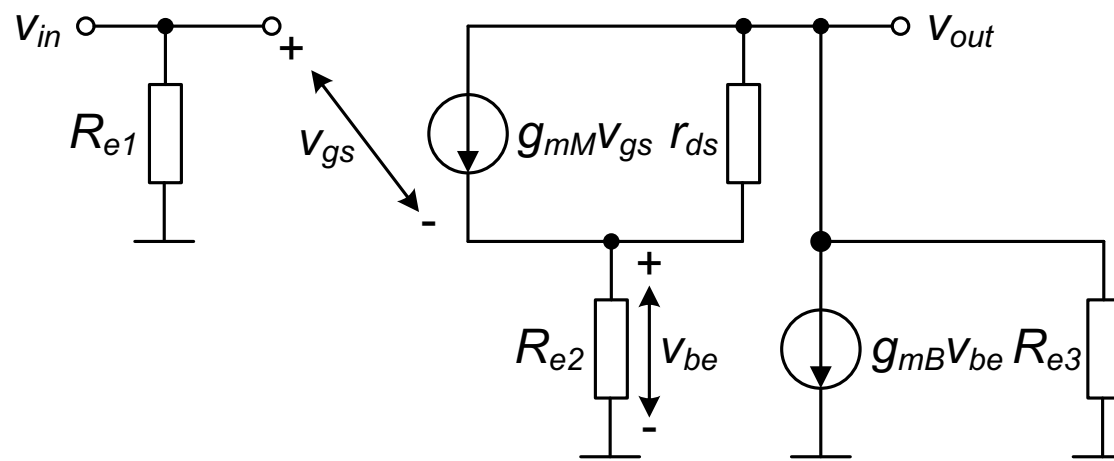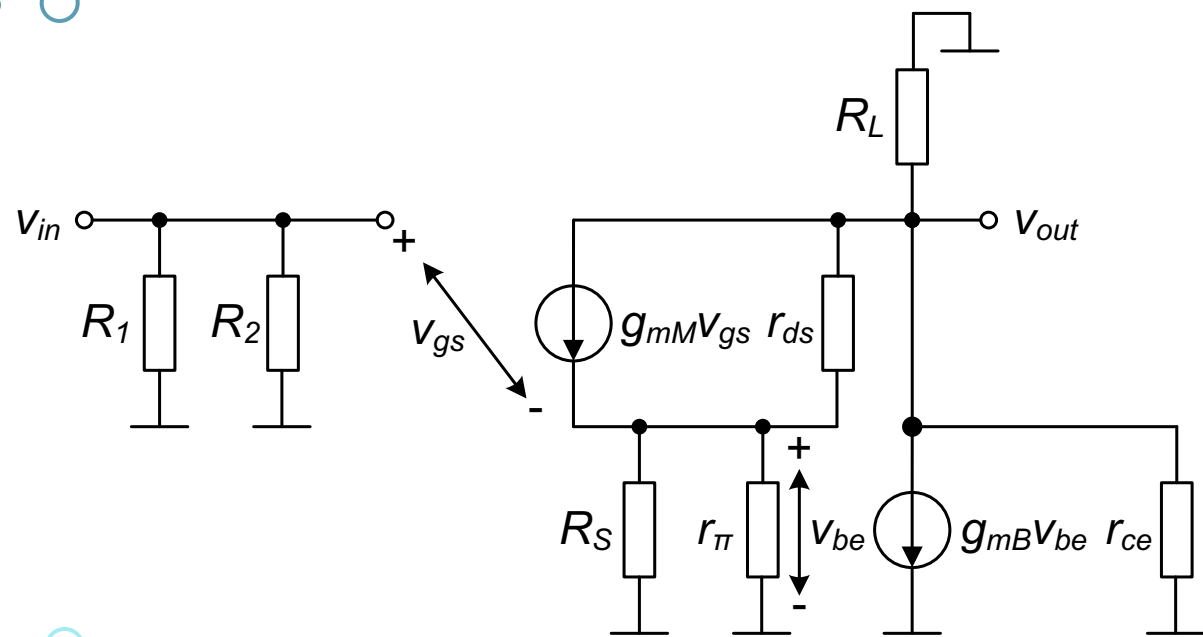

ZADATAK 3

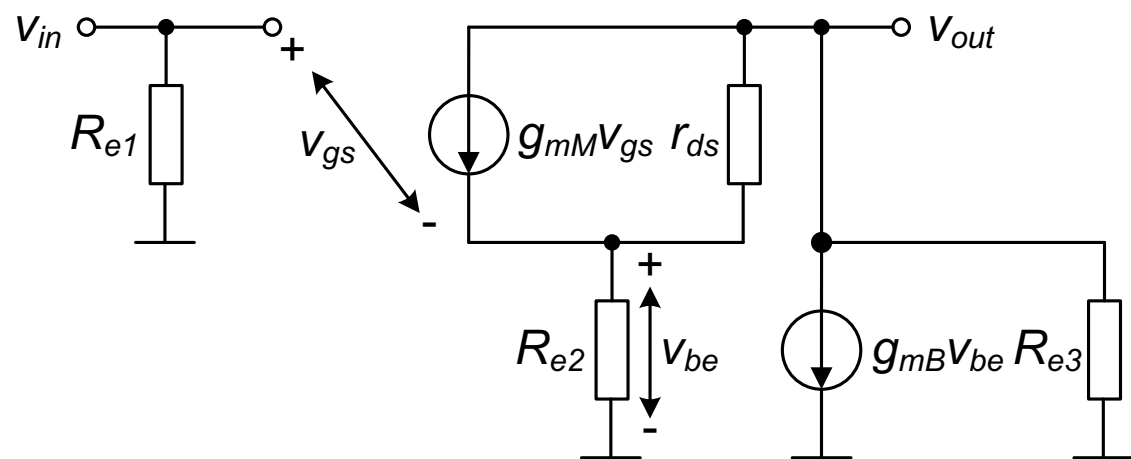


$$R_{e1} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{e2} = \frac{R_S r_\pi}{R_S + r_\pi} = 0.55 \text{ k}\Omega$$

$$R_{e3} = \frac{R_L r_{ce}}{R_L + r_{ce}} = 0.91 \text{ k}\Omega$$

ZADATAK 3

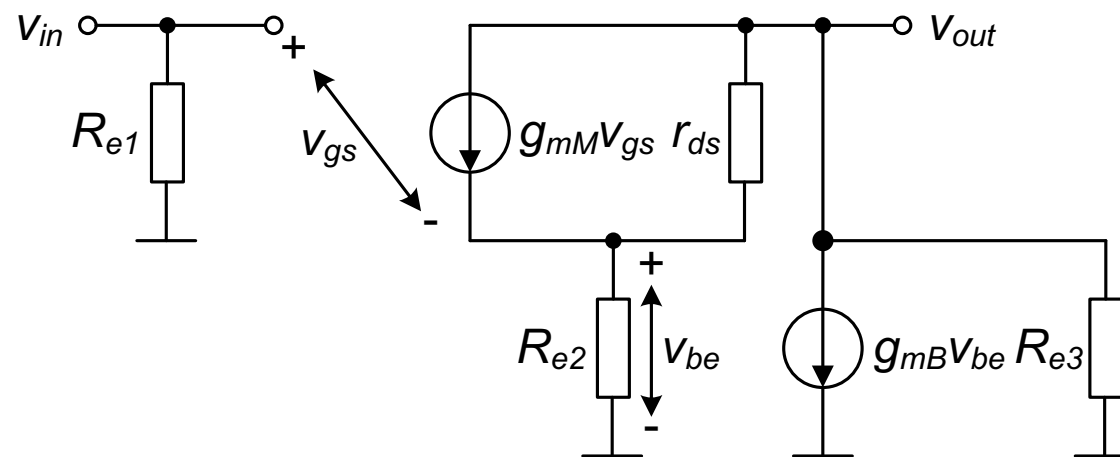

$$g_{mM}v_{gs} + \frac{v_{out} - v_{be}}{r_{ds}} = \frac{v_{be}}{R_{e2}}$$

$$g_{mB}v_{be} + \frac{v_{out}}{R_{e3}} + \frac{v_{be}}{R_{e2}} = 0 \Rightarrow v_{be} = -\frac{v_{out}}{\left(g_{mB} + \frac{1}{R_{e2}}\right)R_{e3}} = -\frac{R_{e2}v_{out}}{(g_{mB}R_{e2} + 1)R_{e3}}$$

$$g_{mM}(v_{in} - v_{be}) + \frac{v_{out} - v_{be}}{r_{ds}} = \frac{v_{be}}{R_{e2}}$$

ZADATAK 3

$$v_{be} = -\frac{R_{e2}v_{out}}{(g_{mB}R_{e2} + 1)R_{e3}}$$

$$g_{mM}(v_{in} - v_{be}) + \frac{v_{out} - v_{be}}{r_{ds}} = \frac{v_{be}}{R_{e2}}$$

$$g_{mM}r_{ds} \gg 1:$$

$$g_{mM}v_{in} + \frac{v_{out}}{r_{ds}} = v_{be} \left(g_{mM} + \frac{1}{r_{ds}} + \frac{1}{R_{e2}} \right) \approx v_{be} \left(g_{mM} + \frac{1}{R_{e2}} \right) = v_{be} \frac{g_{mM}R_{e2} + 1}{R_{e2}}$$

$$v_{in} = -\frac{1}{g_{mM}} \left(\frac{g_{mM}R_{e2} + 1}{(g_{mB}R_{e2} + 1)R_{e3}} + \frac{1}{r_{ds}} \right) v_{out}$$

$$g_{mB}R_{e2} \gg 1:$$

$$v_{in} = -\frac{1}{g_{mM}} \left(\frac{g_{mM}R_{e2} + 1}{g_{mB}R_{e2}R_{e3}} + \frac{1}{r_{ds}} \right) v_{out}$$

ZADATAK 3

$$v_{in} = -\frac{1}{g_{mM}} \left(\frac{g_{mM}R_{e2} + 1}{g_{mB}R_{e2}R_{e3}} + \frac{1}{r_{ds}} \right) v_{out}$$

$$A_v = \frac{v_{out}}{v_{in}} = - \left[\left(\frac{1}{g_{mB}R_{e3}} + \frac{1}{g_{mM}g_{mB}R_{e2}R_{e3}} + \frac{1}{g_{mM}r_{ds}} \right) \right]^{-1} = -34.41$$