




VJEŽBE 8

OSNOVE ELEKTRONIKE, ETR, IV SEMESTAR



DOC. DR MILENA ERCEG

ZADATAK 1


Za kolo prikazano na slici izračunati struju I_{OUT} . Bipolarni tranzistori su identičnih karakteristika, $V_{Ai} = V_A \rightarrow \infty$, $V_{Ti} = V_T = 26 \text{ mV}$, $I_{Si} = I_S$, $\beta_i = \beta \rightarrow \infty$, $i = 1, 2$, struja strujnog izvora $I_{REF} = 10 \mu\text{A}$ i otpornost $R = 12 \text{ k}\Omega$. Ukoliko strujno pojačanje β i *Early*-jev napon imaju konačnu vrijednost, odrediti izlaznu otpornost kola. Bipolarni tranzistor Q_2 je u direktnom aktivnom režimu.

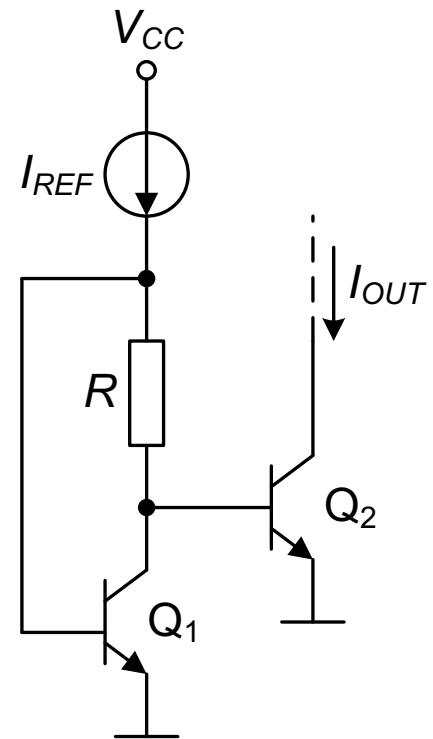

ZADATAK 1 – DC ANALIZA

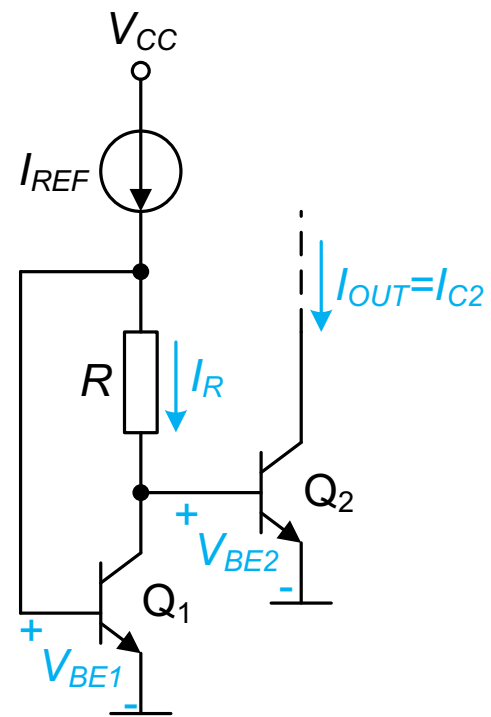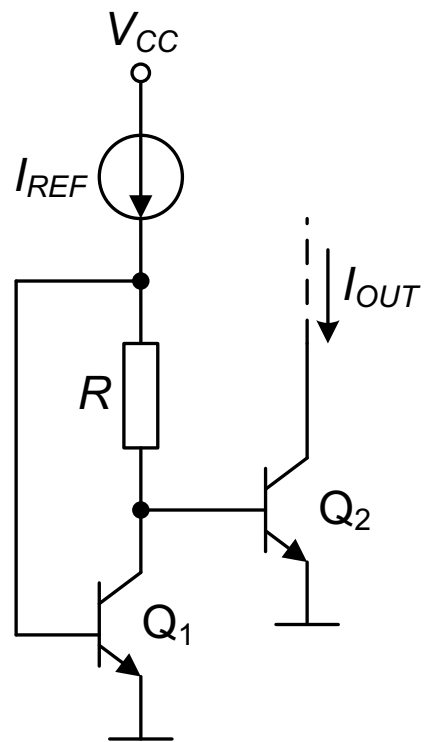

ZADATAK 1 – DC ANALIZA

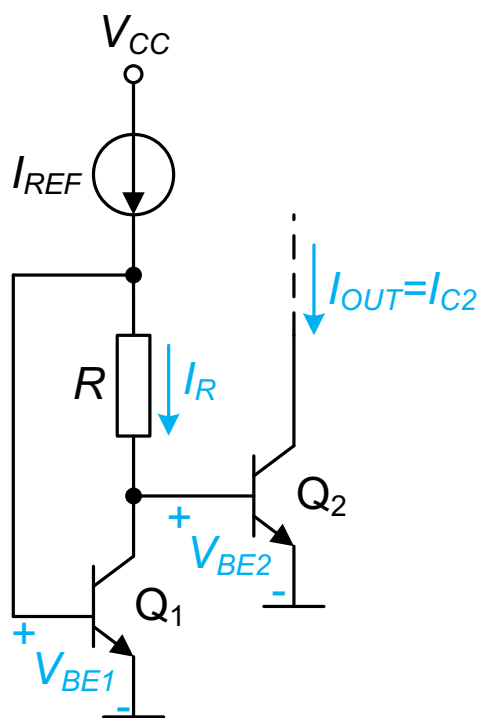

$$I_{OUT} = I_{C2} = I_{S2} e^{\frac{V_{BE2}}{V_T}}$$

$$\beta \rightarrow \infty \Rightarrow I_{C1} \approx I_{REF}, I_{B1} \rightarrow 0$$

$$V_{BE2} = V_{BE1} - R I_R \approx V_{BE1} - R I_{REF}$$



$$I_{OUT} = I_{S2} e^{\frac{V_{BE1} - R I_{REF}}{V_T}} = I_{S1} e^{\frac{V_{BE1}}{V_T}} e^{\frac{-R I_{REF}}{V_T}} = I_{C1} e^{\frac{-R I_{REF}}{V_T}}$$

$$I_{OUT} \approx I_{REF} e^{\frac{-R I_{REF}}{V_T}} = 98.98 \text{ nA}$$


$$V_{CE1} = V_{BE2}$$

Slijedi da je i BJT Q_1 u direktnom aktivnom režimu.

ZADATAK 1 – AC ANALIZA

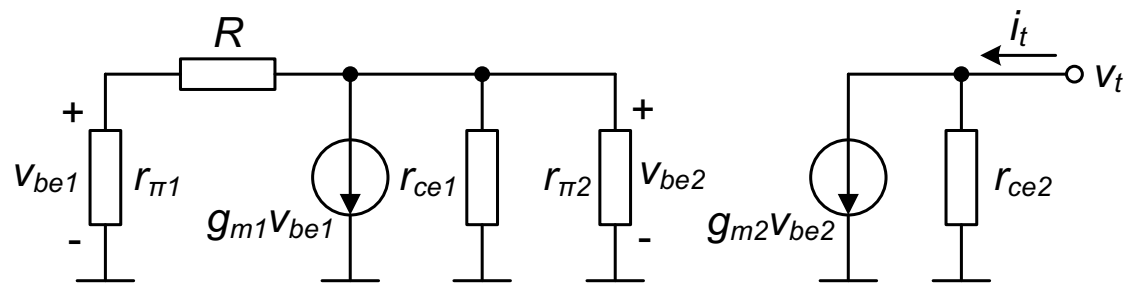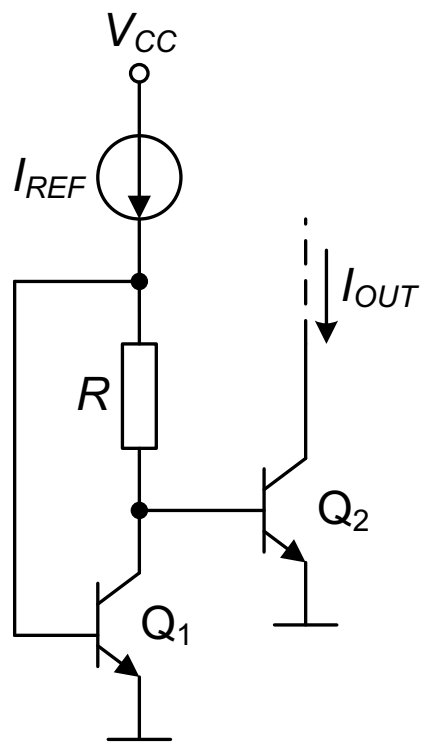

ZADATAK 1 – AC ANALIZA

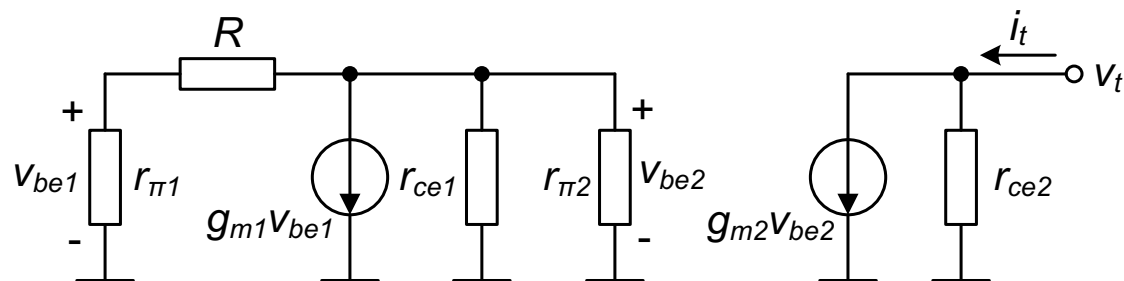

$$\frac{v_{be1}}{r_{\pi1}} + g_{m1}v_{be1} + \frac{v_{be2}}{r_{ce1}} + \frac{v_{be2}}{r_{\pi2}} = 0$$

$$v_{be1} = \frac{r_{\pi1}}{r_{\pi1} + R} v_{be2}$$


$$\left[\frac{r_{\pi1}}{r_{\pi1} + R} \left(\frac{1}{r_{\pi1}} + g_{m1} \right) + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi2}} \right] v_{be2} = 0$$

$$\Rightarrow v_{be1} = 0, v_{be2} = 0$$



$$R_{out} = \frac{v_t}{i_t} = r_{ce2}$$

ZADATAK 2


Za kolo prikazano na slici izračunati odnos otpornosti (R_1 / R_2) tako da izlazna struja I_{OUT} ne zavisi od napona baza-emitor. Bipolarni tranzistori su identičnih karakteristika, $V_{Ai} = V_A \rightarrow \infty$, $V_{Ti} = V_T$, $I_{Si} = I_S$, $\beta_i = \beta$, $i = \overline{1,4}$. Bipolarni tranzistor Q_2 je u direktnom aktivnom režimu.

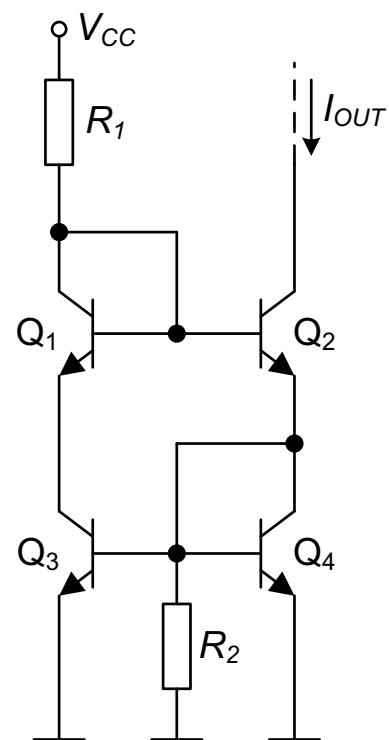

ZADATAK 2

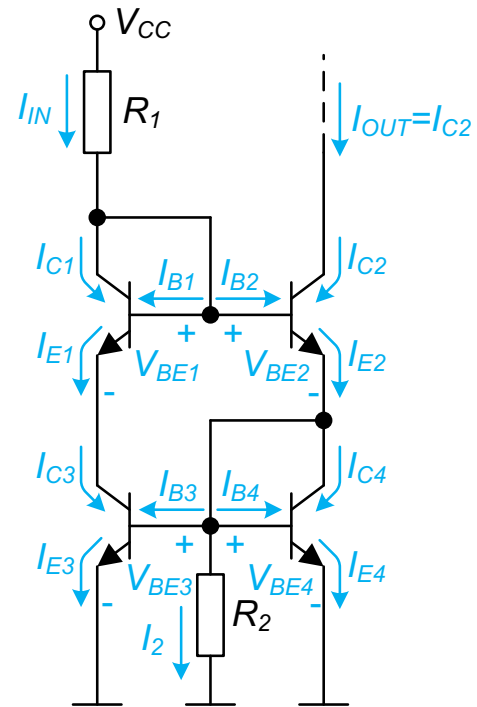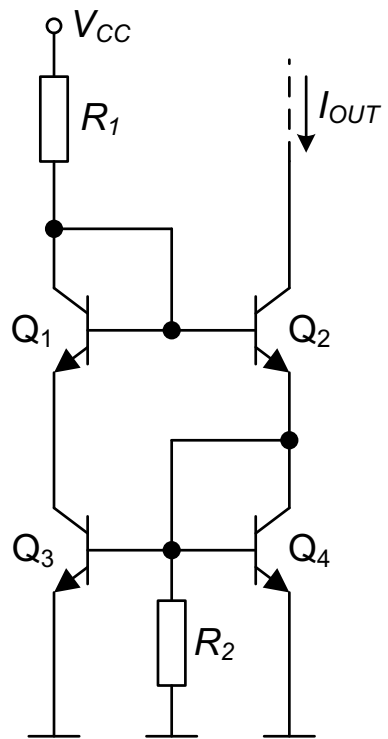

ZADATAK 2

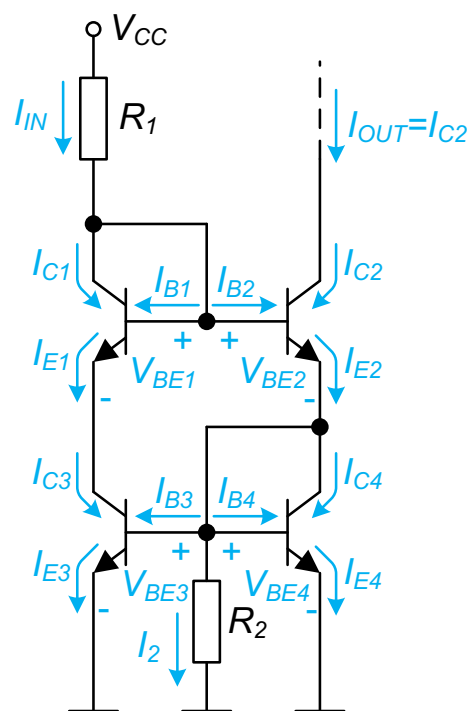

$$V_{CE1} = V_{BE1}$$

$$V_{CE3} = -V_{BE1} + V_{BE2} + V_{BE4}$$

$$V_{CE4} = V_{BE4}$$


Slijedi da su i bipolarni tranzistori Q_1 , Q_3 i Q_4 takođe u direktnom aktivnom režimu.

$$I_{OUT} = I_{C2} = \beta I_{B2}$$

$$I_{B2} = I_{IN} - I_{C1} - I_{B1} = I_{IN} - I_{E1} = I_{IN} - I_{C3}$$

$$I_{IN} = \frac{V_{CC} - V_{BE2} - V_{BE4}}{R_1}$$

ZADATAK 2

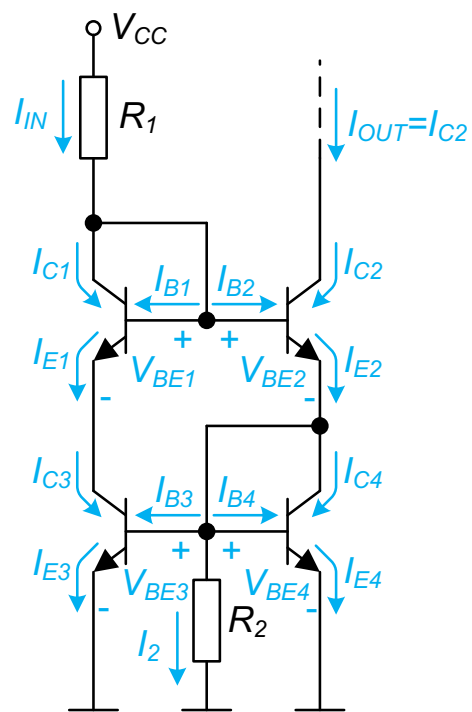

$$V_{BE3} = V_{BE4} \Rightarrow I_{C3} = I_{C4}$$

$$I_{E1} = I_{C3} = I_{C4}$$


$$I_{C4} = I_{E2} - I_{B3} - I_{B4} - I_2 = I_{E2} - 2I_{B4} - \frac{V_{BE4}}{R_2}$$

$$I_{C4} = (\beta + 1)I_{B2} - 2I_{B4} - \frac{V_{BE4}}{R_2}$$

$$(\beta + 2)I_{B4} = (\beta + 1)I_{B2} - \frac{V_{BE4}}{R_2}$$

$$I_{C4} = \frac{\beta}{\beta + 2} \left[(\beta + 1)I_{B2} - \frac{V_{BE4}}{R_2} \right]$$

ZADATAK 2

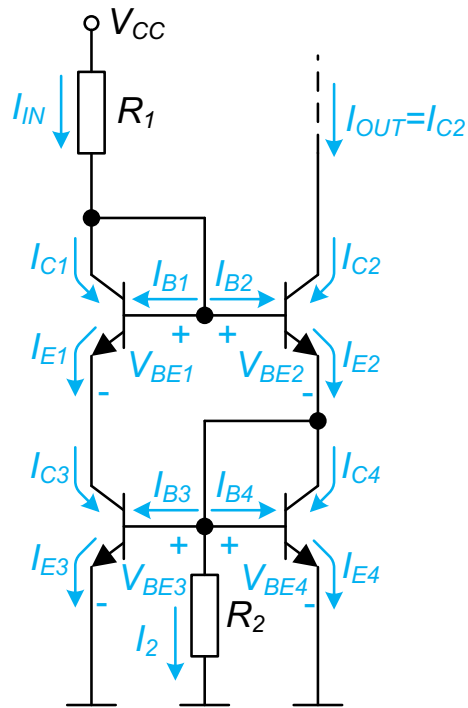

$$I_{B2} = I_{IN} - I_{C1} - I_{B1} = I_{IN} - I_{E1} = I_{IN} - I_{C3}$$

$$I_{C3} = I_{C4} = \frac{\beta}{\beta + 2} \left[(\beta + 1) I_{B2} - \frac{V_{BE4}}{R_2} \right]$$


$$I_{B2} = \frac{V_{CC} - V_{BE2} - V_{BE4}}{R_1} - \frac{\beta}{\beta + 2} \left[(\beta + 1) I_{B2} - \frac{V_{BE4}}{R_2} \right]$$

$$I_{B2} = \frac{\beta + 2}{\beta^2 + 2\beta + 2} \left(\frac{V_{CC} - V_{BE2} - V_{BE4}}{R_1} + \frac{\beta}{\beta + 2} \frac{V_{BE4}}{R_2} \right)$$

$$I_{OUT} = \beta I_{B2}$$

$$I_{OUT} = \beta \frac{\beta + 2}{\beta^2 + 2\beta + 2} \left(\frac{V_{CC} - V_{BE2} - V_{BE4}}{R_1} + \frac{\beta}{\beta + 2} \frac{V_{BE4}}{R_2} \right)$$

ZADATAK 2

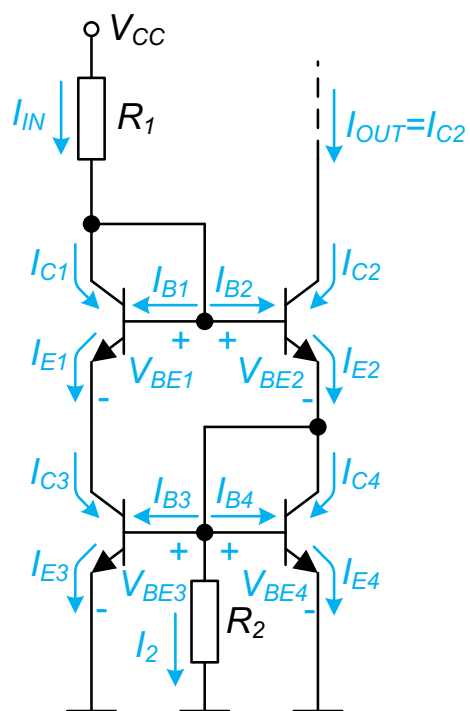

$$I_{OUT} = \beta \frac{\beta + 2}{\beta^2 + 2\beta + 2} \left(\frac{V_{CC} - V_{BE2} - V_{BE4}}{R_1} + \frac{\beta}{\beta + 2} \frac{V_{BE4}}{R_2} \right)$$

$$\frac{-V_{BE2} - V_{BE4}}{R_1} + \frac{\beta}{\beta + 2} \frac{V_{BE4}}{R_2} = 0$$


$$\frac{R_1}{R_2} = \frac{\beta + 2}{\beta} \frac{V_{BE2} + V_{BE4}}{V_{BE4}} \approx 2$$

Ukoliko se odnos otpornosti (R_1 / R_2) izabere prema prethodnoj relaciji, izlazna struja je data sljedećim izrazom:



$$I_{OUT} = \beta \frac{\beta + 2}{\beta^2 + 2\beta + 2} \frac{V_{CC}}{R_1} \approx \frac{V_{CC}}{R_1}$$

ZADATAK 3


Za kolo prikazano na slici izračunati otpornost R_2 tako da izlazna struja iznosi $I_{OUT} = 10 \mu\text{A}$. Poznat je napon napajanja kola $V_{CC} = 30 \text{ V}$ i otpornost $R_1 = 29.3 \text{ k}\Omega$. Bipolarni tranzistori su identičnih karakteristika, $V_{Ai} = V_A \rightarrow \infty$, $V_{Ti} = V_T = 26 \text{ mV}$, $I_{Si} = I_S$, $\beta_i = \beta \rightarrow \infty$, $i = 1, 2$. Bipolarni tranzistor Q_2 je u direktnom aktivnom režimu. Ukoliko *Early*-jev napon V_A i strujno pojačanje β imaju konačnu vrijednost, odrediti izlaznu otpornost kola.

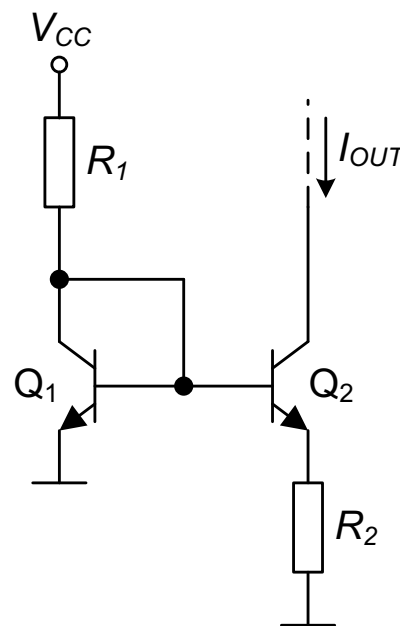

ZADATAK 3 – DC ANALIZA

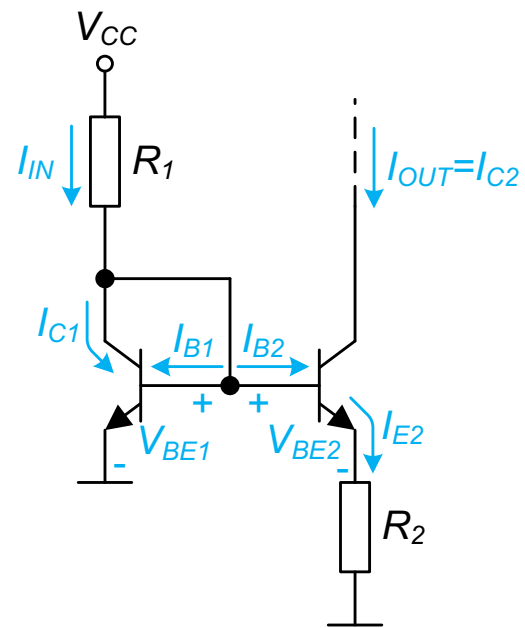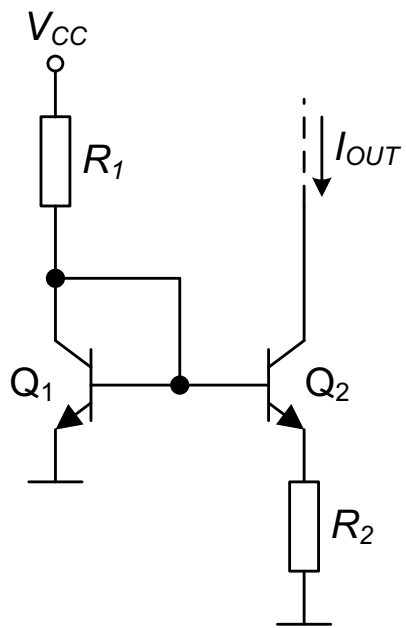

ZADATAK 3 – DC ANALIZA

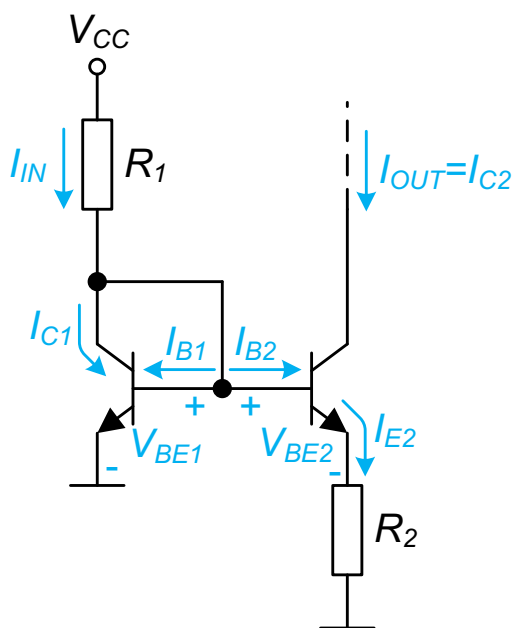

$$V_{CE1} = V_{BE1}$$

Slijedi da je i BJT Q_1 u direktnom aktivnom režimu.

$$I_{OUT} = I_{S2} e^{\frac{V_{BE2}}{V_T}} = I_{S2} e^{\frac{V_{BE1} - R_2 I_{E2}}{V_T}}$$


$$\beta \rightarrow \infty \Rightarrow I_{C2} \approx I_{E2}, I_{C1} \approx I_{E1}, I_{B1}, I_{B2} \rightarrow 0$$

$$I_{C1} \approx I_{IN} = \frac{V_{CC} - V_{BE1}}{R_1} = 1 \text{ mA}$$

$$I_{OUT} = I_{S2} e^{\frac{V_{BE1} - R_2 I_{OUT}}{V_T}} = I_{S1} e^{\frac{V_{BE1}}{V_T}} e^{\frac{-R_2 I_{OUT}}{V_T}} = I_{C1} e^{\frac{-R_2 I_{OUT}}{V_T}}$$

$$I_{OUT} = \frac{V_{CC} - V_{BE1}}{R_1} e^{\frac{-R_2 I_{OUT}}{V_T}}$$

ZADATAK 3 – DC ANALIZA


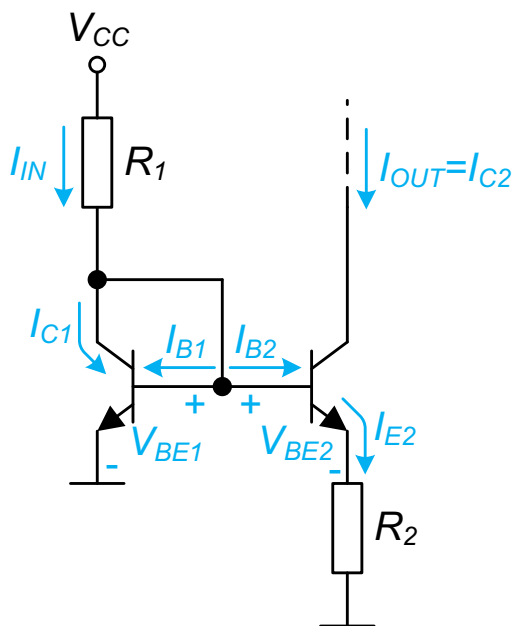


$$I_{OUT} = \frac{V_{CC} - V_{BE1}}{R_1} e^{\frac{-R_2 I_{OUT}}{V_T}}$$


$$R_2 = \frac{V_T}{I_{OUT}} \ln \left(\frac{V_{CC} - V_{BE1}}{R_1 I_{OUT}} \right)$$

Ukoliko je napon $V_{BE1} = 0.7$ V, otpornost R_2 će biti približno jednaka $11.97 \text{ k}\Omega$. Treba napomenuti da varijacija napona V_{BE} za $\pm 10 \%$ ne utiče značajno na rezultat jer je napon napajanja 30 V.

ZADATAK 3 – AC ANALIZA

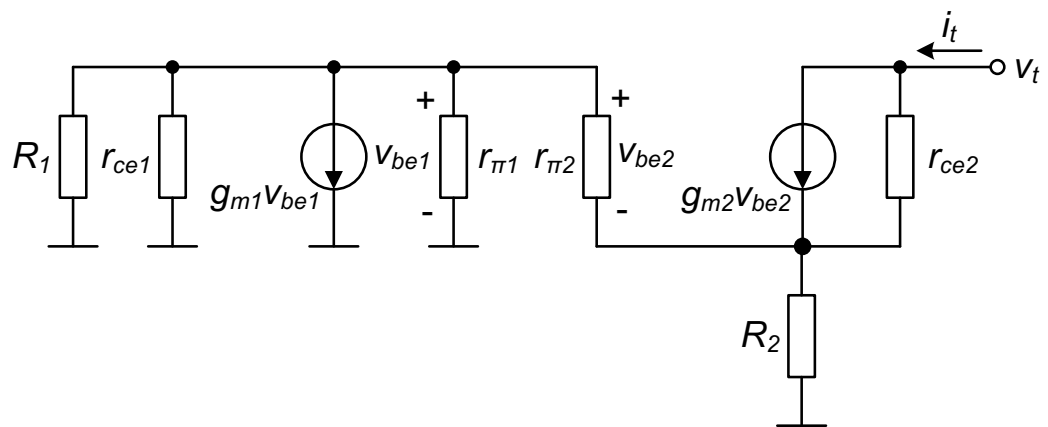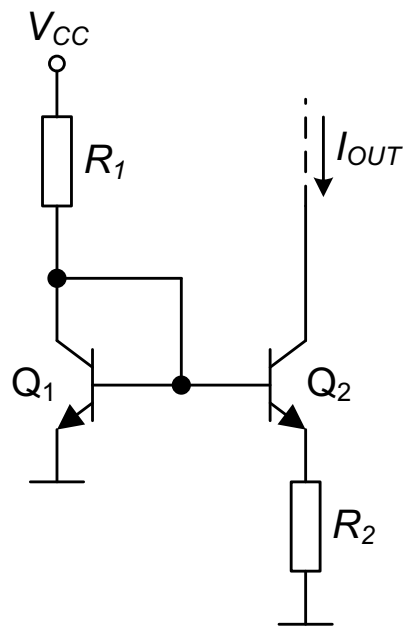

ZADATAK 3 – AC ANALIZA

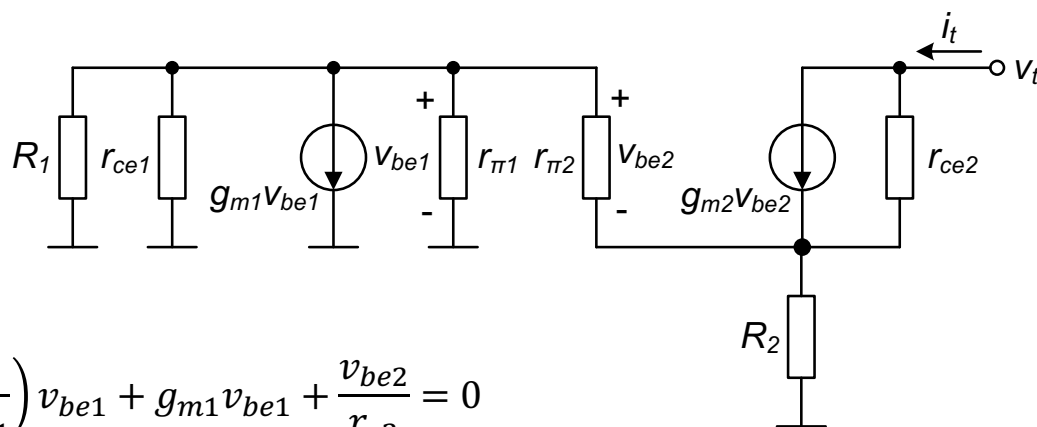


$$\left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}}\right)v_{be1} + g_{m1}v_{be1} + \frac{v_{be2}}{r_{\pi2}} = 0$$

$$v_{be2} = -r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1}\right)v_{be1}$$

$$i_t + \frac{v_{be2}}{r_{\pi2}} = \frac{v_{be1} - v_{be2}}{R_2} \Rightarrow i_t = \frac{v_{be1}}{R_2} - \left(\frac{1}{r_{\pi2}} + \frac{1}{R_2}\right)v_{be2}$$

$$i_t = \left[\frac{1}{R_2} + \left(\frac{1}{r_{\pi2}} + \frac{1}{R_2}\right)r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1}\right)\right]v_{be1}$$

ZADATAK 3 – AC ANALIZA

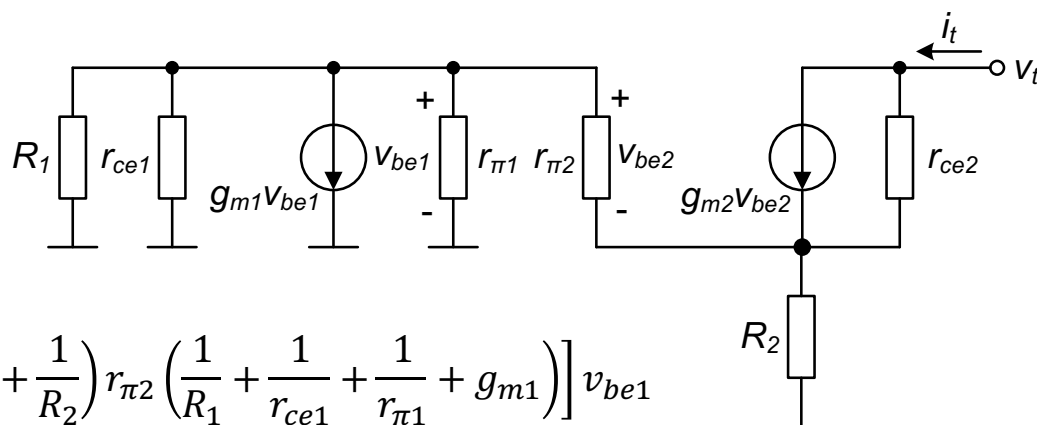


$$i_t = \left[\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce 1}} + \frac{1}{r_{\pi 1}} + g_{m1} \right) \right] v_{be1}$$

$$v_{be1} = \frac{i_t}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce 1}} + \frac{1}{r_{\pi 1}} + g_{m1} \right)}$$

$$i_t = g_{m2}v_{be2} + \frac{v_t - v_{be1} + v_{be2}}{r_{ce2}} = \frac{v_t - v_{be1}}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}} \right) v_{be2}$$

$$i_t = \frac{v_t - v_{be1}}{r_{ce2}} - \left(g_{m2} + \frac{1}{r_{ce2}} \right) r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce 1}} + \frac{1}{r_{\pi 1}} + g_{m1} \right) v_{be1}$$

ZADATAK 3 – AC ANALIZA

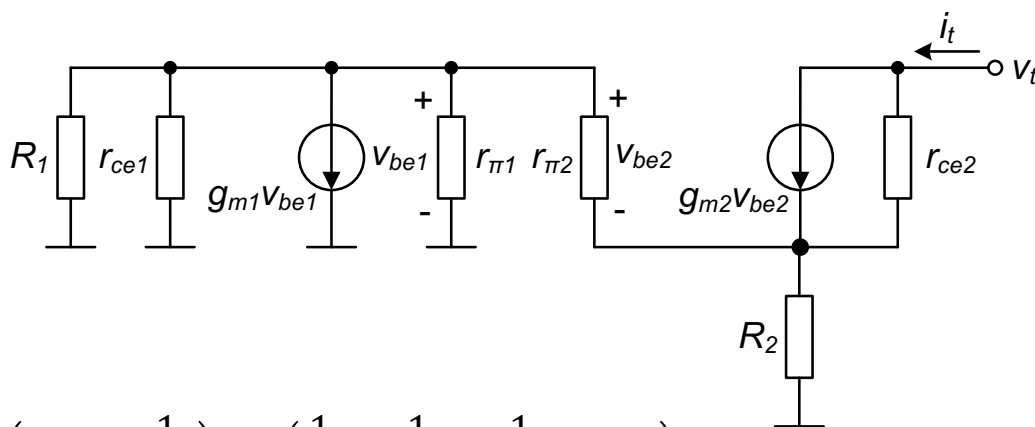


$$i_t = \frac{v_t - v_{be1}}{r_{ce2}} - \left(g_{m2} + \frac{1}{r_{ce2}} \right) r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1} \right) v_{be1}$$

$$i_t = \frac{v_t}{r_{ce2}} - \left[\frac{1}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}} \right) r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1} \right) \right] v_{be1}$$

$$i_t = \frac{v_t}{r_{ce2}} - \frac{\frac{1}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}} \right) r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi2}} + \frac{1}{R_2} \right) r_{\pi2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi1}} + g_{m1} \right)} i_t$$


ZADATAK 3 – AC ANALIZA

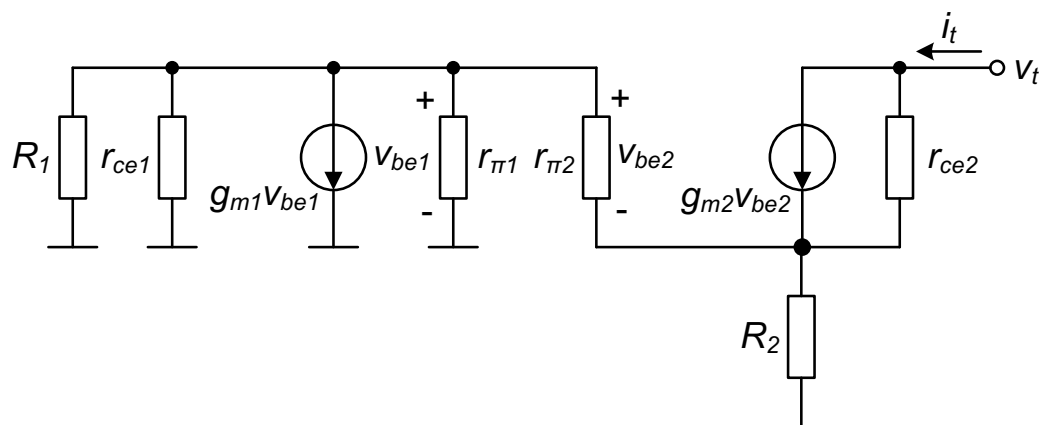

$$i_t = \frac{v_t}{r_{ce2}} - \frac{\frac{1}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}}\right)r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1}\right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2}\right)r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1}\right)} i_t$$

$$R_{out} = \frac{v_t}{i_t} = r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}}\right)r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1}\right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2}\right)r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1}\right)} \right]$$

ZADATAK 3 – AC ANALIZA

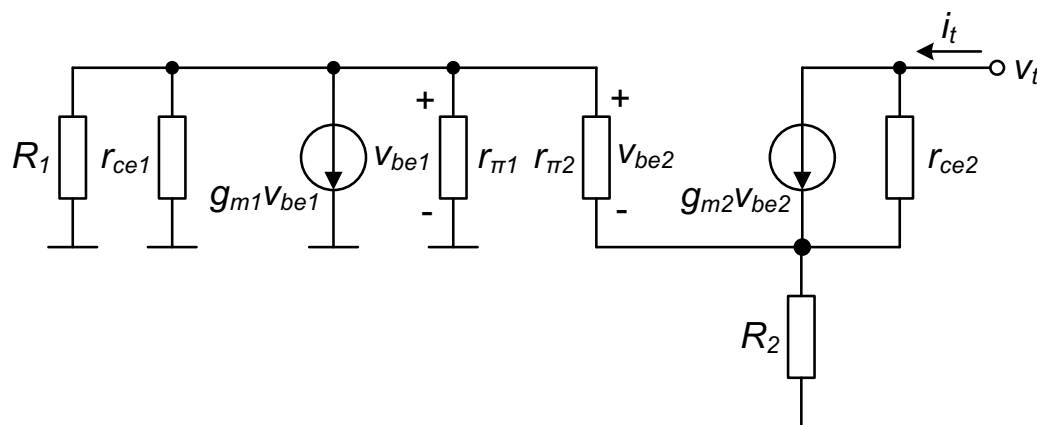

$$R_{out} = \frac{v_t}{i_t} = r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + \left(g_{m2} + \frac{1}{r_{ce2}} \right) r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + \frac{1}{r_{ce1}} + \frac{1}{r_{\pi 1}} + g_{m1} \right)} \right]$$

$$g_{m1}r_{\pi 1} \gg 1, g_{m1}r_{ce1} \gg 1, g_{m2}r_{\pi 2} \gg 1, g_{m2}r_{ce2} \gg 1 :$$

$$R_{out} \approx r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + g_{m2}r_{\pi 2} \left(\frac{1}{R_1} + g_{m1} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + g_{m1} \right)} \right]$$

ZADATAK 3 – AC ANALIZA

$$R_{out} \approx r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + g_{m2} r_{\pi 2} \left(\frac{1}{R_1} + g_{m1} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + g_{m1} \right)} \right]$$

Kako je izlazna struja I_{OUT} 100 puta manja od ulazne struje I_{IN} , transkonduktansa BJT-a Q_1 je 100 puta veća od transkonduktanse BJT-a Q_2 , dok je izlazna otpornost BJT-a Q_1 100 puta manja od izlazne otpornosti BJT-a Q_2 . Slijedi da se izraz za izlaznu otpornost dalje može aproksimirati:

$$\begin{aligned} R_{out} &\approx r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + g_{m2} r_{\pi 2} \left(\frac{1}{R_1} + 100g_{m2} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + 100g_{m2} \right)} \right] \approx r_{ce2} \left[1 + \frac{g_{m2}}{\frac{1}{R_2 r_{\pi 2} \left(\frac{1}{R_1} + 100g_{m2} \right)} + \frac{1}{r_{\pi 2}} + \frac{1}{R_2}} \right] \\ &\approx r_{ce2} \left(1 + \frac{g_{m2}}{\frac{1}{r_{\pi 2}} + \frac{1}{R_2}} \right) \end{aligned}$$

ZADATAK 3 – AC ANALIZA

$$R_{out} \approx r_{ce2} \left[1 + \frac{\frac{1}{r_{ce2}} + g_{m2} r_{\pi 2} \left(\frac{1}{R_1} + 100 g_{m2} \right)}{\frac{1}{R_2} + \left(\frac{1}{r_{\pi 2}} + \frac{1}{R_2} \right) r_{\pi 2} \left(\frac{1}{R_1} + 100 g_{m2} \right)} \right] \approx r_{ce2} \left[1 + \frac{g_{m2}}{\frac{1}{R_2 r_{\pi 2} \left(\frac{1}{R_1} + 100 g_{m2} \right)} + \frac{1}{r_{\pi 2}} + \frac{1}{R_2}} \right]$$
$$\approx r_{ce2} \left(1 + \frac{g_{m2}}{\frac{1}{r_{\pi 2}} + \frac{1}{R_2}} \right)$$

Kako je kolektorska struja BJT-a Q_2 : $I_{C2} = 10 \mu\text{A}$, transkonduktansa iznosi $g_{m2} = (I_{C2} / V_T) = 0.385 \text{ mS}$. Za strujno pojačanje β reda stotinu, otpornost $r_{\pi 2}$ je reda 2-3 stotine $\text{k}\Omega$, što je značajno veće od R_2 . Konačan izraz za izlaznu otpornost bi bio:

$$R_{out} \approx r_{ce2}(1 + g_{m2}R_2) = 5.61r_{ce2}$$