
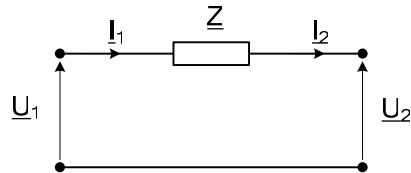


1. Odrediti „a“ parametre sljedećih mreža sa dva para krajeva:


a)

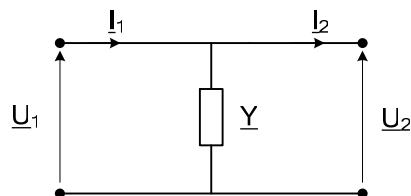


b)





c)

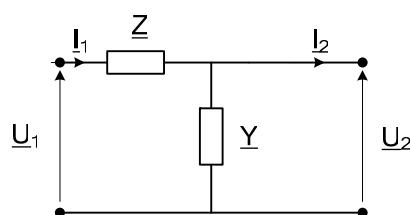


d)

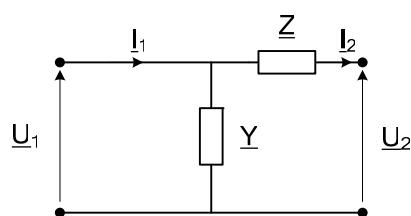

e)

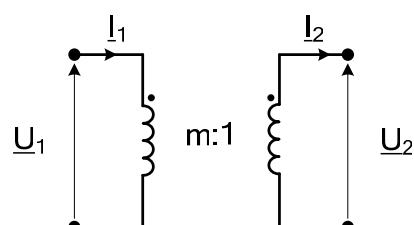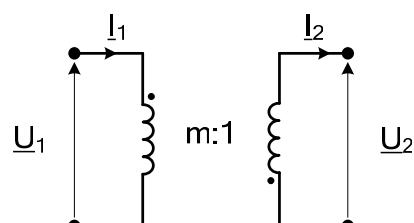

f)

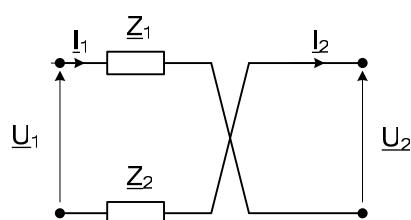

R

a)

$$\left. \begin{array}{l} \underline{U}_1 = \underline{U}_2 + \underline{Z}\underline{I}_2 \\ \underline{I}_1 = \underline{I}_2 \end{array} \right\} \rightarrow \begin{bmatrix} \underline{U}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} \underline{U}_2 \\ \underline{I}_2 \end{bmatrix} \rightarrow \begin{array}{ll} a_{11} = 1 & a_{12} = \underline{Z} \\ a_{21} = 0 & a_{22} = 1 \end{array}$$

b)

$$\left. \begin{array}{l} \underline{U}_1 = \underline{U}_2 \\ \underline{I}_1 = \underline{Y}\underline{U}_2 + \underline{I}_2 \end{array} \right\} \rightarrow \begin{bmatrix} \underline{U}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} \underline{U}_2 \\ \underline{I}_2 \end{bmatrix} \rightarrow \begin{array}{ll} a_{11} = 1 & a_{12} = 0 \\ a_{21} = \underline{Y} & a_{22} = 1 \end{array}$$

c)

$$\left. \begin{array}{l} \underline{U}_1 = \underline{Z}\underline{I}_1 + \underline{U}_2 \\ \underline{I}_1 = \underline{Y}\underline{U}_2 + \underline{I}_2 \end{array} \right\} \rightarrow \begin{bmatrix} \underline{U}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} \underline{Z}(\underline{Y}\underline{U}_2 + \underline{I}_2) + \underline{U}_2 \\ \underline{Y}\underline{U}_2 + \underline{I}_2 \end{bmatrix} \rightarrow$$

$$\left. \begin{array}{l} \underline{U}_1 = (\underline{Z}\underline{Y} + 1)\underline{U}_2 + \underline{Z}\underline{I}_2 \\ \underline{I}_1 = \underline{Y}\underline{U}_2 + \underline{I}_2 \end{array} \right\} \rightarrow \begin{array}{ll} a_{11} = (\underline{Z}\underline{Y} + 1) & a_{12} = \underline{Z} \\ a_{21} = \underline{Y} & a_{22} = 1 \end{array}$$

d)

$$\left. \begin{array}{l} \underline{U}_1 = \underline{Z}\underline{I}_2 + \underline{U}_2 \\ \underline{I}_1 = \underline{Y}(\underline{Z}\underline{I}_2 + \underline{U}_2) + \underline{I}_2 \end{array} \right\} \rightarrow \begin{bmatrix} \underline{U}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} \underline{U}_2 + \underline{Z}\underline{I}_2 \\ \underline{Y}\underline{U}_2 + (\underline{Y}\underline{Z} + 1)\underline{I}_2 \end{bmatrix} \rightarrow \begin{array}{ll} a_{11} = 1 & a_{12} = \underline{Z} \\ a_{21} = \underline{Y} & a_{22} = 1 + \underline{Y}\underline{Z} \end{array}$$

e)

IT sa saglasnim krajevima

$$\left. \begin{array}{l} \underline{U}_1 = -m\underline{U}_2 \\ \underline{I}_1 = -\frac{1}{m}\underline{I}_2 \end{array} \right\} \rightarrow \begin{array}{ll} a_{11} = -m & a_{12} = 0 \\ a_{21} = 0 & a_{22} = -\frac{1}{m} \end{array}$$

IT sa nesaglasnim krajevima

$$\left. \begin{array}{l} \underline{U}_1 = m\underline{U}_2 \\ \underline{I}_1 = \frac{1}{m}\underline{I}_2 \end{array} \right\} \rightarrow \begin{array}{ll} a_{11} = m & a_{12} = 0 \\ a_{21} = 0 & a_{22} = \frac{1}{m} \end{array}$$

f)

$$\left. \begin{array}{l} \underline{U}_1 = \underline{Z}_1\underline{I}_1 - \underline{U}_2 - \underline{Z}_2\underline{I}_2 \\ \underline{I}_1 = -\underline{I}_2 \end{array} \right\} \rightarrow \begin{bmatrix} \underline{U}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} -\underline{U}_2 - (\underline{Z}_1 + \underline{Z}_2)\underline{I}_2 \\ -\underline{I}_2 \end{bmatrix} \rightarrow \begin{array}{ll} a_{11} = -1 & a_{12} = -(\underline{Z}_1 + \underline{Z}_2) \\ a_{21} = 0 & a_{22} = -1 \end{array}$$

2. Posmatra se mreža prema šemi. Da li je impedansa kola data izrazom


$$\underline{Z}_1' = \frac{\underline{Z}_{10}\underline{Z}_p + \underline{Z}_{1k}\underline{Z}_T}{\underline{Z}_p + \underline{Z}_T}, \text{ gdje su:}$$

\underline{Z}_{10} - ulazna impedansa mreže sa strane 1-1' kada su krajevi 2-2' otvoreni

\underline{Z}_{1k} - ulazna impedansa mreže sa strane 1-1' kada su krajevi 2-2' zatvoreni

\underline{Z}_T - impedansa Teveninovog generatora u odnosu na krajeve 2-2'

\underline{Z}_p - impedansa prijemnika

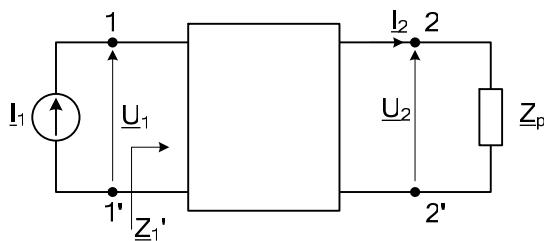

R

Ulagna impedansa na krajevima 1-1'

$$\underline{Z}_1' = \frac{\underline{U}_1}{\underline{I}_1}$$

Ako se iskoriste „a“ parametri

$$\begin{aligned}\underline{U}_1 &= \underline{a}_{11}\underline{U}_2 + \underline{a}_{12}\underline{I}_2 \quad (\#) \\ \underline{I}_1 &= \underline{a}_{21}\underline{U}_2 + \underline{a}_{22}\underline{I}_2\end{aligned}$$

A ako se još doda relacija koja definiše uslove na krajevima 2-2'

$$\underline{U}_2 = \underline{Z}_p \underline{I}_2$$

Kako se traži ulagna impedansa podijele se jednačine iz sistema (#)

$$\underline{Z}_1' = \frac{\underline{U}_1}{\underline{I}_1} = \frac{\underline{a}_{11}\underline{U}_2 + \underline{a}_{12}\underline{I}_2}{\underline{a}_{21}\underline{U}_2 + \underline{a}_{22}\underline{I}_2} = \frac{\underline{a}_{11}\underline{Z}_p \underline{I}_2 + \underline{a}_{12}\underline{I}_2}{\underline{a}_{21}\underline{Z}_p \underline{I}_2 + \underline{a}_{22}\underline{I}_2} = \frac{\underline{a}_{11}\underline{Z}_p + \underline{a}_{12}}{\underline{a}_{21}\underline{Z}_p + \underline{a}_{22}}$$

Ako se izraz podijeli sa \underline{a}_{21}

$$\underline{Z}_1' = \frac{\frac{\underline{a}_{11}}{\underline{a}_{21}}\underline{Z}_p + \frac{\underline{a}_{12}}{\underline{a}_{21}}}{\underline{Z}_p + \frac{\underline{a}_{22}}{\underline{a}_{21}}}$$


Ako se impedanse definisane u zadatku izraze preko „a“ parametara

$$\underline{Z}_{10} = \left. \frac{\underline{U}_1}{\underline{I}_1} \right|_{\underline{I}_2=0} = \frac{\underline{a}_{11}}{\underline{a}_{21}} \quad \underline{Z}_{1k} = \left. \frac{\underline{U}_1}{\underline{I}_1} \right|_{\underline{U}_2=0} = \frac{\underline{a}_{12}}{\underline{a}_{22}} \quad \underline{Z}_T = \left. \frac{\underline{U}_2}{-\underline{I}_2} \right|_{\underline{I}_1=0} = \frac{\underline{a}_{22}}{\underline{a}_{21}}$$

Zamjenom u prethodnu relaciju, dolazi se do

$$\underline{Z}_1' = \frac{\underline{Z}_{10}\underline{Z}_p + \frac{\underline{a}_{12}}{\underline{a}_{21}}\frac{\underline{a}_{22}}{\underline{a}_{22}}}{\underline{Z}_p + \frac{\underline{a}_{22}}{\underline{a}_{21}}} = \frac{\underline{Z}_{10}\underline{Z}_p + \frac{\underline{a}_{12}}{\underline{a}_{22}}\frac{\underline{a}_{22}}{\underline{a}_{21}}}{\underline{Z}_p + \underline{Z}_T} = \frac{\underline{Z}_{10}\underline{Z}_p + \underline{Z}_{1k}\underline{Z}_T}{\underline{Z}_p + \underline{Z}_T}.$$

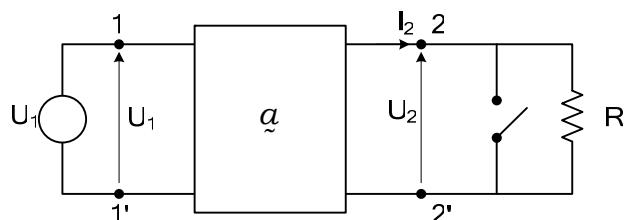3. Ako se na krajeve jedne simetrične mreže sa dva para krajeva koja se sastoji samo od otpornika priključi konstantan napon $U_1=100$ V, struje na pristupima pri kratko spojenim krajevima 2-2' su $I_{1k}=8mA$ i $I_{2k}=6mA$. Odrediti struje na krajevima kola ako je između krajeva 2-2' vezan otpornik $R=10k\Omega$.



R

Ako se napišu jednačine prema „a“ parametrima:

$$\underline{U}_1 = a_{11}\underline{U}_2 + a_{12}I_2 \quad (\#)$$

$$\underline{I}_1 = a_{21}\underline{U}_2 + a_{22}I_2$$

Uzimajući u obzir da je mreža sastavljena od otpornika, sistem jednačina se ne mora pisati u kompleksnoj formi. Takođe, kako bi se odredila tražena struja potrebno je prethodno odrediti parametre.

Kako su date struje na pristupima pri kratko spojenim krajevima 2-2' ($\underline{U}_2=0$), tada su jednačine:

$$U_1 = a_{12}I_{2k} \rightarrow a_{12} = \frac{U_1}{I_{2k}} = \frac{100}{6} = \frac{50}{3} k\Omega$$

$$I_{1k} = a_{22}I_{2k} \rightarrow a_{22} = \frac{I_{1k}}{I_{2k}} = \frac{8}{6} = \frac{4}{3}$$

Kako je u zadatku navedeno da je mreža simetrična, to važi

$$a_{11} = a_{22} = \frac{4}{3}$$

Takođe, poznato je da važi

$$\det \underline{a} = 1 \rightarrow a_{11}^2 - a_{12}a_{21} = 1 \rightarrow a_{21} = \frac{a_{11}^2 - 1}{a_{12}} = \frac{7}{150} mS$$

Sada, kada su poznati „a“ parametri moguće je odrediti nepoznatu struju uvrštavajući u sistem (#) uslove koji važe na krajevima,

$$U_1 = 100V$$

$$U_2 = RI_2$$

Kada se prethodni uslovi uvrste, dobija se


$$U_1 = a_{11}\underline{U}_2 + a_{12}I_2$$

$$\underline{I}_1 = a_{21}\underline{U}_2 + a_{22}I_2$$

$$U_1 = a_{11}RI_2 + a_{12}I_2 \rightarrow I_2 = \frac{U_1}{a_{11}R + a_{12}} = \frac{10}{3} mA$$

$$I_1 = a_{21}RI_2 + a_{22}I_2 = (a_{21}R + a_{22})I_2 = 6mA$$

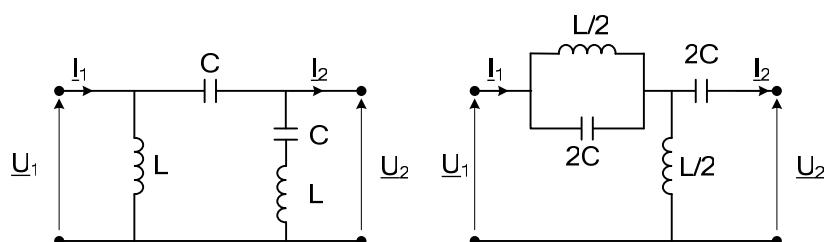4. Pokazati da su reaktivne mreže sa dva para krajeva prikazane na slici ekvivalentne.



R

Ako se posmatraju „y“ parametri,

$$\begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$

Ekvivalentnost posmatranih mreža se može dokazati ako se pokaže da su „y“ parametri jednaki. Ako se posmatra prva šema


$$\underline{I}_1 = \underline{y}_{11} \underline{U}_1 + \underline{y}_{12} \underline{U}_2$$

$$-\underline{I}_2 = \underline{y}_{21} \underline{U}_1 + \underline{y}_{22} \underline{U}_2$$

$$\underline{y}_{11} = \frac{\underline{I}_1}{\underline{U}_1} \Big|_{\underline{U}_2=0} = j\omega C + \frac{1}{j\omega L}$$

$$\underline{y}_{22} = -\frac{\underline{I}_2}{\underline{U}_2} \Big|_{\underline{U}_1=0} = j\omega C + \frac{j\omega C \frac{1}{j\omega L}}{j\omega C + \frac{1}{j\omega L}} = j\omega C + j\omega C \frac{1}{1 - \omega^2 LC} = j\omega C \frac{2 - \omega^2 LC}{1 - \omega^2 LC}$$

$$\underline{y}_{12} = \frac{\underline{I}_1}{\underline{U}_2} \Big|_{\underline{U}_1=0} = -j\omega C = \underline{y}_{21}$$

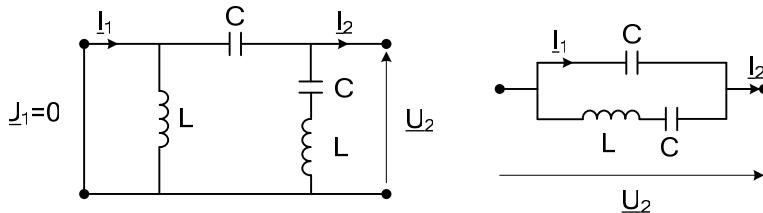


Ako se sad parametri odrede za drugu šemu iz zadatka,

$$\underline{y}_{11} = \frac{\underline{I}_1}{\underline{U}_1} \Big|_{\underline{U}_2=0} = \frac{1}{2} \left(j\omega 2C + \frac{2}{j\omega L} \right) = j\omega C + \frac{1}{j\omega L}$$

$$\underline{y}_{22} = -\frac{\underline{I}_2}{\underline{U}_2} \Big|_{\underline{U}_1=0} = \frac{\left(j\omega 2C + \frac{2}{j\omega L} + \frac{2}{j\omega L} \right) j\omega 2C}{j\omega 2C + \frac{2}{j\omega L} + \frac{2}{j\omega L} + j\omega 2C} = j\omega C \frac{4 \frac{2 - \omega^2 LC}{j\omega L}}{4 \frac{1 - \omega^2 LC}{j\omega L}} = j\omega C \frac{2 - \omega^2 LC}{1 - \omega^2 LC}$$


$$\underline{y}_{12} = \frac{\underline{I}_1}{\underline{U}_2} \Big|_{\underline{U}_1=0} = \frac{\frac{\underline{I}_1}{j\omega \frac{L}{2} \frac{1}{j2\omega C}} + \frac{1}{j2\omega C} \frac{j\omega \frac{L}{2} + \frac{j\omega L}{1 - \omega^2 LC}}{j\omega \frac{L}{2}}} {\left[\frac{j\omega \frac{L}{2} \frac{1}{j2\omega C}}{j\omega \frac{L}{2} \frac{1}{j2\omega C}} + \frac{1}{j2\omega C} \frac{j\omega \frac{L}{2}}{j\omega \frac{L}{2}} \right]} = -j\omega C = \underline{y}_{21}$$

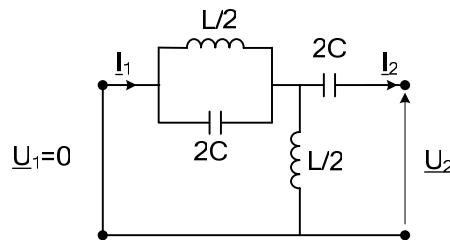

5. Data je reaktivna mreža sa dva para krajeva.

a) Odrediti impedanse ekvivalentne „T“ šeme i nacrtati njenu šemu

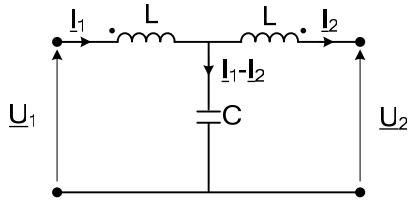b) Na šta se svodi ekvivalentna mreža u dijelu zadatka pod a) u slučaju kada je koeficijent sprege između kalemova k=1?



R

Potrebno je najprije odrediti parametre mreže sa dva para krajeva. Ako se posmatraju „a“ parametri.

$$\underline{U}_1 = \underline{a}_{11}\underline{U}_2 + \underline{a}_{12}\underline{I}_2$$

$$\underline{I}_1 = \underline{a}_{21}\underline{U}_2 + \underline{a}_{22}\underline{I}_2$$

Ako se posmatra šema, može se napisati

$$\underline{U}_1 = j\omega L\underline{I}_1 - j\omega kL\underline{I}_2 + \frac{1}{j\omega C}(\underline{I}_1 - \underline{I}_2) \quad (\#)$$

$$\underline{U}_2 = -j\omega L\underline{I}_2 + \frac{1}{j\omega C}(\underline{I}_1 - \underline{I}_2) + j\omega kL\underline{I}_1$$


Iz druge jednačine sistema (#) dobija se

$$\underline{U}_2 + j\omega L\underline{I}_2 + \frac{1}{j\omega C}\underline{I}_2 = \left(\frac{1}{j\omega C} + j\omega kL \right) \underline{I}_1 \rightarrow \underline{I}_1 = \underbrace{\frac{1}{j\omega kL + \frac{1}{j\omega C}}}_{\underline{a}_{21}} \underline{U}_2 + \underbrace{\frac{1 - \omega^2 LC}{1 - \omega^2 kLC}}_{\underline{a}_{22}} \underline{I}_2$$

Zamjenom u prvu jednačinu sistema (#) dolazi se do

$$\underline{U}_1 = \underbrace{\frac{1 - \omega^2 LC}{1 - \omega^2 kLC}}_{\underline{a}_{11}} \underline{U}_2 + \underbrace{\frac{1}{j\omega C} \frac{\omega^2 LC(k-1)(2-(k+1)\omega^2 LC)}{1 - \omega^2 kLC}}_{\underline{a}_{12}} \underline{I}_2$$

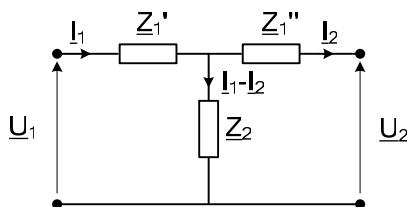Iz jednakosti $\underline{a}_{11} = \underline{a}_{22}$ zaključuje se da je mreža simetrična. Ako se nacrta proizvoljna „T“ šema



i napišu jednačine za napon i struju na početku:

$$\underline{U}_1 = \underline{Z}_1' \underline{I}_1 + \underline{Z}_1'' \underline{I}_2 + \underline{U}_2$$

$$\underline{I}_1 = \frac{\underline{U}_2 + \underline{Z}_1'' \underline{I}_2}{\underline{Z}_2} + \underline{I}_2$$

Zamjenom druge jednačine, prethodnog sistema jednačina, u prvu, dobija se:

$$\underline{U}_1 = \left(1 + \frac{\underline{Z}_1'}{\underline{Z}_2} \right) \underline{U}_2 + \left(\underline{Z}_1' + \underline{Z}_1'' + \frac{\underline{Z}_1' \underline{Z}_1''}{\underline{Z}_2} \right) \underline{I}_2$$

$$\underline{I}_1 = \frac{1}{\underline{Z}_2} \underline{U}_2 + \left(1 + \frac{\underline{Z}_1''}{\underline{Z}_2} \right) \underline{I}_2$$

Data mreža je simetrična što znači da se može realizovati pomoću simetrične „T“ mreže, za koju važi


$$\underline{Z}_1' = \underline{Z}_1''$$

Upoređivanjem sistema jednačina „a“ parametara jedne i druge mreže dolazi se do


$$\underline{a}_{21} = \frac{1}{j\omega kL + \frac{1}{j\omega C}} = \frac{1}{\underline{Z}_2} \rightarrow \underline{Z}_2 = j\omega kL + \frac{1}{j\omega C}$$

$$\underline{a}_{22} = \frac{1 - \omega^2 LC}{1 - \omega^2 kLC} = 1 + \frac{\underline{Z}_1''}{\underline{Z}_2} \rightarrow \underline{Z}_1' = \underline{Z}_1'' = \left(\frac{1 - \omega^2 LC}{1 - \omega^2 kLC} - 1 \right) \underline{Z}_2 = j\omega L(1 - k)$$


Dakle, ekvivalentna „T“ šema ima oblik

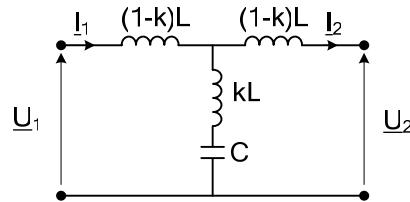

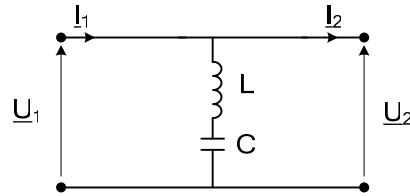b) u slučaju kada je koeficijent sprege kalemova jednak 1, mreža prelazi u



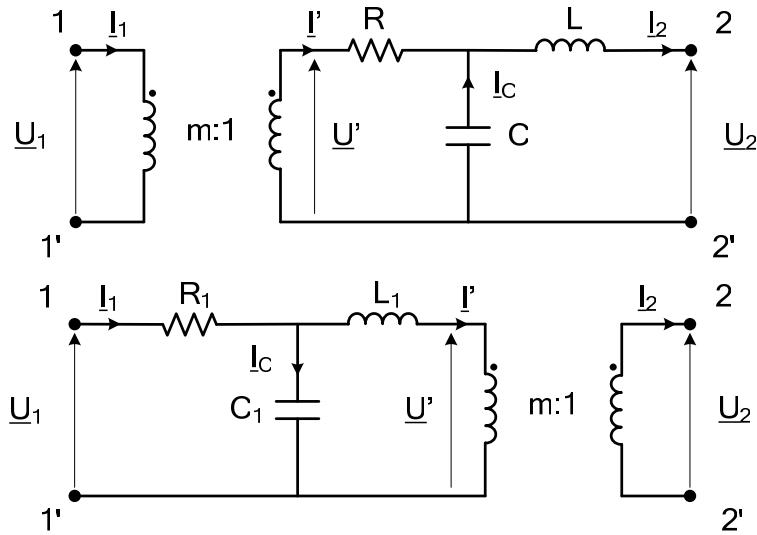6. Koji odnos mora postojati između parametara L i L_1 , C i C_1 , R i R_1 da bi mreže sa dva para krajeva prema slici bile ekvivalentne.



R

Ako se napiše sistem jednačina pomoću „z“ parametara

$$\underline{U}_1 = \underline{Z}_{11} \underline{I}_1 + \underline{Z}_{12} (-\underline{I}_2)$$

$$\underline{U}_2 = \underline{Z}_{21} \underline{I}_1 + \underline{Z}_{22} (-\underline{I}_2)$$

Za prvu mrežu važi

$$\frac{\underline{U}_1}{\underline{U}'} = m \quad \frac{\underline{I}_1}{\underline{I}'} = \frac{1}{m} \quad \underline{I}_C = \underline{I}_2 - \underline{I}' \rightarrow \underline{U}' = \frac{1}{m} \underline{U}_1 \quad \underline{I}' = m \underline{I}_1 \quad \underline{I}_C = \underline{I}_2 - m \underline{I}_1$$

tada slijedi

$$\underline{U}' = R\underline{I}' - \frac{1}{j\omega C} \underline{I}_C = Rm \underline{I}_1 - \frac{1}{j\omega C} (\underline{I}_2 - m \underline{I}_1) = \left(Rm + \frac{m}{j\omega C} \right) \underline{I}_1 + \frac{1}{j\omega C} (-\underline{I}_2)$$

$$\frac{1}{m} \underline{U}_1 = \left(Rm + \frac{m}{j\omega C} \right) \underline{I}_1 + \frac{1}{j\omega C} (-\underline{I}_2) / \cdot m$$

$$\underline{U}_1 = \left(Rm^2 + \frac{m^2}{j\omega C} \right) \underline{I}_1 + \frac{m}{j\omega C} (-\underline{I}_2) \rightarrow \underline{z}_{11} = Rm^2 + \frac{m^2}{j\omega C} \quad \underline{z}_{12} = \frac{m}{j\omega C}$$

a napon na krajevima 2-2' je

$$\underline{U}_2 = -j\omega L \underline{I}_2 - \frac{1}{j\omega C} \underline{I}_C = -j\omega L \underline{I}_2 - \frac{1}{j\omega C} (\underline{I}_2 - m \underline{I}_1)$$

$$\underline{U}_2 = \frac{m}{j\omega C} \underline{I}_1 + \left(j\omega L + \frac{1}{j\omega C} \right) (-\underline{I}_2) \rightarrow \underline{z}_{21} = \frac{m}{j\omega C} \quad \underline{z}_{22} = j\omega L + \frac{1}{j\omega C}.$$

Ako se posmatra druga mreža iz zadatka, važi

$$\frac{\underline{U}'}{\underline{U}_2} = m \quad \frac{\underline{I}'}{\underline{I}_2} = \frac{1}{m} \quad \underline{I}_C = \underline{I}_1 - \underline{I}' \rightarrow \underline{U}' = m \underline{U}_2 \quad \underline{I}' = \frac{1}{m} \underline{I}_2 \quad \underline{I}_C = \underline{I}_1 - \frac{1}{m} \underline{I}_2$$

tada je napon

$$\underline{U}_1 = R_1 \underline{I}_1 + \frac{1}{j\omega C_1} \underline{I}_C = R_1 \underline{I}_1 + \frac{1}{j\omega C_1} \left(\underline{I}_1 - \frac{1}{m} \underline{I}_2 \right)$$

$$\underline{U}_1 = \left(R_1 + \frac{1}{j\omega C_1} \right) \underline{I}_1 + \frac{1}{j\omega m C_1} (-\underline{I}_2) \rightarrow \underline{z}_{11} = R_1 + \frac{1}{j\omega C_1} \quad \underline{z}_{12} = \frac{1}{j\omega m C_1}.$$

Napon sa druge strane je

$$\underline{U}' = -j\omega L_1 \underline{I}' + \frac{1}{j\omega C_1} \underline{I}_C$$

$$m \underline{U}_2 = \frac{1}{j\omega C_1} \underline{I}_1 + \left(\frac{j\omega L_1}{m} + \frac{1}{j\omega C_1 m} \right) (-\underline{I}_2) / \cdot \frac{1}{m}$$

$$\underline{U}_2 = \frac{1}{j\omega m C_1} \underline{I}_1 + \left(\frac{j\omega L_1}{m^2} + \frac{1}{j\omega m^2 C_1} \right) (-\underline{I}_2) \rightarrow \underline{z}_{21} = \frac{1}{j\omega m C_1} \quad \underline{z}_{22} = \frac{j\omega L_1}{m^2} + \frac{1}{j\omega m^2 C_1}.$$

Da bi mreže bile ekvivalentne parametri moraju biti jednaki, pa važi

$$\underline{z}_{11} = \underline{z}_{21} \rightarrow Rm^2 + \frac{m^2}{j\omega C} = R_1 + \frac{1}{j\omega C_1} \rightarrow Rm^2 = R_1 \rightarrow \frac{R_1}{R} = m^2 \quad \frac{m^2}{j\omega C} = \frac{1}{j\omega C_1} \rightarrow \frac{C}{C_1} = m^2$$

$$\underline{z}_{22} = \underline{z}_{22} \rightarrow \frac{1 - \omega^2 LC}{j\omega C} = \frac{1 - \omega^2 L_1 C_1}{jm^2 \omega C_1} \rightarrow \frac{L_1}{L} = m^2.$$

Dakle, traženi odnosi su


$$\frac{R_1}{R} = \frac{L_1}{L} = \frac{C}{C_1} = m^2$$

7. Dvije mreže sa dva para krajeva vezane su kaskadno. Njihove \underline{h} matrice su:

$$\underline{h}^{(a)} = \begin{bmatrix} s & -3 \\ -s & s+3 \end{bmatrix}, \underline{h}^{(b)} = \begin{bmatrix} 4 & 1 \\ -1 & s+1 \end{bmatrix}$$

- a) odrediti \underline{h} matricu rezultujuće mreže
- b) odrediti ekvivalentnu T mrežu.

Rješenje:

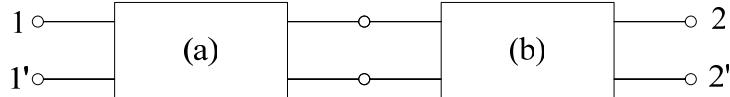

a) Za kaskadnu vezu najpovoljniji su a parametri, jer važi:

$$\underline{a} = \underline{a}^{(a)} \underline{a}^{(b)}$$

Važi da je:

$$\underline{a}^{(a)} = \frac{\begin{bmatrix} -\det\{\underline{h}^{(a)}\} & -h_{11}^{(a)} \\ -h_{22}^{(a)} & -1 \end{bmatrix}}{h_{21}^{(a)}} = \begin{bmatrix} s & 1 \\ \frac{s+3}{s} & \frac{1}{s} \end{bmatrix}$$


$$\underline{a}^{(b)} = \begin{bmatrix} 4s+5 & 4 \\ s+1 & 1 \end{bmatrix}$$

$$\underline{a} = \underline{a}^{(a)} \underline{a}^{(b)} = \begin{bmatrix} s & 1 \\ \frac{s+3}{s} & \frac{1}{s} \end{bmatrix} \begin{bmatrix} 4s+5 & 4 \\ s+1 & 1 \end{bmatrix} = \begin{bmatrix} 4s^2+6s+1 & 4s+1 \\ \frac{4s^2+18s+16}{s} & \frac{4s+13}{s} \end{bmatrix}$$

Sada se na osnovu veze \underline{a} i \underline{h} matrice nalazi:

$$\underline{h} = \begin{bmatrix} \frac{a_{12}}{a_{22}} & \frac{\det(\underline{a})}{a_{22}} \\ \frac{-1}{a_{22}} & \frac{a_{21}}{a_{22}} \end{bmatrix} = \frac{\begin{bmatrix} 4s+1 & -\frac{3}{s} \\ -1 & \frac{4s^2+18s+16}{s} \end{bmatrix}}{\frac{4s+13}{s}} = \begin{bmatrix} \frac{s(4s+1)}{4s+13} & -\frac{3}{4s+13} \\ \frac{-s}{4s+13} & \frac{4s^2+18s+16}{4s+13} \end{bmatrix}$$

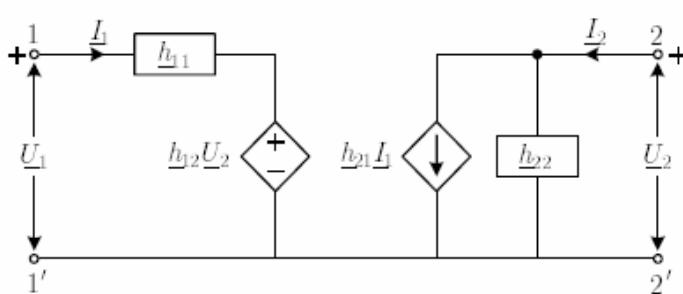b) Pošto nije ispunjen uslov $h_{12} = -h_{21}$ mreža nije recipročna. Za ekvivalentnu T mrežu nerecipročne mreže preko \underline{h} parametara dobija se šema:




$$\underline{U}_1 = h_{11} \underline{I}_1 + h_{12} \underline{U}_2$$

$$\underline{I}_2 = h_{21} \underline{I}_1 + h_{22} \underline{U}_2$$

Vrijednosti impedansi ikontrolisanih izvora su označene na slici.

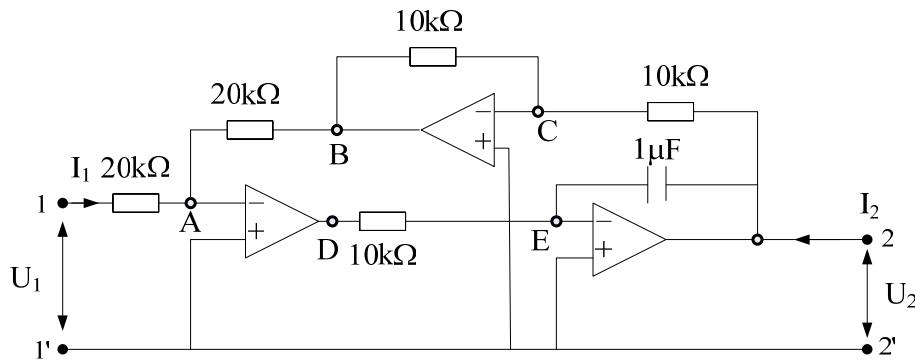8. Za kolo na slici odrediti g parametre. Nakon toga odrediti i matrice h , y , z , i a .



Rješenje:

Odredimo napone tačaka označenih na slici:

$$A: \left(\frac{1}{20} + \frac{1}{20} \right) V_A - \frac{1}{20} V_B - \frac{1}{20} V_1 = 0$$

$$C: \left(\frac{1}{10} + \frac{1}{10} \right) V_C - \frac{1}{10} V_B - \frac{1}{10} V_2 = 0$$

$$E: \left(\frac{1}{10} + s \cdot 10^{-3} \right) V_E - \frac{1}{10} V_D - s \cdot 10^{-3} V_2 = 0$$

$$V_A = V_E = V_C = 0$$

Slijedi:


$$\begin{cases} -V_1 - V_B = 0 \\ -V_B - V_2 = 0 \end{cases} \Rightarrow V_1 = V_2$$

$$-V_D - 10^{-2} s V_2 = 0$$

Treba još jedna jednačina.

$$V_1 = 20 \cdot 10^3 \cdot I_1 + V_A \Rightarrow I_1 = \frac{V_1}{20 \cdot 10^3}$$

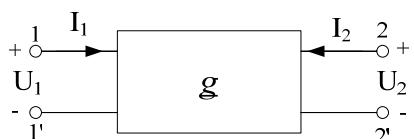g parametri su opisani sledećim relacijama:



$$\begin{bmatrix} I_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ I_2 \end{bmatrix}$$

$$\text{Tj: } \begin{aligned} I_1 &= g_{11} U_1 + g_{12} I_2 \\ U_2 &= g_{21} U_1 + g_{22} I_2 \end{aligned}$$

Iz gornjih relacija važe jednačine:

$$I_1 = g^{-1} I_1 = \frac{1}{20 \cdot 10^3} V_1 + 0 I_2 \Rightarrow \boxed{g_{11} = \frac{1}{20 \cdot 10^3}} \text{ i } \boxed{g_{12} = 0}$$

$$U_2 = V_1 + 0 I_2 \Rightarrow \boxed{g_{21} = 1} \text{ i } \boxed{g_{22} = 0}$$

Prema tome:

$$\tilde{g} = \begin{bmatrix} 1/2 \cdot 10^4 & 0 \\ 1 & 0 \end{bmatrix}, \quad \det(\tilde{g}) = 0$$

Kako je $\det(\underline{g}) = 0$, a $\underline{h} = \underline{g}^{-1}$, matrica \underline{h} ne egzistira.

$$\underline{y} = \begin{bmatrix} \frac{\det(\underline{g})}{g_{22}} & \frac{g_{12}}{g_{22}} \\ \frac{g_{22}}{g_{22}} & \frac{1}{g_{22}} \\ -\frac{g_{21}}{g_{22}} & \frac{1}{g_{22}} \end{bmatrix}, \quad g_{22} = 0, \text{ pa ni matrica } \underline{y} \text{ ne egzistira.}$$

$$\underline{a} = \begin{bmatrix} \frac{1}{g_{21}} & \frac{g_{22}}{g_{21}} \\ \frac{g_{11}}{g_{21}} & \frac{\det(\underline{g})}{g_{21}} \\ \frac{g_{21}}{g_{21}} & \frac{1}{g_{21}} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{2 \cdot 10^4} & 0 \end{bmatrix}$$

$$\underline{z} = \begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{\det(\underline{g})}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{1}{g_{11}} \end{bmatrix} = \begin{bmatrix} 2 \cdot 10^4 & 0 \\ 2 \cdot 10^4 & 0 \end{bmatrix}$$